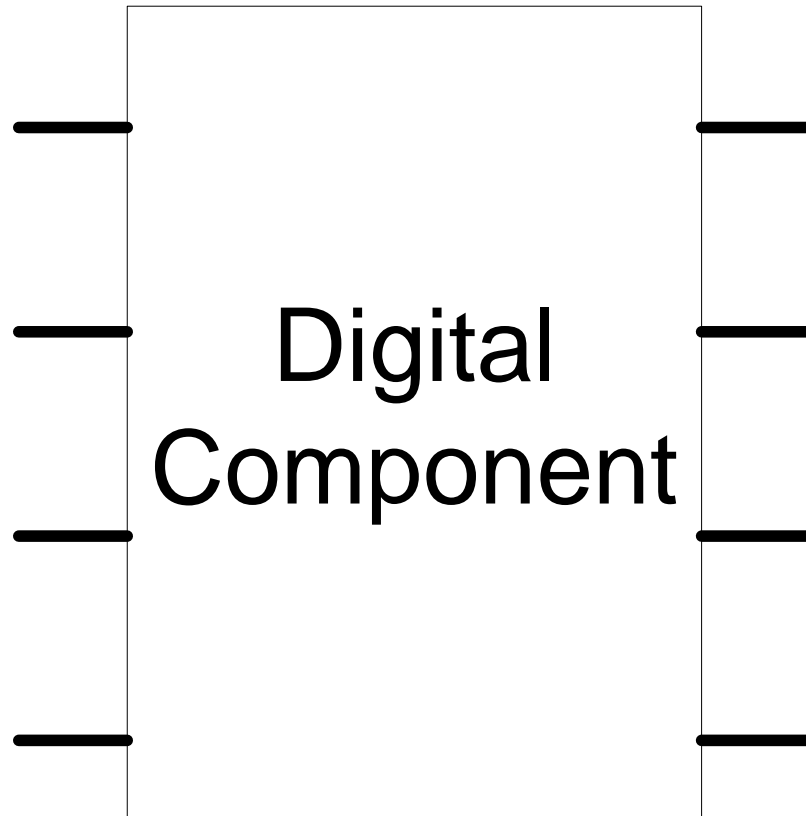


VHDL Coding Basics

Overview



VHDL structure

- **Library**
 - **Definitions, constants**
- **Entity**
 - **Interface**
- **Architecture**
 - **Implementation, function**

Libraries

- Library ieee;
- Use ieee.std_logic_1164.all;
- Use ieee.std_logic_arith.all;
- Use ieee.std_logic_signed.all;
- Use ieee.std_logic_unsigned.all;

VHDL - Library

- Include library

library IEEE;

- ***Define the library package used***

use IEEE.STD_LOGIC_1164.all;


- ***Define the library file used***

- ***For example, STD_LOGIC_1164 defines '1' as logic high and '0' as logic low***

- ***output <= '1'; --Assign logic high to output***

VHDL - Entity

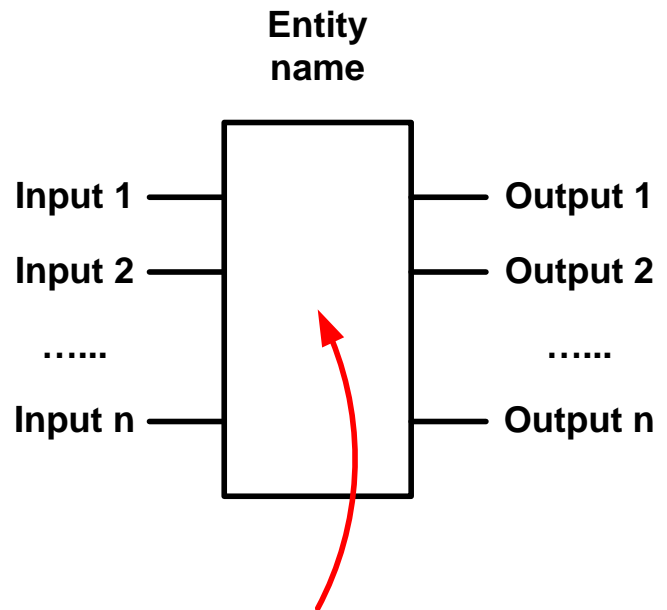- Interface for communication among different modules / components
- Define the signal port modes (INPUT and OUTPUT)



This is a black box implemented by the statements in Architecture

VHDL - Entity

- Input port can only be read inside architecture
 - `input1 <= temp;` -- This statement is NOT allowed
- Output port can only be written inside architecture
 - `temp <= output1;` -- This statement is NOT allowed

output <= inputa and inputb;

- output is assigned to be inputa AND inputb


Entity

- Define inputs and outputs
- Example:

Entity test is

```
Port( A,B,C,D: in std_logic;  
      E: out std_logic);
```


```
End test;
```

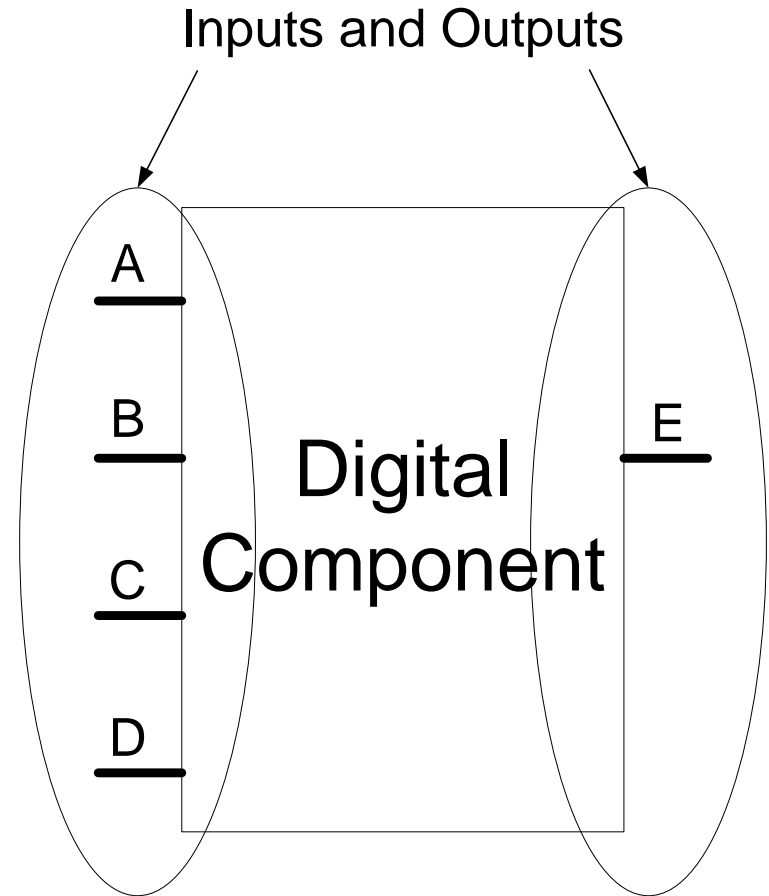

Architecture

- Define functionality of the component

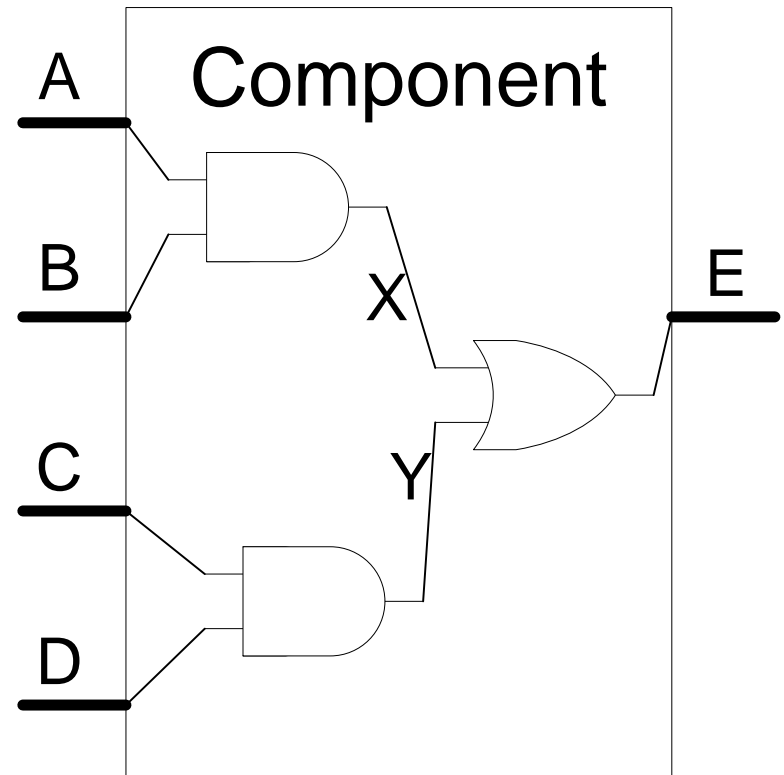
- $X \leq A \text{ AND } B;$
- $Y \leq C \text{ AND } D;$
- $E \leq X \text{ OR } Y;$



Signal

- All internal variables

Signal X,Y : std_logic;

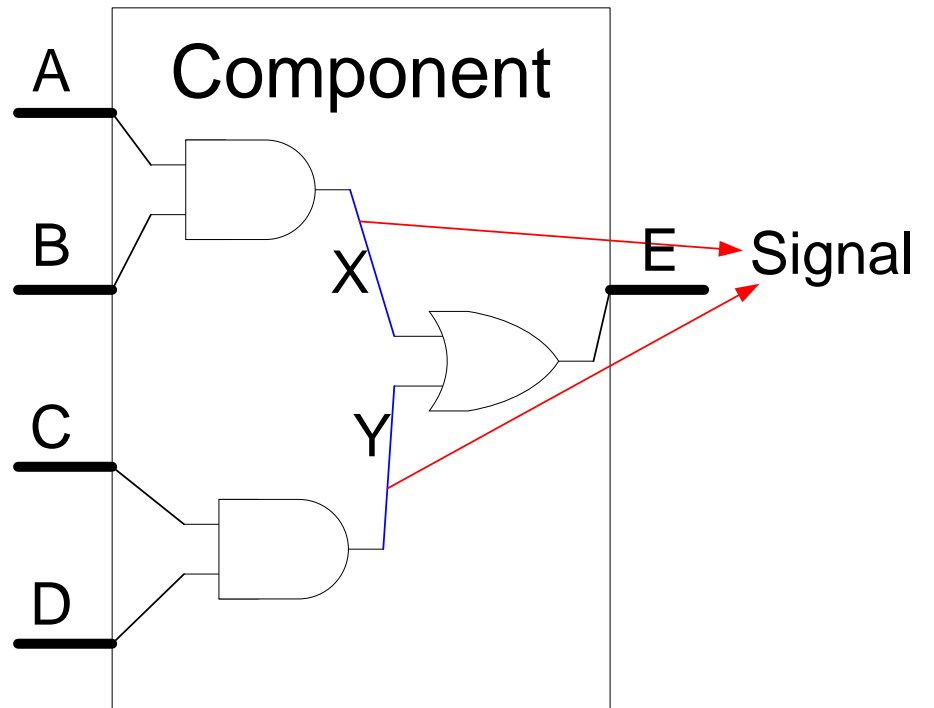

Final code

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY TEST IS
PORT (A,B,C,D : IN STD_LOGIC;
      E   : OUT STD_LOGIC);
END TEST;

ARCHITECTURE BEHAVIOR OF TEST IS
SIGNAL X,Y : STD_LOGIC;

BEGIN


    X <= A AND B;
    Y <= C AND D;
    E <= X OR Y;

END BEHAVIOR;
```

VHDL features


- **Case insensitive**
 - **inputa, INPUTA and InputA are refer to the same variable**
- **Comments**
 - **'--' until end of line**
 - **If you want to comment multiple lines, '--' need to be put at the beginning of every single line**
- **Statements are terminated by ';'**
- **Signal assignment:**
 - **'<='**
- **Variable assignment:**
 - **':='**
- **User defined names:**
 - **letters, numbers, underscores ('_')**
 - **start with a letter**

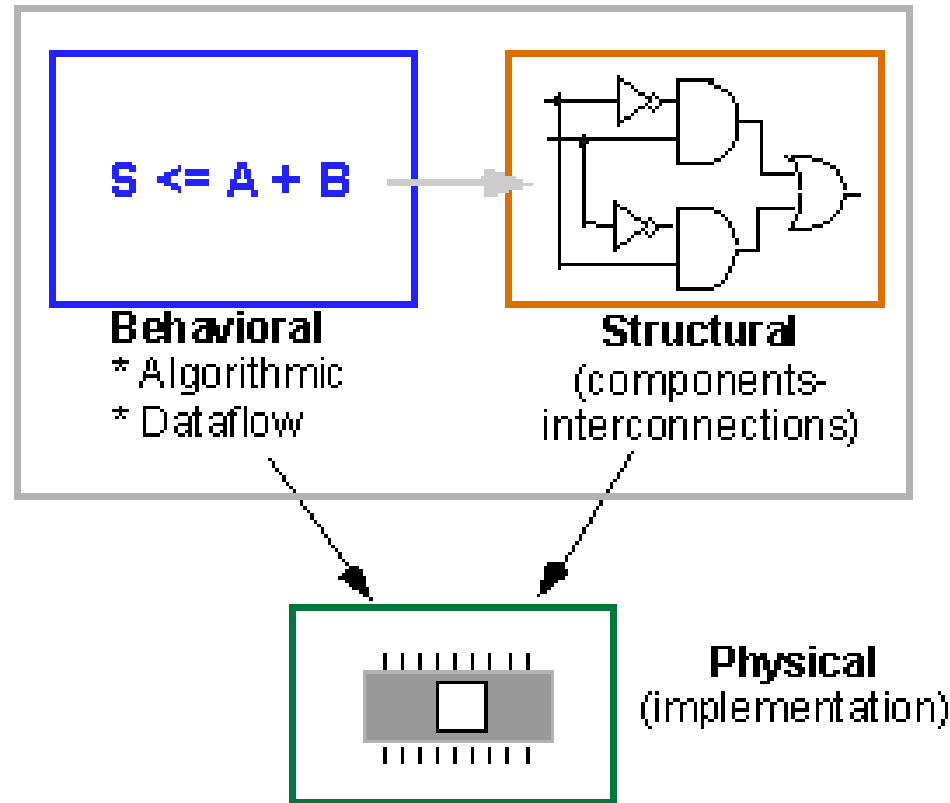Different ways to describe a digital system in VHDL



- Description of a complex system is typically a mix of both behavioral description and structural description

Structural Description

 

- $\text{WARNING} \leftarrow (\text{not DOOR and IGNITION}) \text{ or } (\text{not SBELT and IGNITION})$

Structural Description

```
architecture structural of BUZZER is
    -- Declarations
    component AND2
        port (in1, in2: in std_logic;
              out1: out std_logic);
    end component;
    component OR2
        port (in1, in2: in std_logic;
              out1: out std_logic);
    end component;
    component NOT1
        port (in1: in std_logic;
              out1: out std_logic);
    end component;
    -- declaration of signals used to interconnect gates
    signal DOOR_NOT, SBELT_NOT, B1, B2: std_logic;

begin

    -- Component instantiations statements
    U0: NOT1 port map (DOOR, DOOR_NOT);
    U1: NOT1 port map (SBELT, SBELT_NOT);
    U2: AND2 port map (IGNITION, DOOR_NOT, B1);
    U3: AND2 port map (IGNITION, SBELT_NOT, B2);
    U4: OR2 port map (B1, B2, WARNING);

end structural;
```


Port Map

Chip1 : Chip_A

Port map (A,B,C,X,Y);

Chip2 : Chip_B

Port map (X,Y,D,E);

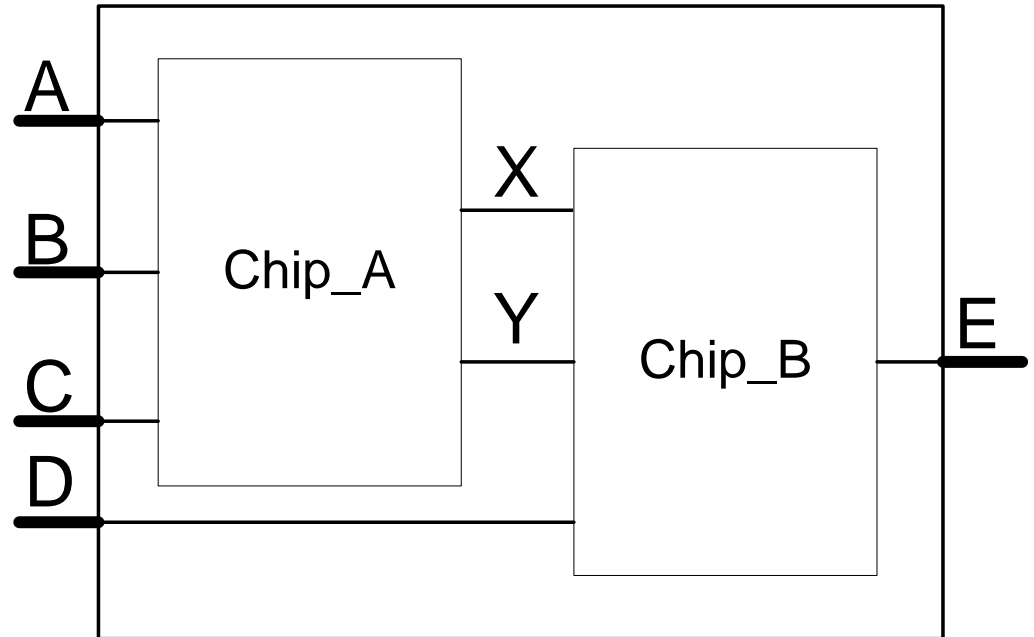

Final code

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY TEST IS  
PORT (A,B,C,D : IN STD_LOGIC;  
      E       : OUT STD_LOGIC);  
END TEST;
```

```
ARCHITECTURE BEHAVIOR OF TEST IS
```

```
SIGNAL X,Y : STD_LOGIC;
```

```
COMPONENT Chip_A  
PORT (L,M,N : IN STD_LOGIC;  
      O,P   : OUT STD_LOGIC);  
END COMPONENT;
```

```
COMPONENT Chip_B  
PORT (Q,R,S : IN STD_LOGIC;  
      T     : OUT STD_LOGIC);  
END COMPONENT;
```

```
BEGIN
```

```
Chip1 : Chip_A  
PORT MAP (A,B,C,X,Y);
```

```
Chip2 : Chip_B  
PORT MAP (X,Y,D,E);
```

```
END BEHAVIOR;
```

Port Mapping

- Two ways to associate the port signals and actual signals in an entity
 - Positional association
 - Ordering matters
(actual₀, actual₁, actual₂, ..., actual_n)
 - Named association
 - Ordering does not matter
(port₀=>actual₀, port₁=>actual₁, port₂=>actual₂, ..., port_n=>actual_n)

Structural Modeling

- Declare a list of components being used
- Declare signals which define the nets (i.e., wires) that interconnect components
- Label multiple instances of the same component so that each instance is uniquely defined

```
architecture architecture_name of NAME_OF_ENTITY is  
    -- Declarations  
        component declarations  
        signal declarations  
begin  
    -- Statements  
        component instantiation and connections  
        :  
        :  
end architecture_name;
```

Component Declaration

- Before components can be instantiated they need to be declared in the architecture declaration section

```
component component_name [is
    [port ( port_signal_names: mode type;
            port_signal_names: mode type;
            :
            port_signal_names: mode type); ]
end component [component_name];
```

```
component OR2
    port (in1, in2: in std_logic;
          out1: out std_logic);
end component;
```

Component Instantiation and Interconnections

- The component instantiation statement references a component that can be
 - Previously defined at the current level of the hierarchy
 - Defined in a technology library (e.g., vendor's library)

instance_name : *component_name*

port map (*port1*=>*signal1*, *port2*=> *signal2*,... *port3*=>*signaln*);

instance_name : *component_name*

port map (*signal1*, *signal2*,... *signaln*);

```
component NAND2
```

```
    port (in1, in2: in std_logic;
```

```
          out1: out std_logic);
```

```
end component;
```

```
signal int1, int2, int3: std_logic;
```

```
:
```

```
U1: NAND2 port map (A,B,int1);
```

```
U2: NAND2 port map (in1=>C, in2=>D, out1=>int2);
```

```
U3: NAND3 port map (int1, int2, Z);
```

Data Objects

■ Constant

- A constant can have a single value of a given type and cannot be changed
- Constants declared at the start of an architecture
 - can be used anywhere within the architecture
- Constants declared within a process
 - can only be used inside that specific process

constant *list_of_name_of_constant*: type [:= initial value] ;

```
constant RISE_FALL_TME: time := 2 ns;
```

```
constant DELAY1: time := 4 ns;
```

```
constant RISE_TIME, FALL_TIME: time:= 1 ns;
```

```
constant DATA_BUS: integer:= 16;
```

Data Objects

■ Variable

- can be updated using a variable assignment statement

Variable_name := expression;

- is updated without any delay as soon as the statement is executed
- must be declared *inside* a process
 - is local to the process

variable *list_of_variable_names*: type [:= initial value] ;

```
variable CNTR_BIT: bit :=0;
```

```
variable VAR1: boolean :=FALSE;
```

```
variable SUM: integer range 0 to 256 :=16;
```

```
variable STS_BIT: bit_vector (7 downto 0);
```

Data Objects

■ Signal

- Represent wires and storage elements
- Declared inside the architecture, outside the process
- Updated when the signal assignment statement is executed, *after a certain delay*

```
signal_name <= expression;
```

```
signal list_of_signal_names: type [ := initial value] ;
```

```
signal SUM, CARRY: std_logic;
```

```
signal CLOCK: bit;
```

```
signal TRIGGER: integer :=0;
```

```
signal DATA_BUS: bit_vector (0 to 7);
```

```
signal VALUE: integer range 0 to 100;
```


Data Objects

- Signal
 - Initial value for signals representing wires
 - Not necessary
 - Initial value for signals representing storage elements
 - Use explicit control signal, e.g., “reset” to initialize all storage elements to a pre-determined state

Difference between variables and signals

■ Example of a process using Variables

```
architecture VAR of EXAMPLE is
    signal TRIGGER, RESULT: integer := 0;
begin
    process
        variable variable1: integer :=1;
        variable variable2: integer :=2;
        variable variable3: integer :=3;

    begin
        wait on TRIGGER;
        variable1 := variable2;
        variable2 := variable1 + variable3;
        variable3 := variable2;
        RESULT <= variable1 + variable2 + variable3;
    end process;
end VAR
```

- What are the values of “variable1”, “variable2”, “variable3”, and “RESULT” after the process is executed?

Difference between variables and signals

■ Example of a process using Signals

```
architecture SIGN of EXAMPLE is
    signal TRIGGER, RESULT: integer := 0;
    signal signal1: integer :=1;
    signal signal2: integer :=2;
    signal signal3: integer :=3;
begin
    process
    begin
        wait on TRIGGER;
        signal1 <= signal2;
        signal2 <= signal1 + signal3;
        signal3 <= signal2;
        RESULT <= signal1 + signal2 + signal3;
    end process;
end SIGN;
```

- What are the values of “signal1”, “signal2”, “signal3”, and “RESULT” after the process is executed?

Data Types

- **bit** values: '0', '1'
- **boolean** values: TRUE, FALSE
- **integer** values: $-(2^{31})$ to $+(2^{31} - 1)$

- **std_logic** values: 'U','X','1','0','Z','W','H','L','-'
 - 'U' = uninitialized
 - 'X' = unknown
 - 'W' = weak 'X'
 - 'Z' = floating
 - 'H'/'L' = weak '1'/'0'
 - '-' = don't care

- **Std_logic_vector** (n downto 0);
- **Std_logic_vector** (0 upto n);

Concurrency in the Architecture

```
architecture architecture_name of NAME_OF_ENTITY is  
  -- Declarations  
    -- components declarations  
    -- signal declarations  
    :  
  
begin  
  -- Statements  
  -- Processes  
  :  
  
end architecture_name;
```

- A statement will be executed when one or more of the signals on the right hand side change their value
- A process will be executed if there is any change in the value of the signals in the sensitivity list

Process

- All statements in a process occur sequentially
 - The values of signals are assigned after a delay
- Processes typically have sensitivity list
 - If the sensitivity list is not specified, one has to include a wait statement to make sure that the process will halt
 - Cannot include both a sensitivity list and a wait statement
- Processes are used to model both sequential circuits and combinational circuits

```
Process (A,B,C)
Begin
    statements;
End process;
```

Process Statement

```
[process_label:] process [ (sensitivity_list) ] [is]  
  [ process_declarations ]  
begin  
  list of sequential statements such as:  
    signal assignments  
    variable assignments  
    case statement  
    exit statement  
    if statement  
    loop statement  
    next statement  
    null statement  
    procedure call  
    wait statement  
end process [process_label];
```

Process

■ Example: Sequential Circuit

```
library ieee;
use ieee.std_logic_1164.all;
entity DFF_CLEAR is
    port (CLK, CLEAR, D : in std_logic;
          Q : out std_logic);
end DFF_CLEAR;

architecture BEHAV_DFF of DFF_CLEAR is
begin
DFF_PROCESS: process (CLK, CLEAR)
    begin
        if (CLEAR = '1') then
            Q <= '0';
        elsif (CLK'event and CLK = '1') then
            Q <= D;
        end if;
    end process;
end BEHAV_DFF;
```


Process

■ Example: Combinational Circuit

```
library ieee;
use ieee.std_logic_1164.all;
entity FULL_ADDER is
    port (A, B, Cin : in std_logic;
          Sum, Cout : out std_logic);
end FULL_ADDER;
```

```
architecture BEHAV_FA of FULL_ADDER is
    signal int1, int2, int3: std_logic;
begin
```

```
-- Process P1 that defines the first half adder
```

```
P1: process (A, B)
```

```
    begin
```

```
        int1<= A xor B;
```

```
        int2<= A and B;
```

```
    end process;
```

```
-- Process P2 that defines the second half adder and the OR -- gate
```

```
P2: process (int1, int2, Cin)
```

```
    begin
```


```
        Sum <= int1 xor Cin;
```

```
        int3 <= int1 and Cin;
```

```
        Cout <= int2 or int3;
```

```
    end process;
```

```
end BEHAV_FA;
```

 

Process

- Test
 - How to use process to model a multiplexer?

VHDL language elements

VHDL is composed of language *building blocks* that consist of more than **75 reserved words** and about 200 *descriptive words* or *word combinations*

Reserved VHDL keywords

ABS ACCESS AFTER ALIAS ALL AND ARCHITECTURE ARRAY ASSERT ATTRIBUTE BEGIN BLOCK BODY BUFFER BUS CASE COMPONENT CONFIGURATION CONSTANT	DISCONNECT DOWNTO ELSE ELSIF END ENTITY EXIT FILE FOR FUNCTION GENERATE GENERIC GROUP GUARDED IF IMPURE	IN INERTIAL INOUT IS LABEL LIBRARY LINKAGE LITERAL LOOP MAP MOD NAND NEW NEXT NOR NOT NULL	OF ON OPEN OR OTHERS OUT PACKAGE PORT POSTPONED PROCEDURE PROCESS PURE RANGE RECORD REGISTER REM REPORT ROL ROR	RETURN SELECT SEVERITY SIGNAL SHARED SLA SLL SRA SRL SUBTYPE THEN TO TRANSPORT TYPE UNAFFECTED UNITS UNTIL USE	VARIABLE WAIT WHEN WHILE WITH XNOR XOR
---	--	---	--	---	---

VHDL Operators

Class						
1. Logical operators	and	or	nand	nor	xor	xnor
2. Relational operators	=	/=	<	<=	>	>=
3. Shift operators	sll	srl	sla	sra	rol	ror
4. Addition operators	+	=	&			
5. Unary operators	+	-				
6. Multiplying op.	*	/	mod	rem		
7. Miscellaneous op.	**	abs	not			

- Logical operators are bitwise

reference

- VHDL Tutorial
 - Jan Van der Spiegel, University of Pennsylvania
 - http://www.seas.upenn.edu/~ese171/vhdl/vhdl_primer.html