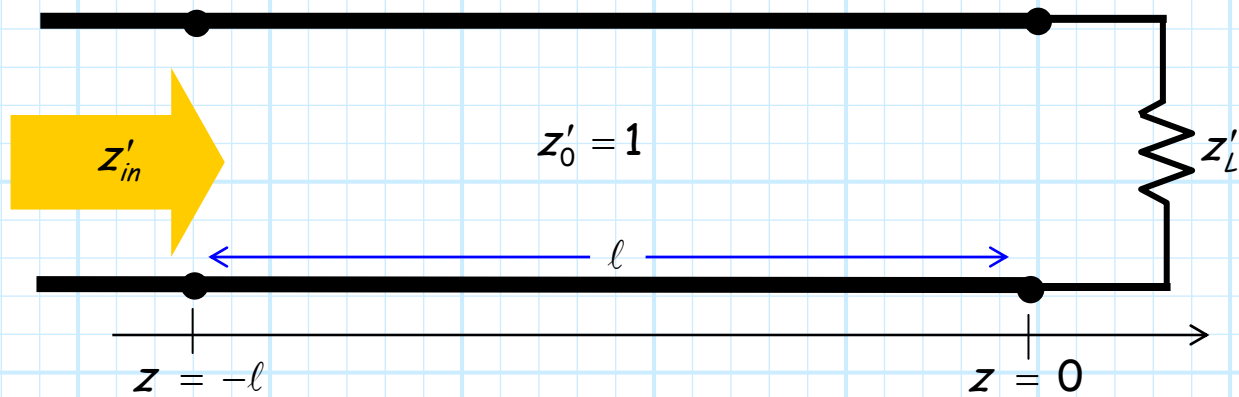


# Z<sub>in</sub> Calculations using the Smith Chart



The normalized input impedance  $z'_in$  of a transmission line length  $l$ , when terminated in normalized load  $z'_L$ , can be determined as:

$$\begin{aligned}
 z'_in &= \frac{Z_{in}}{Z_0} \\
 &= \frac{1}{Z_0} Z_0 \left( \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right) \\
 &= \frac{Z_L/Z_0 + j \tan \beta l}{1 + j Z_L/Z_0 \tan \beta l} \\
 &= \frac{z'_L + j \tan \beta l}{1 + j z'_L \tan \beta l}
 \end{aligned}$$



**Q:** Evaluating this unattractive expression looks not the least bit pleasant. Isn't there a less disagreeable method to determine  $z'_in$ ?

**A:** Yes there is! Instead, we could determine this normalized input impedance by following these **three** steps:

1. Convert  $z'_L$  to  $\Gamma_L$ , using the equation:

$$\begin{aligned}\Gamma_L &= \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} \\ &= \frac{z'_L - 1}{z'_L + 1}\end{aligned}$$

2. Convert  $\Gamma_L$  to  $\Gamma_{in}$ , using the equation:

$$\Gamma_{in} = \Gamma_L e^{-j2\beta\ell}$$

3. Convert  $\Gamma_{in}$  to  $z'_{in}$ , using the equation:

$$z'_{in} = \frac{Z_{in}}{Z_0} = \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}}$$



**Q:** But performing these **three** calculations would be even **more** difficult than the **single** step you described earlier. What short of dimwit would ever use (or recommend) this approach?

**A:** The benefit in this last approach is that **each** of the three steps can be executed using a **Smith Chart**—no complex calculations are required!

### 1. Convert $z'_L$ to $\Gamma_L$

Find the point  $z'_L$  from the impedance mappings on your Smith Chart. **Place your pencil at that point—you have now located the correct  $\Gamma_L$  on your complex  $\Gamma$  plane!**

For **example**, say  $z'_L = 0.6 - j1.4$ . We find on the Smith Chart the circle for  $r=0.6$  and the circle for  $x=-1.4$ . The **intersection** of these two circles is the point on the complex  $\Gamma$  plane corresponding to normalized impedance  $z'_L = 0.6 - j1.4$ .

This point is a **distance** of 0.685 units from the origin, and is located at **angle** of -65 degrees. Thus the value of  $\Gamma_L$  is:

$$\Gamma_L = 0.685 e^{-j65^\circ}$$

### 2. Convert $\Gamma_L$ to $\Gamma_{in}$

Since we have correctly located the point  $\Gamma_L$  on the complex  $\Gamma$  plane, we merely need to **rotate** that point **clockwise** around a circle ( $|\Gamma| = 0.685$ ) by an angle  $2\beta l$ .

When we **stop**, we are located at the point on the complex  $\Gamma$  plane where  $\Gamma = \Gamma_{in}$ !

For **example**, if the length of the transmission line terminated in  $z'_L = 0.6 - j1.4$  is  $\ell = 0.307\lambda$ , we should rotate around the Smith Chart a total of  $2\beta\ell = 1.228\pi$  radians, or  $221^\circ$ . We are now at the point on the complex  $\Gamma$  plane:

$$\Gamma = 0.685 e^{+j74^\circ}$$

**This is the value of  $\Gamma_{in}$ !**


### 3. Convert $\Gamma_{in}$ to $z'_{in}$


When you get finished rotating, and your pencil is located at the point  $\Gamma = \Gamma_{in}$ , **simply lift your pencil and determine the values  $r$  and  $x$  to which the point corresponds!**

For **example**, we can determine directly from the Smith Chart that the point  $\Gamma_{in} = 0.685 e^{+j74^\circ}$  is located at the **intersection of circles  $r = 0.5$  and  $x = 1.2$** . In other words:

$$z'_{in} = 0.5 + j1.2$$

# Step 1

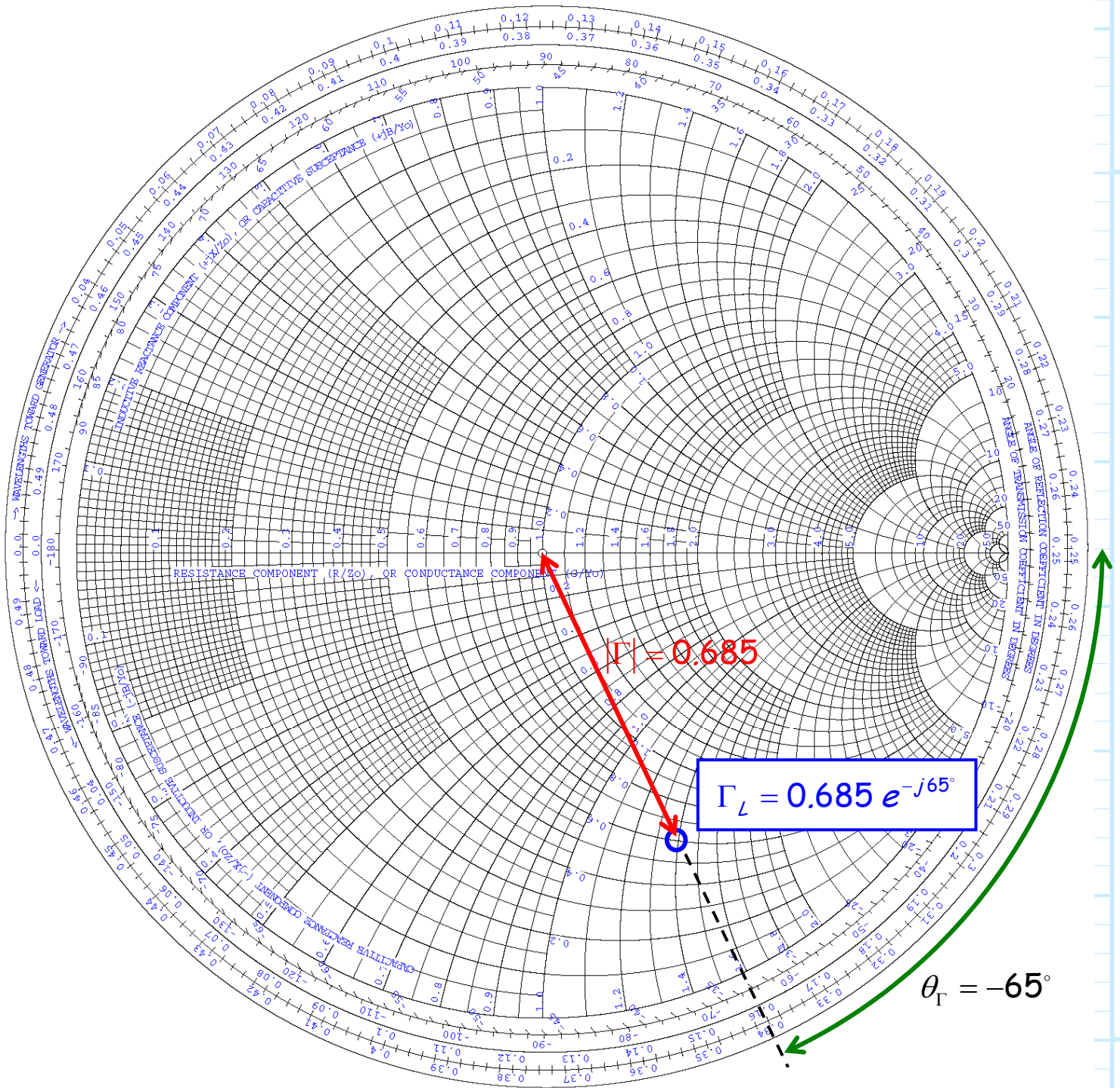

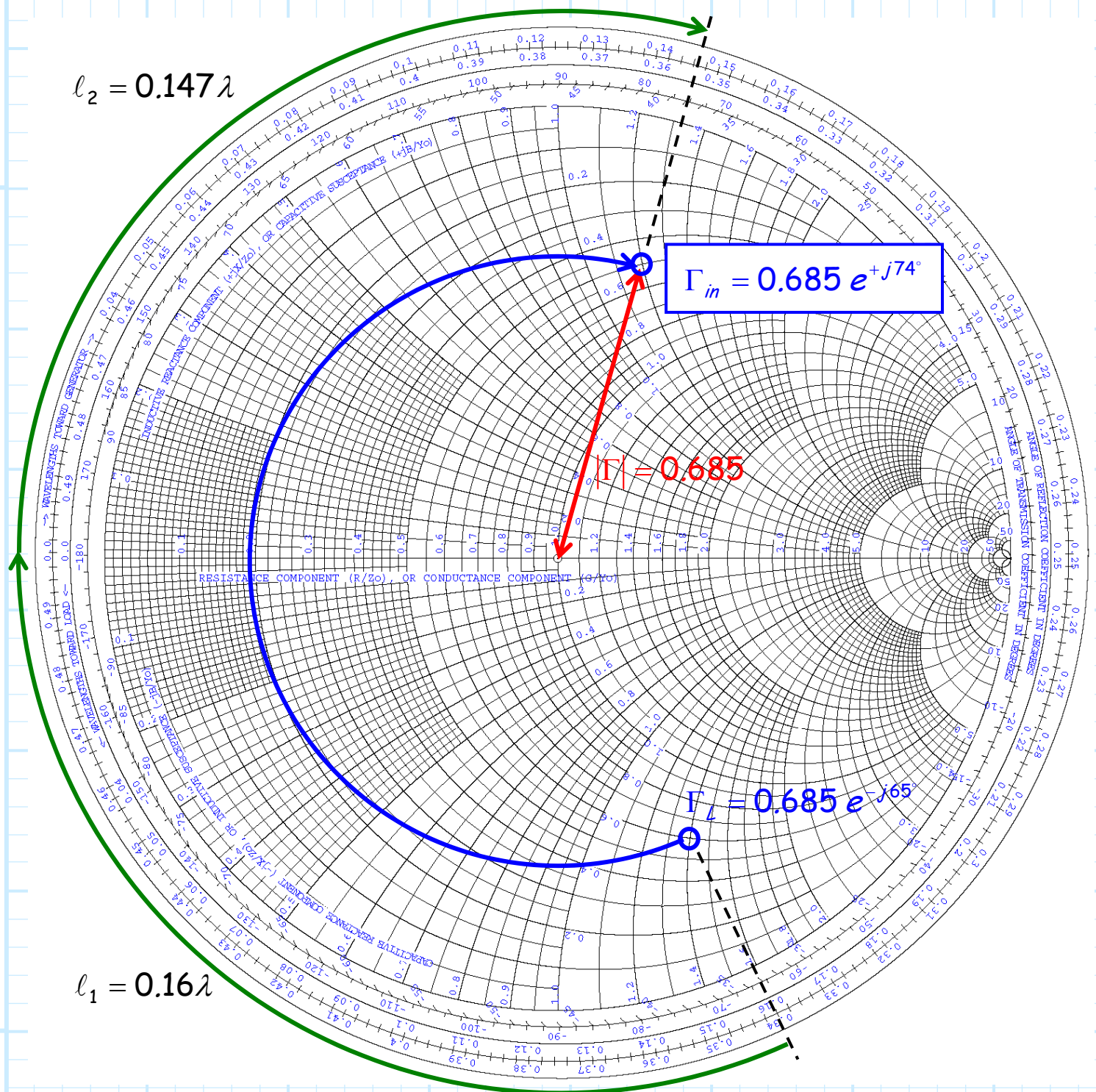**Step 2**

$$l = l_1 + l_2 = 0.160\lambda + 0.147\lambda = 0.307\lambda$$

$$2\beta l = 221^\circ$$



### Step 3

