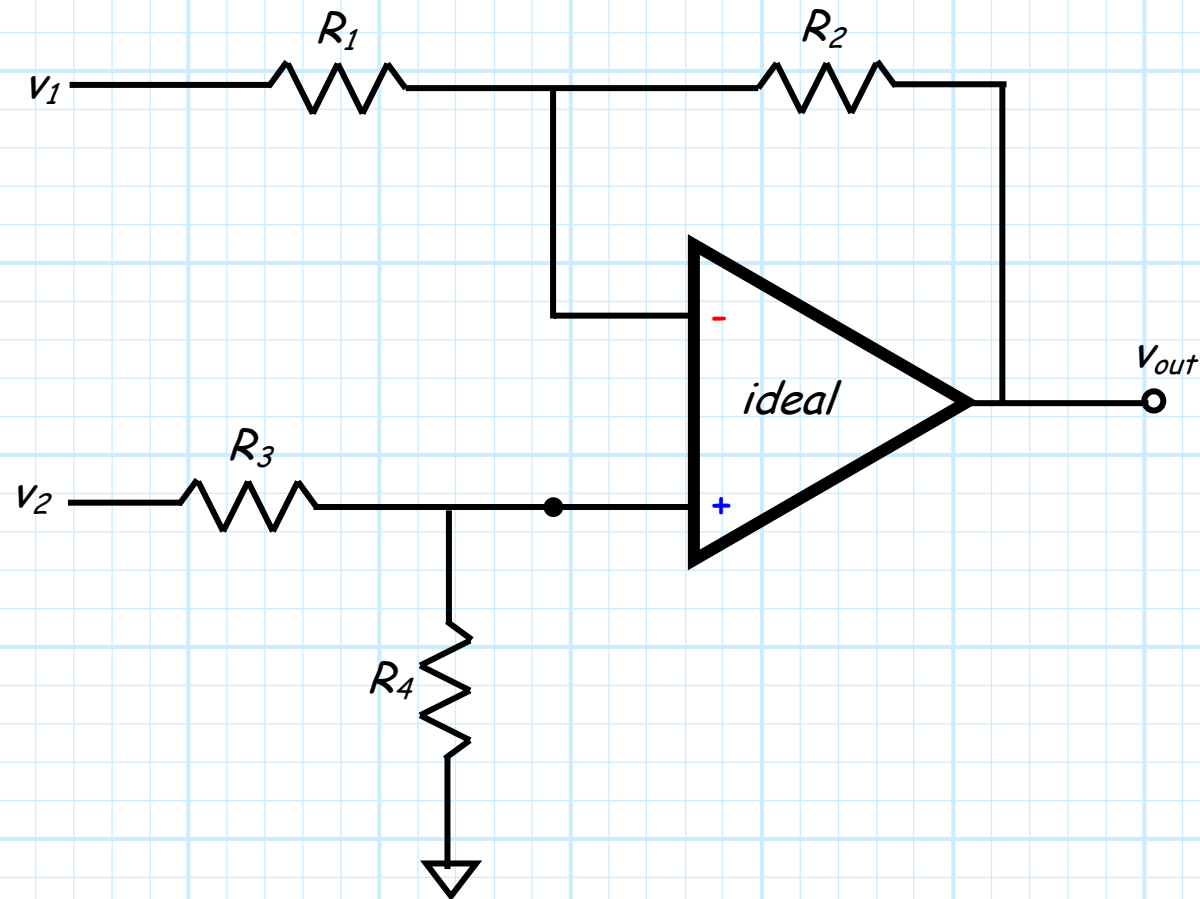


# Differential and Common-Mode Gain

Recall that in a previous handout, we analyzed **this** circuit:



## Common mode and differential mode

We found that the output is related to the inputs as:

$$v_{out} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) v_2 - \left(\frac{R_2}{R_1}\right) v_1$$

This circuit is a **weighted difference amplifier**, and typically, it is expressed in terms of its **differential gain**  $A_d$  and **common-mode gain**  $A_{cm}$ .

To understand what these gains mean, we must first define the **difference signal**  $v_d(t)$  and **common-mode signal**  $v_{cm}(t)$  of two inputs  $v_1(t)$  and  $v_2(t)$ .

## Definitions

The **difference**, as we might expect, is defined as:

$$v_d(t) \doteq v_2(t) - v_1(t)$$

whereas the **common-mode** signal is simply the **average** of the two inputs:

$$v_{cm}(t) \doteq \frac{v_2(t) + v_1(t)}{2}$$

Using these definitions, we can express the two input signals as:

$$v_2(t) = v_{cm}(t) + \frac{v_d(t)}{2}$$

$$v_1(t) = v_{cm}(t) - \frac{v_d(t)}{2}$$

## A new way to express the output

Thus, the differential signal  $v_d(t)$  and the common-mode signal  $v_{cm}(t)$  provide another way to **completely** specify input signals  $v_1(t)$  and  $v_2(t)$ —if you know  $v_d(t)$  and  $v_{cm}(t)$ , you know  $v_1(t)$  and  $v_2(t)$ .

Moreover, we can express the behavior of our **differential amplifier** in terms of  $v_d(t)$  and  $v_{cm}(t)$ . Inserting these functions into the expression of the amplifier output  $v_o(t)$ , we find:

$$\begin{aligned}
 v_{out} &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) v_2 - \left(\frac{R_2}{R_1}\right) v_1 \\
 &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) \left(v_{cm}(t) + \frac{v_d(t)}{2}\right) - \left(\frac{R_2}{R_1}\right) \left(v_{cm}(t) - \frac{v_d(t)}{2}\right) \\
 &= \frac{1}{2} \left[ \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) + \left(\frac{R_2}{R_1}\right) \right] v_d(t) \\
 &\quad + \left[ \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \left(\frac{R_2}{R_1}\right) \right] v_{cm}(t) \\
 &= \frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{2R_1 (R_3 + R_4)} v_d(t) + \frac{R_1 R_4 - R_2 R_3}{R_1 (R_3 + R_4)} v_{cm}(t)
 \end{aligned}$$

## A more "common" form

Thus, we now have an expression for the **open-circuit** output in the form:

$$v_{out}(t) = A_d v_d(t) + A_{cm} v_{cm}(t)$$

where:

$A_d \doteq$  differential gain

$A_{cm} \doteq$  common-mode gain

## Difference amplifiers should have no common-mode gain

Note that each of these gains are **open-circuit voltage** gains.

- \* An **ideal** differential amplifier has **zero** common-mode gain (i.e.,  $A_{cm}=0$ )!
- \* In other words, the output of an **ideal** differential amplifier is **independent** of the **common-mode** (i.e., average) of the two input signals.
- \* We refer to this characteristic as **common-mode suppression**.

Typically, **real** differential amplifiers exhibit **small**, but non-zero common mode gain.

## Common-Mode Rejection ratio

The **Common-Mode Rejection Ratio (CMRR)** is therefore used to indicate the **quality** of a differential amplifier:

$$\text{CMRR} = 10 \log_{10} \frac{|A_d|^2}{|A_{cm}|^2} \quad (\text{dB})$$

Note the CMRR of a **good** differential amplifier is very **large** (e.g., > 40 dB).

For our **example** circuit, we find that the differential and common-mode gain are:

$$A_d = \frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{2R_1 (R_3 + R_4)}$$

$$A_{cm} = \frac{R_1 R_4 - R_2 R_3}{R_1 (R_3 + R_4)}$$

## Common-mode gain depends on design

The ratio of these two gains is thus:

$$\frac{A_d}{A_{cm}} = \left( \frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{2R_1 (R_3 + R_4)} \right) \left( \frac{R_1 R_4 - R_2 R_3}{R_1 (R_3 + R_4)} \right)^{-1}$$

$$= \frac{1}{2} \frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{R_1 R_4 - R_2 R_3}$$

and therefore CMRR is:

$$\text{CMRR} = 10 \log_{10} \left| \frac{1}{2} \frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{R_1 R_4 - R_2 R_3} \right|^2 \quad (\text{dB})$$

It is evident that for **this** example, the common-mode gain  $A_{cm}$  is **minimized**, and thus the CMRR is **maximized**, when:

$$R_1 R_4 = R_2 R_3$$

so that  $R_1 R_4 - R_2 R_3 = 0$ .