

CS/EE 260M
Homework 3 Solutions

1. (MK 2-16)


Simplify the following Boolean functions by means of a four-variable map:

(a) $F(A,B,C,D) = \sum m (1,5,9,12,13,15)$

(b) $F(W,X,Y,Z) = \sum m (1,3,9,11,12,13,14,15)$


(c) $F(A,B,C,D) = \sum m (0,2,4,5,6,7,8,10,13,15)$

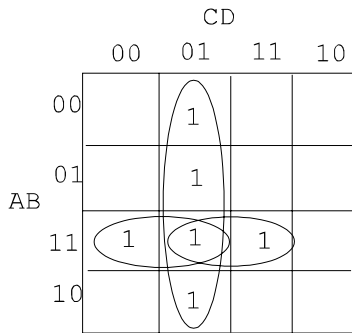(a) $F(A,B,C,D) = \sum m (1,5,9,12,13,15)$




$F = AB(C' + D) + C'D$

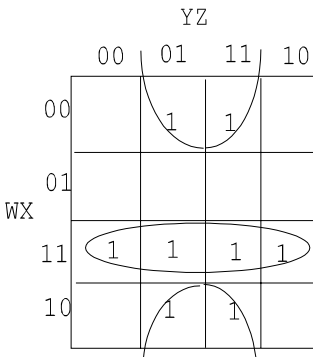(b) $F(W,X,Y,Z) = \sum m (1,3,9,11,12,13,14,15)$



$F = WX + X'Z$

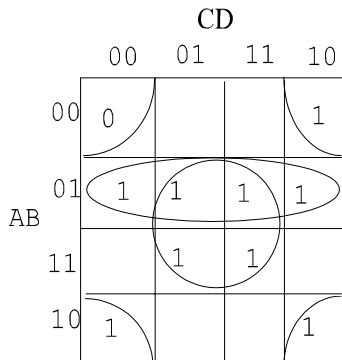(c) $F(A,B,C,D) = \sum m (0,2,4,5,6,7,8,10,13,15)$



$F = A'B + BD + B'D'$

2. (MK 2-20)


Simplify the following Boolean functions by finding all prime implicants and essential prime implicants and applying the selection rule:

(a) $F(W,X,Y,Z) = \sum m (1,5,6,7,11,12,13,15)$

(b) $F(A,B,C,D) = \sum m (1,3,4,5,7,8,9,12)$

(c) $F(W,X,Y,Z) = \sum m (0,1,2,5,6,7,8,9,10,13,14,15)$

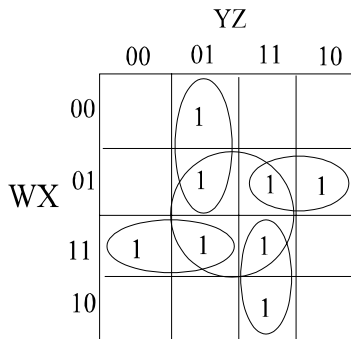(a) $F(W,X,Y,Z) = \sum m (1,5,6,7,11,12,13,15)$




prime implicants: $XZ, WXY', W'XY, W'Y'Z, WYZ$

all are essential, so

$F = XZ + WXY' + W'XY + W'Y'Z + WYZ$

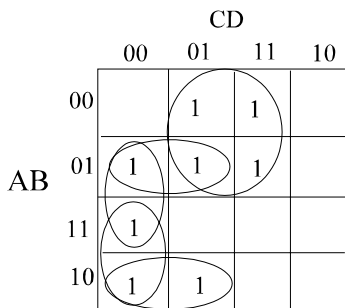(b) $F(A,B,C,D) = \sum m (1,3,4,5,7,8,9,12)$




prime implicants: $A'D, A'BC', BC'D', AC'D', AB'C'$

essential: $A'D, AB'C'$

so select $BC'D'$ to complete cover

$F = A'D + AB'C' + BC'D'$

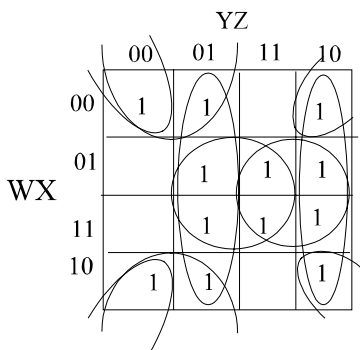(c) $F(W,X,Y,Z) = \sum m (0,1,2,5,6,7,8,9,10,13,14,15)$



prime implicants: $XZ, XY, YZ', Y'Z, X'Z', X'Y'$

essential: none

$F = XZ + YZ' + X'Y'$

3. (MK 2-23)

Simplify the following functions into (1) sum-of-products and (2) product.

(a) $F(A,B,C,D) = \sum m(2,3,5,7,8,10,12,13)$

(b) $F(W,X,Y,Z) = \prod M(2,10,13)$

(a) $F(A,B,C,D) = \sum m(2,3,5,7,8,10,12,13)$

	CD			
	00	01	11	10
00	0	0	1	1
01	0	1	1	0
11	1	1	0	0
10	1	0	0	1

1) $F = A'B'C + A'BD + ABC' + AB'D'$

2) $F' = A'B'C' + A'BD' + ABC + AB'D$

$F = (A+B+C)(A+B'+D)(A'+B'+C')(A'+B+D')$

(b) $F(W,X,Y,Z) = \prod M(2,10,13)$

	YZ			
	00	01	11	10
00	1	1	1	0
01	1	1	1	1
11	1	0	1	1
10	1	1	1	0

1) $F = XZ' + X'Y' + YZ + W'Y'$

2) $F' = X'YZ' + WXY'Z$

$F = (X+Y'+Z)(W'+X'+Y+Z')$

4. (MK 2-24)

Simplify the following Boolean functions F together with the don't-care conditions d :

(a) $F(X,Y,Z) = \sum m(0,1,2,4,5), d(X,Y,Z) = \sum m(3,6,7)$

(b) $F(A,B,C,D) = \sum m(0,6,8,13,14), d(A,B,C,D) = \sum m(2,4,10)$


(c) $F(A,B,C,D) = \sum m(1,3,5,7,9,15), d(A,B,C,D) = \sum m(4,6,12,13)$

(a) $F(X,Y,Z) = \sum m(0,1,2,4,5), d(X,Y,Z) = \sum m(3,6,7)$

	YZ			
	00	01	11	10
0	1	1	x	1
1	1	1	x	x


$F = 1$

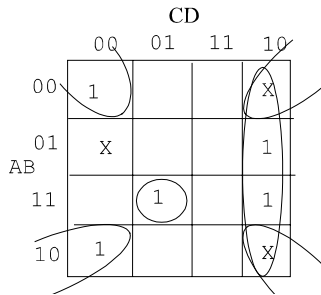(b) $F(A,B,C,D) = \sum m(0,6,8,13,14)$, $d(A,B,C,D) = \sum m(2,4,10)$



$F = CD' + B'D' + ABC'D$

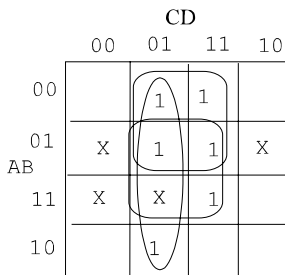(c) $F(A,B,C,D) = \sum m(1,3,5,7,9,15)$, $d(A,B,C,D) = \sum m(4,6,12,13)$




$F = C'D + A'D + BD$

5. (MK 2-27)


Simplify each of the following expressions, and implement them with NAND gates. Assume that both true and complement versions of the input variables are available.

(a) $WX' + WXZ + W'Y'Z' + W'XY' + WXZ'$ (b) $XZ + XYZ' + WX'Y'$


(a) $WX' + WXZ + W'Y'Z' + W'XY' + WXZ'$

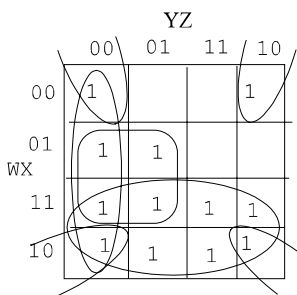


$F = XY' + W + Y'Z' + X'Z'$

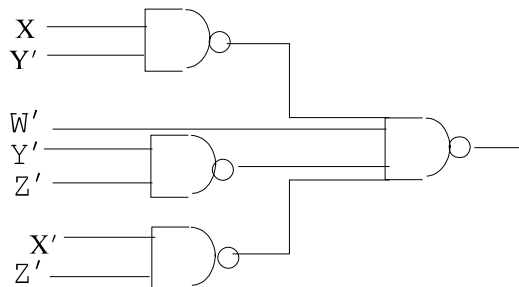

(b) $XZ + XYZ' + WX'Y'$

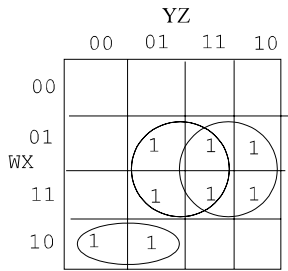

$F = XZ + XY + WX'Y'$

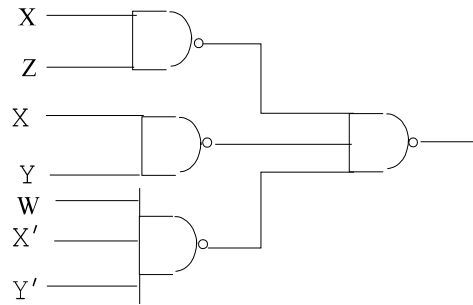


6. (MK 2-29)

Draw the NAND logic diagram for each of the following questions using a multiple-level NAND circuit:



(a) $W(X+Y+Z) + XYZ$

(b) $(A'B + CD')E + BD'(A + B)$

(a) $W(X+Y+Z) + XYZ$

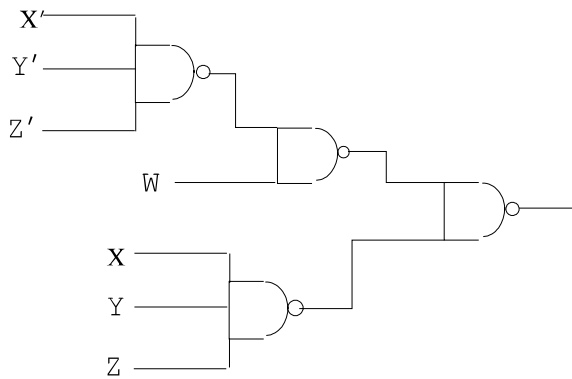


(b) $(A'B + CD')E + BD'(A + B)$

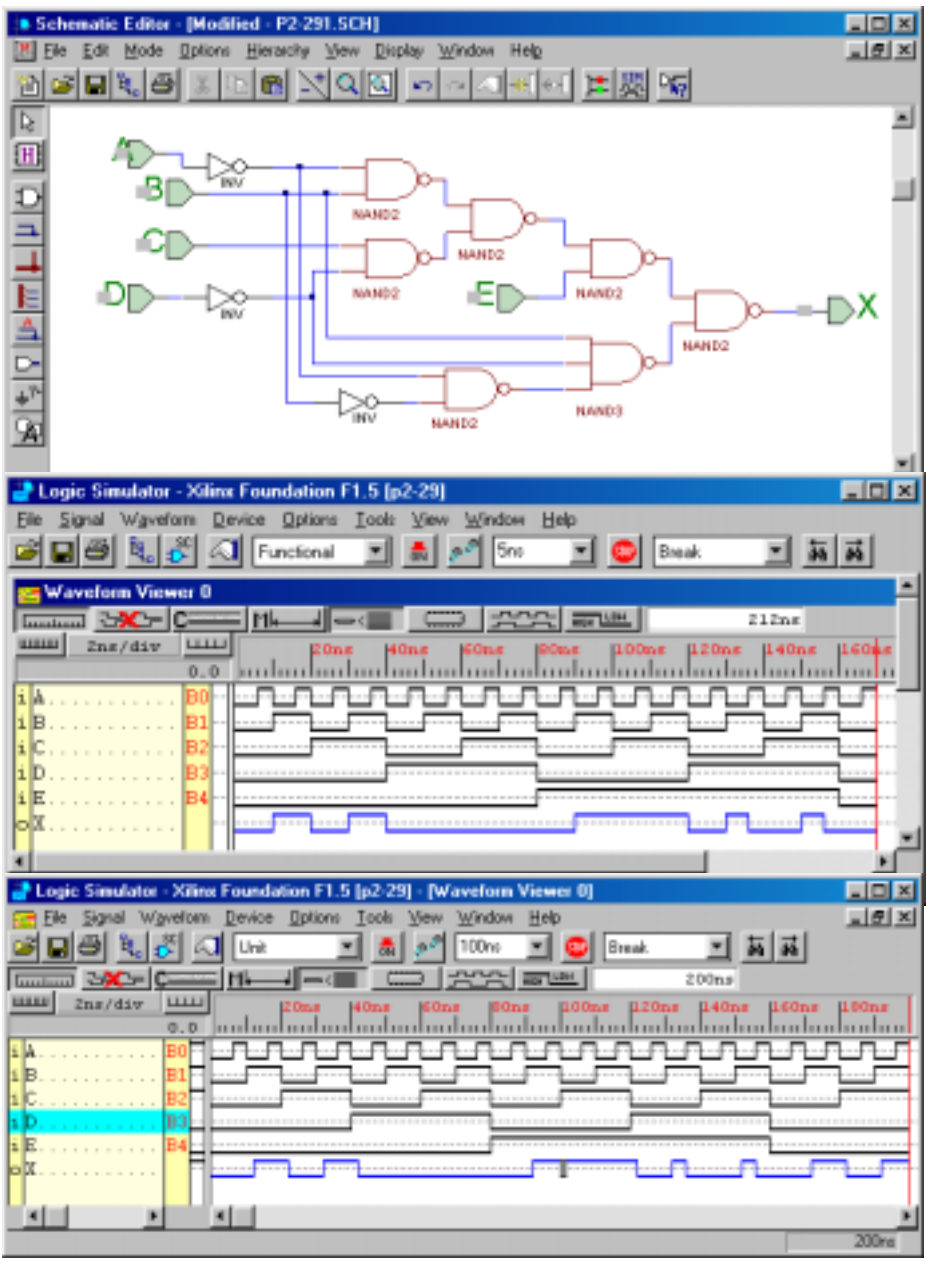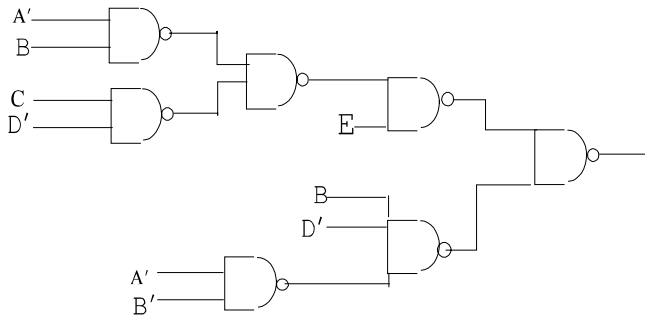


7. (MK 2-32)

Convert the AND/OR/NOT logic diagram in Figure 2-46 to a) a NAND logic diagram and b) a NOR logic diagram

a) a NAND logic diagram

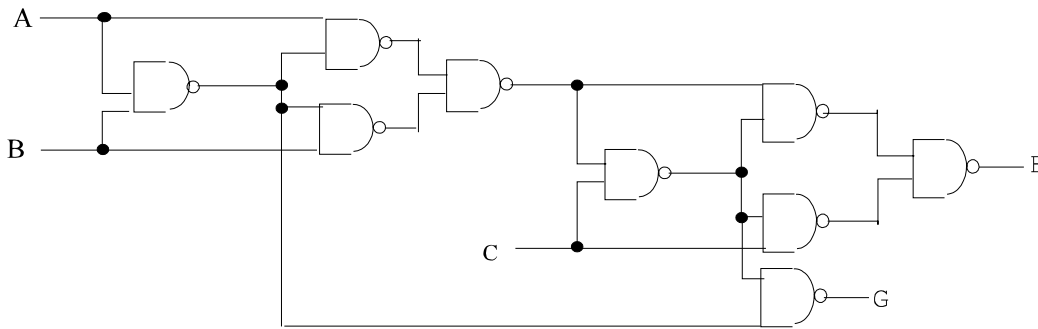

b) a NOR logic diagram

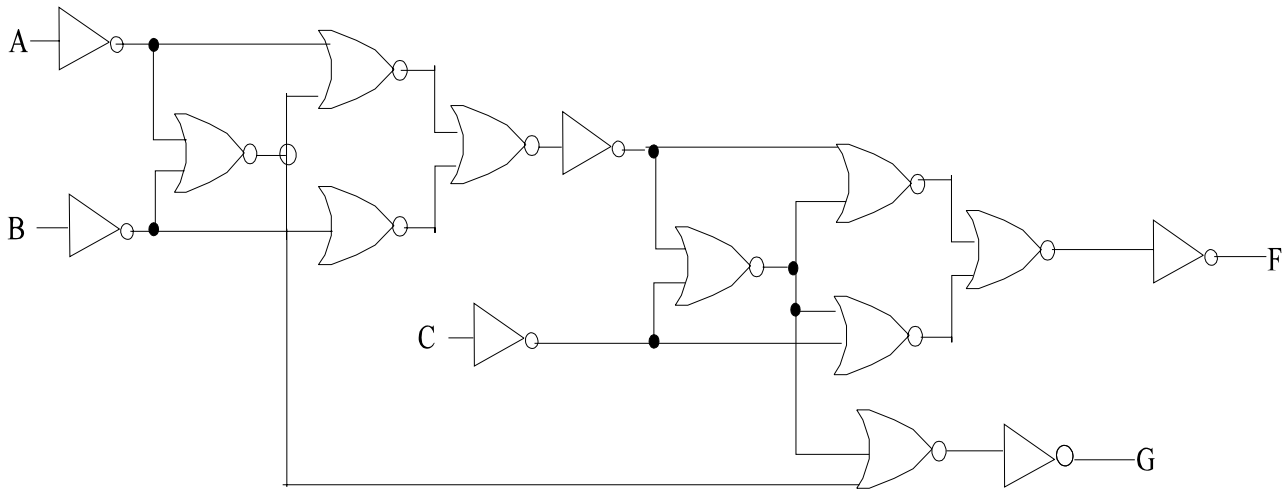

8.
When A, B or C changes, the output can change after 3 ns. This is the minimum.
Changes in C or D can cause output changes after 6 ns. This is the maximum.