


Operational Amplifier Configurations

Jaehyun Lim, Kyusun Choi

Department of Computer Science and Engineering
The Pennsylvania State University

Ideal Op-Amp

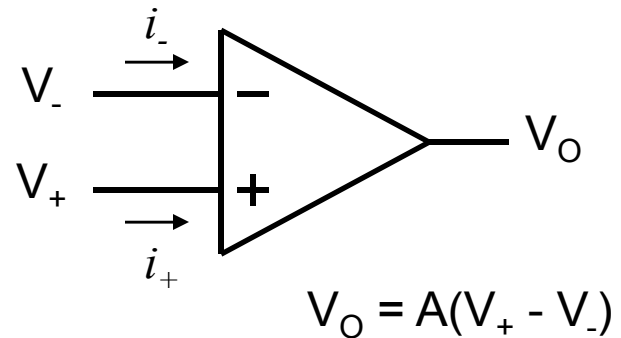- infinite voltage gain ($A = \infty$, $V_- = V_+$ for finite V_O)
- infinite input impedance ($i_- = i_+ = 0$)
- zero output impedance
- infinite bandwidth
- zero input offset



Ideal Op-Amp

■ Inverting Amplifier Configuration


- current through R_1 = current through R_f ($\because i_- = i_+ = 0$)

$$(V_{in} - V_-) / R_1 = (V_- - V_O) / R_f$$

- and

$$V_- = V_+ = 0$$

- $V_O = -(R_f / R_1) \cdot V_{in}$

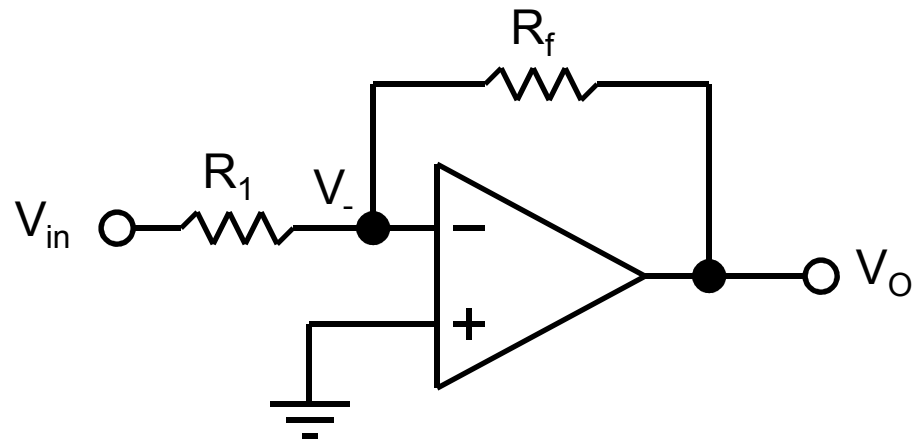

Ideal Op-Amp

■ Non-Inverting Amplifier Configuration


- current through R_1 = current through R_f ($\because i_- = i_+ = 0$)

$$(V_O - V_-) / R_f = V_- / R_1$$

- and


$$V_- = V_+ = V_{in}$$

- $V_O = (1 + R_f / R_1) \cdot V_{in}$

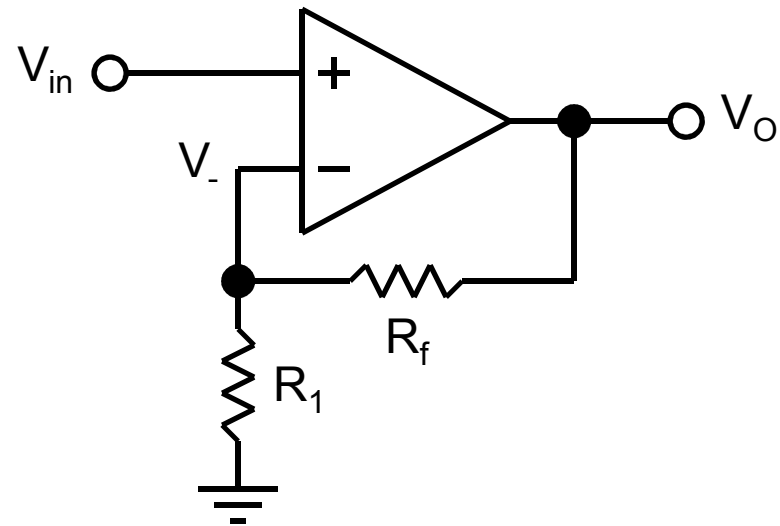

Ideal Op-Amp

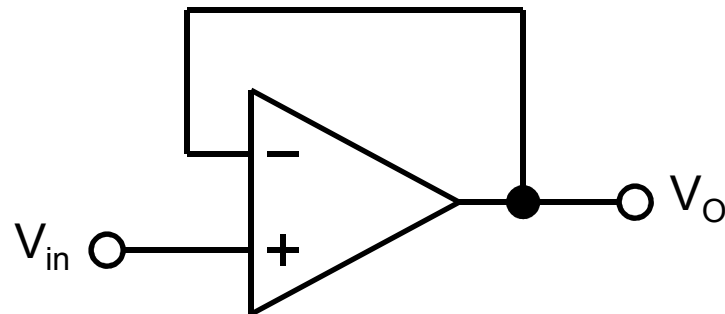- Voltage Follower (Unit Gain Buffer)
 - unit-gain non-inverting amplifier
 - $V_O = V_{in}$



Non-Ideal Op-Amp

- Real World

- gain is not infinite

- $V_- \neq V_+$

- gate current


- $i_+ \neq 0, i_- \neq 0$ (but still negligible)

- finite bandwidth

- requires frequency compensation

Non-Ideal Op-Amp

- Inverting Amplifier Configuration

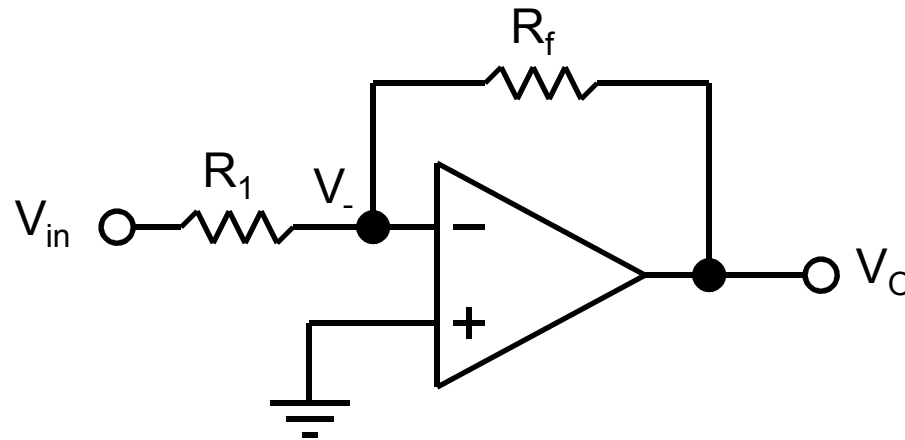


$$\left. \begin{aligned} V_O &= A(V_+ - V_-) \rightarrow V_- = -V_O / A \\ (V_{in} - V_-) / R_1 &= (V_- - V_O) / R_f \end{aligned} \right\} V_O = \frac{-R_f/R_1}{1+(1+R_f/R_1)/A} V_{in}$$

note that if $A \rightarrow \infty$, $V_O \rightarrow -(R_f / R_1)V_{in}$

Non-Ideal Op-Amp

- Non-Inverting Amplifier Configuration

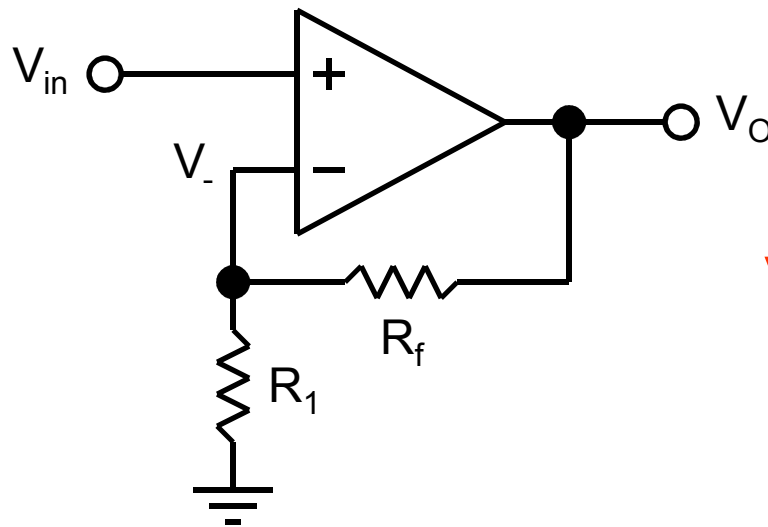


$$V_O = \frac{A}{1 + \frac{R_1}{R_1 + R_f} A} V_{in}$$

note that if $A \rightarrow \infty$, $V_O \rightarrow (1 + R_f / R_1) V_{in}$


Op-Amp with Single Supply

- Inverting Amplifier Configuration

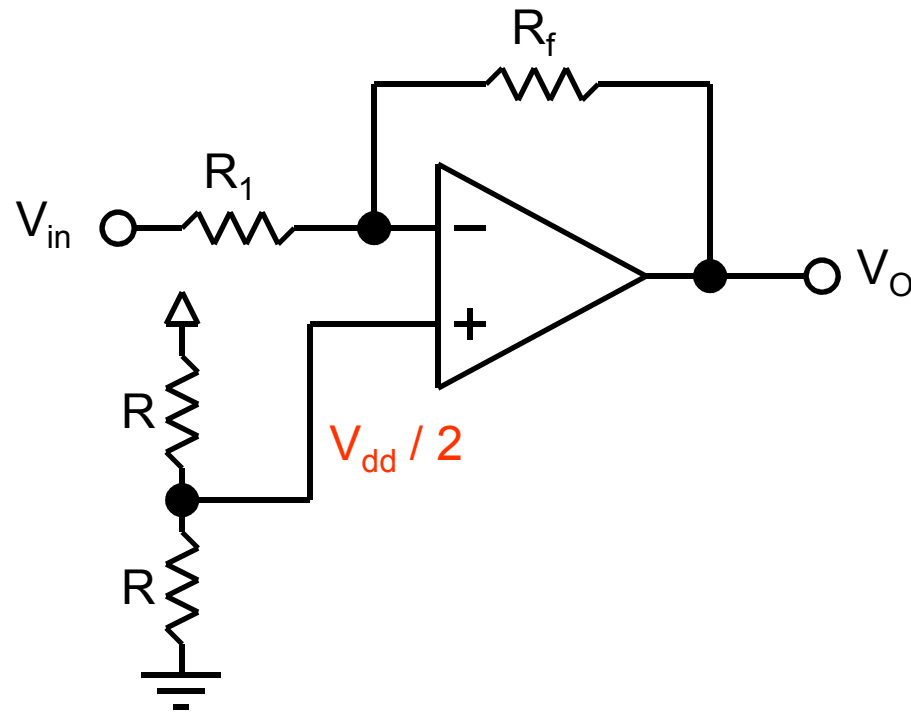

Op-Amp with Single Supply



- Non-Inverting Amplifier Configuration

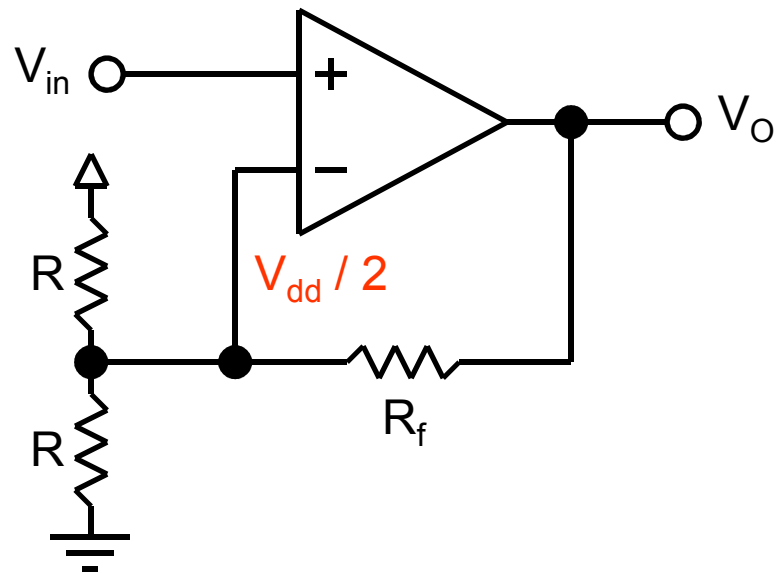

Op-Amp with Single Supply

- Amplifier Design

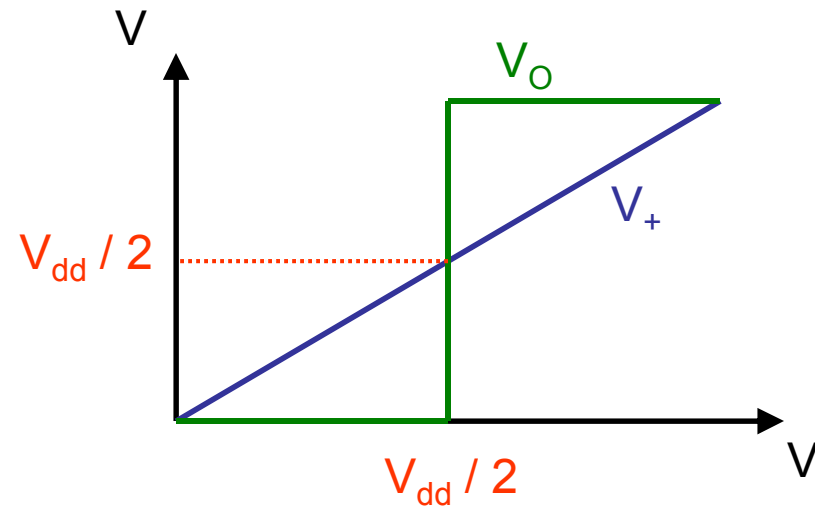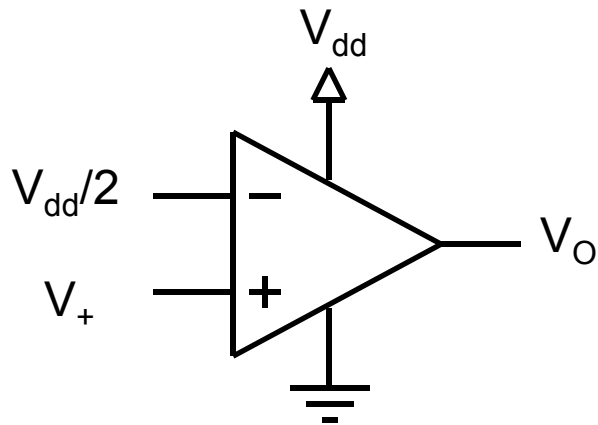
- well-designed amplifier should have a transition point centered at $V_{dd} / 2$



Op-Amp with Single Supply

- Examples from Last Class

- voltage comparator

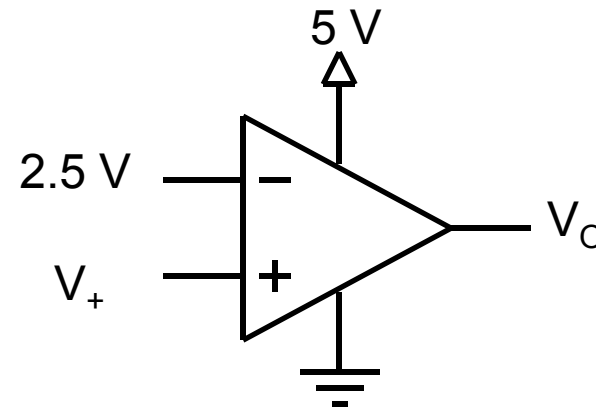

- $V_+ = 2.5\text{ V} \rightarrow V_O = ?$


- $V_+ = 2.501\text{ V} \rightarrow V_O = ?$

- $V_+ = 2.499\text{ V} \rightarrow V_O = ?$

Op-Amp with Single Supply

■ Examples from Last Class

- ideal case (gain = ∞)

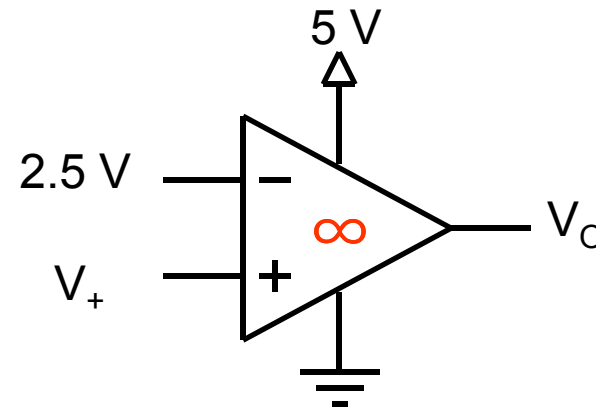


- $V_+ = 2.5 \text{ V} \rightarrow V_O = 2.5 \text{ V}$
($V_+ = V_-$ for finite V_O and V_O centered at 2.5 V)
- $V_+ = 2.501 \text{ V} \rightarrow V_O = 2.5 + A(V_+ - V_-) = \infty$
 $\rightarrow V_O = 5 \text{ V}$ (limited to supply)
- $V_+ = 2.449 \text{ V} \rightarrow V_O = 2.5 + A(V_+ - V_-) = -\infty$
 $\rightarrow V_O = 0 \text{ V}$ (limited to supply)

Op-Amp with Single Supply

■ Examples from Last Class


- gain $A = 1000$

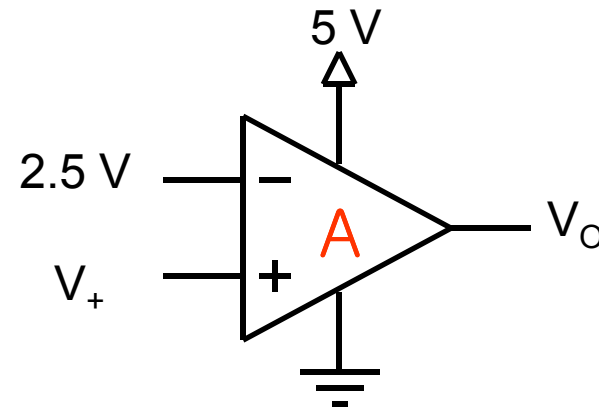

- $V_+ = 2.5\text{ V} \rightarrow V_O = 2.5\text{ V}$ (V_O centered at 2.5 V)
- $V_+ = 2.501\text{ V} \rightarrow V_O = 2.5 + 1000(V_+ - V_-) = 3.5\text{ V}$
- $V_+ = 2.449\text{ V} \rightarrow V_O = 2.5 + 1000(V_+ - V_-) = 1.5\text{ V}$

Op-Amp with Single Supply

■ HSpice Simulation

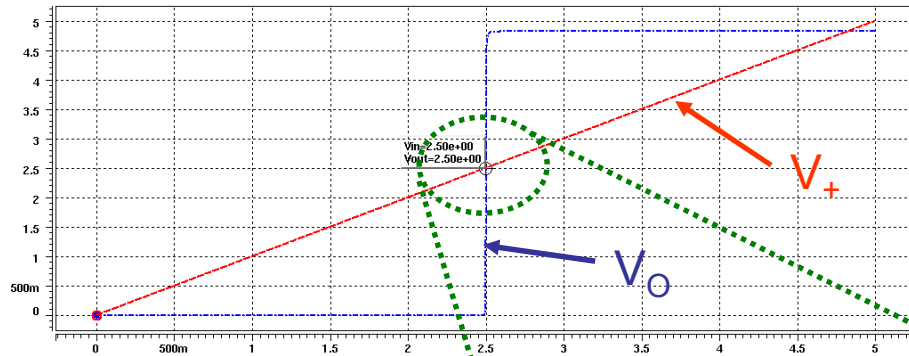

- .DC analysis
- centered at 2.5 V
- gain $\approx 1,175$
- $V_+ = 2.501 \text{ V} \rightarrow V_O = 3.421 \text{ V}$
- $V_+ = 2.449 \text{ V} \rightarrow V_O = 1.324 \text{ V}$

