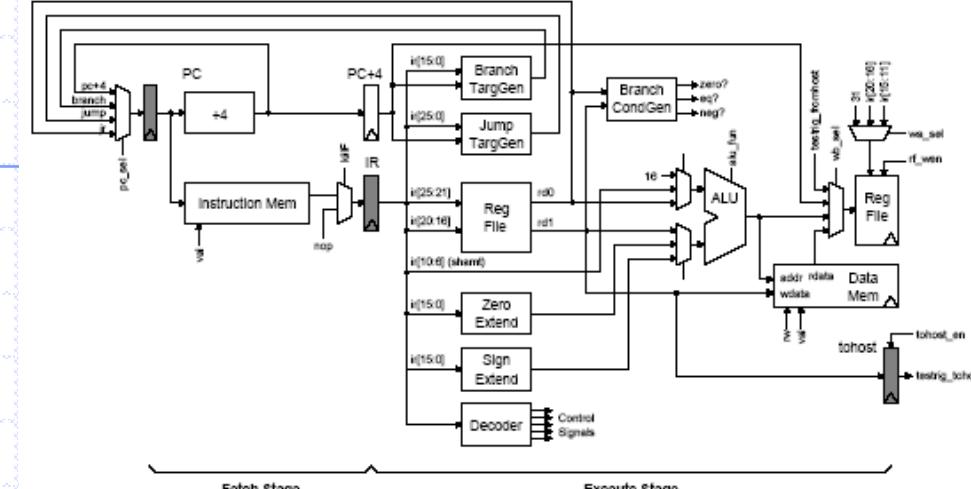


Verilog 2 - Design Examples



Courtesy of Arvind

L03-1

Verilog can be used at several levels

High-Level Behavioral



Register Transfer Level



Gate Level

A common approach is to use C/C++ for initial behavioral modeling, and for building test rigs

automatic tools to synthesize a low-level gate-level model

Writing synthesizable Verilog: Combinational logic

- ◆ Use continuous assignments (**assign**)

```
assign C_in = B_out + 1;
```

- ◆ Use **always@(*)** blocks with blocking assignments (=)

```
always @(*)
begin
    out = 2'd0;
    if (in1 == 1)
        out = 2'd1;
    else if (in2 == 1)
        out = 2'd2;
end
```

always blocks allow
more expressive control
structures, though not
all will synthesize
default

- ◆ Every variable should have a default value to avoid inadvertent introduction of latches
- ◆ Do not assign the same variable from more than one always block – ill defined semantics

Writing synthesizable Verilog: Sequential logic


- ◆ Use **always @(posedge clk)** and non-blocking assignments (**<=**)

```
always @ ( posedge clk )  
    c_out <= c_in;
```

- ◆ Use only positive-edge triggered flip-flops for state
- ◆ Do not assign the same variable from more than one always block – ill defined semantics
- ◆ Do not mix blocking and non-blocking assignments
- ◆ Only leaf modules should have functionality; use higher-level modules only for wiring together sub-modules

An example
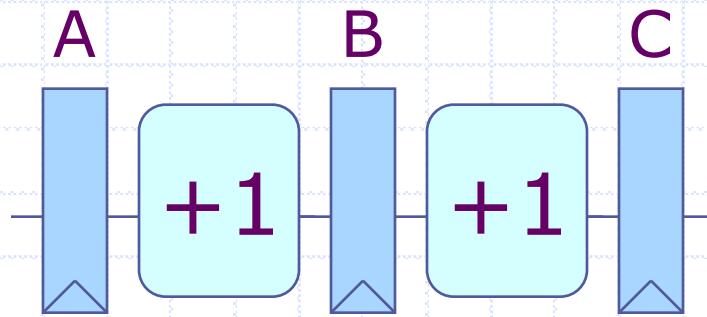
```
wire A_in, B_in, C_in;  
reg A_out, B_out, C_out;  
  
always @ ( posedge clk )  
begin  
    A_out <= A_in;  
    B_out <= A_out + 1;  
    C_out <= B_out + 1;  
end
```




The order of non-blocking assignments does not matter!

Why? Because they generate registers!

Another way

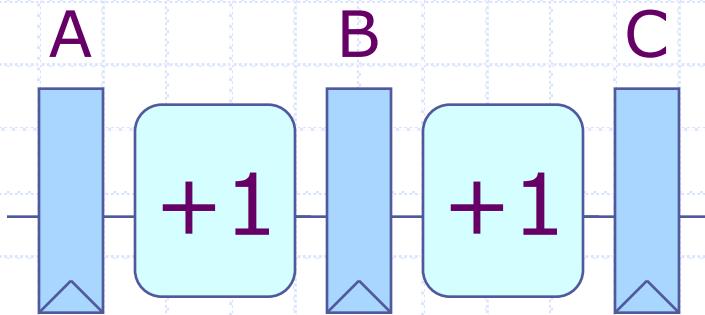
```
wire A_in, B_in, C_in;  
reg A_out, B_out, C_out;  
  
always @ ( posedge clk )  
begin  
    A_out <= A_in;  
    B_out <= B_in;  
    C_out <= C_in;  
end  
  
assign B_in = A_out + 1;  
assign C_in = B_out + 1;
```



Same behavior; we've just generated the combinational logic separately.

An example: Some wrong solutions

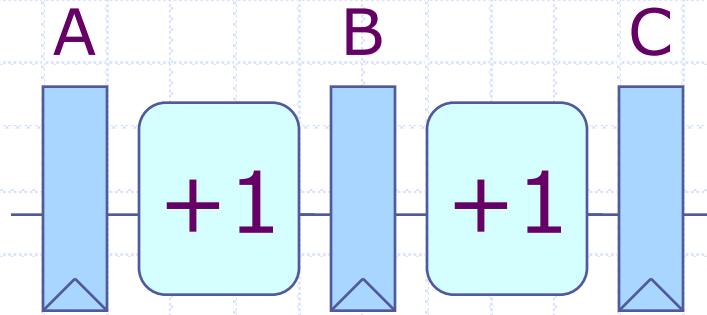
```
wire A_in, B_in, C_in;  
reg A_out, B_out, C_out;  
  
always @ ( posedge clk )  
begin  
    A_out <= A_in;  
    B_out <= B_in;  
    C_out <= C_in;  
    assign B_in = A_out + 1;  
    assign C_in = B_out + 1;  
end
```



Syntactically illegal

Another style - multiple always blocks
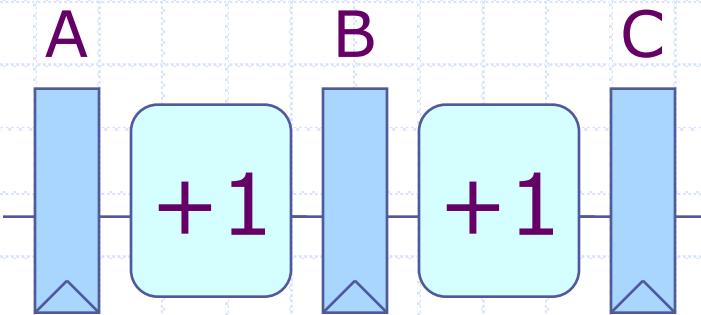
```
wire A_in, B_in, C_in;  
reg A_out, B_out, C_out;  
  
always @ ( posedge clk )  
  A_out <= A_in;  
  
assign B_in = A_out + 1;  
  
always @ ( posedge clk )  
  B_out <= B_in;  
  
assign C_in = B_out + 1;  
  
always @ ( posedge clk )  
  C_out <= C_in;
```




Does it have the same functionality?

Yes. But why?

It generates the same underlying circuit.

Yet another style – blocking assignments
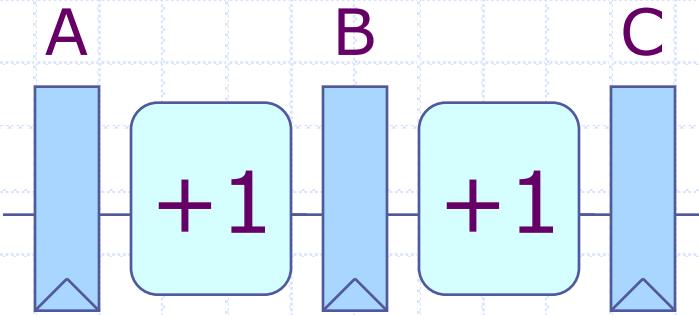
```
wire A_in, B_in, C_in;  
reg A_out, B_out, C_out;  
  
always @(posedge clk)  
begin  
    A_out = A_in;  
    B_out = B_in;  
    C_out = C_in;  
end  
  
assign B_in = A_out + 1;  
assign C_in = B_out + 1;
```



Will this synthesize?

→ Yes

Is it correct?


→ No; Do not use “blocking assignments” in @posedge clk blocks. It is forbidden in this class.

Verilog execution semantics


- Confusing
- Best solution is to write synthesizable verilog that corresponds exactly to logic you have already designed on paper, as described by the “verilog breakdown” slide.

Taylor's Simplified Verilog Semantics

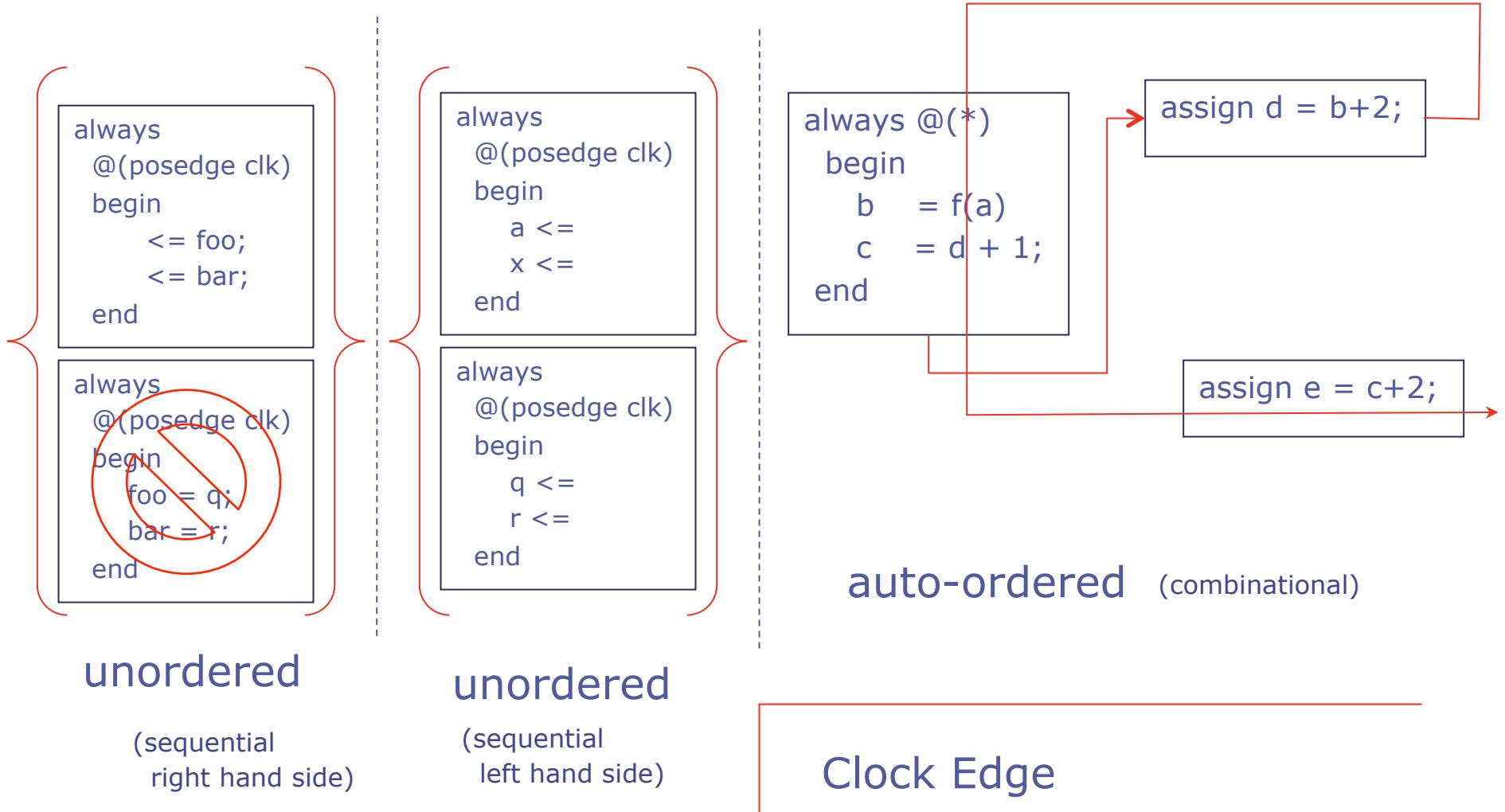If you treat verilog as a language for coding up hardware you have already designed on paper/whiteboard, you will not need to rely on this.




Taylor's Simplified Verilog Semantics

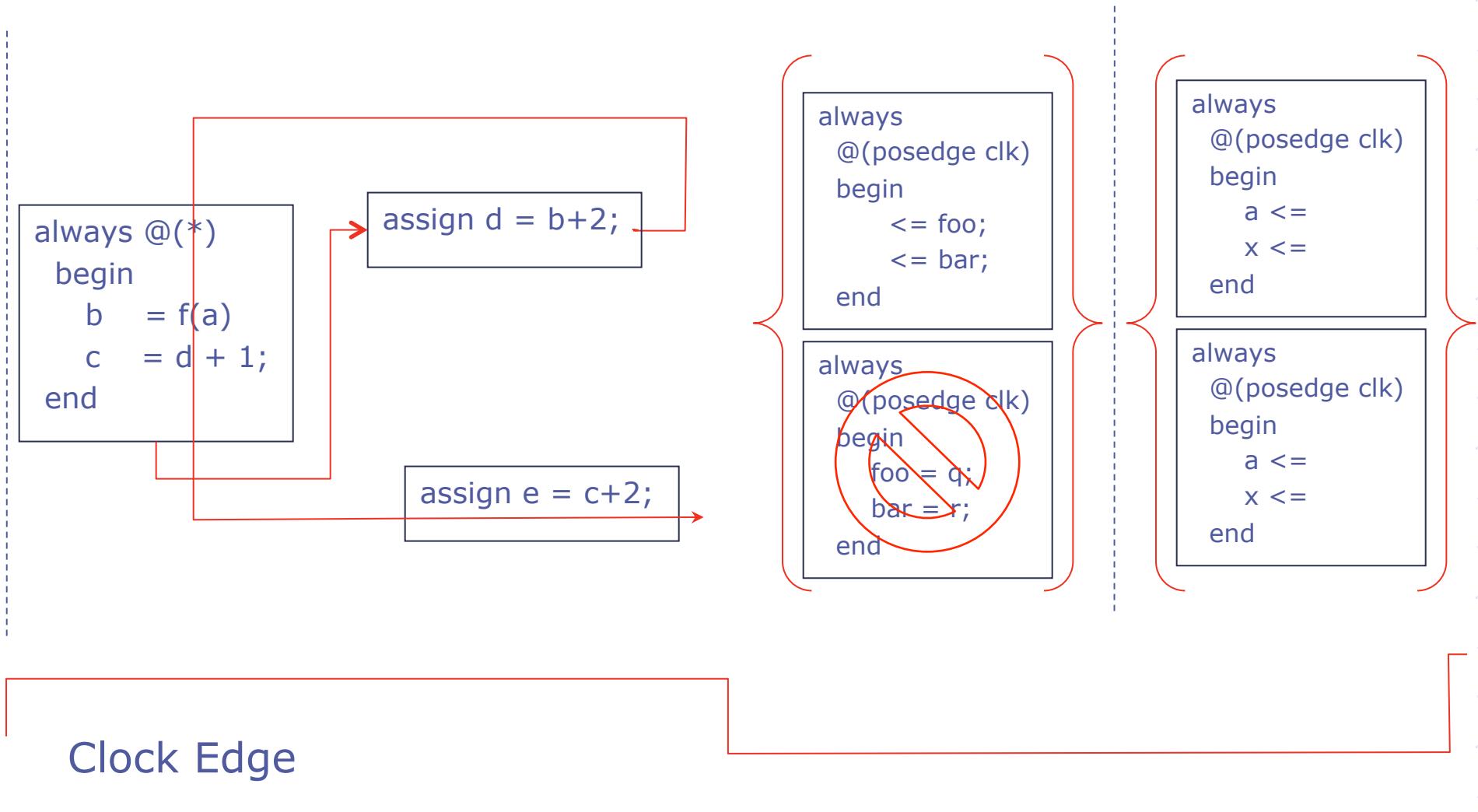

Verilog Design Examples

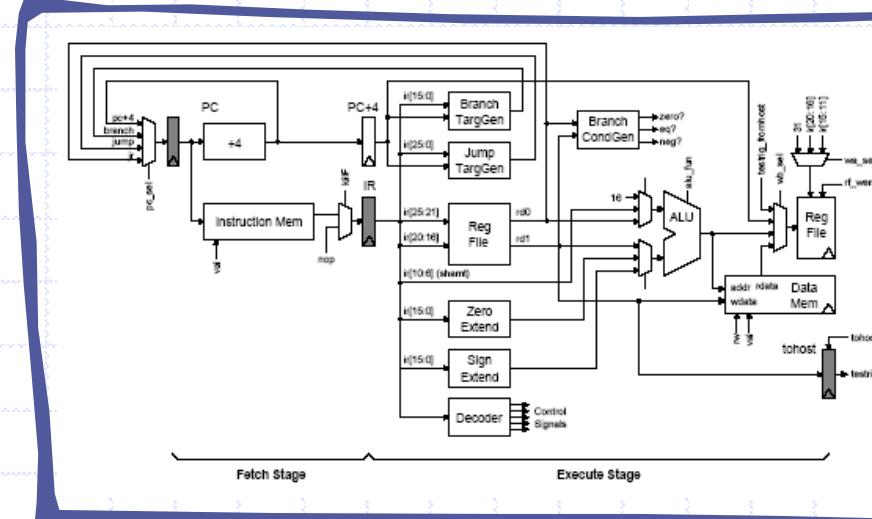- ◆ Greatest Common Divisor
- ◆ Unpipelined SMIPSv1 processor



Courtesy of Arvind

L03-13

GCD in C

```
int GCD( int inA, int inB )
{
    int done = 0;
    int A = inA;
    int B = inB;
    while ( !done )
    { if ( A < B )
        { swap = A;
        A = B;
        B = swap;
        }
        else if ( B != 0 )
            A = A - B;
        else
            done = 1;
    }
    return A;
}
```

Such a GCD description can be easily written in Behavioral Verilog

It can be simulated but it will have nothing to do with hardware, i.e. it won't synthesize.


We don't spend much time on Behavioral Verilog because it is not a particularly good language and isn't useful for hardware synthesis.

GCD in C


What does the RTL implementation need?

```
int GCD( int inA, int inB )
{
    int done = 0;
    int A = inA; ← State
    int B = inB;
    while ( !done )
    { if ( A < B ) ← Less-Than Comparator
        { swap = A;
        A = B;
        B = swap;
        }
        else if ( B != 0 ) ← Equal Comparator
            A = A - B;
        else
            done = 1;
    }
    return A;
}
```

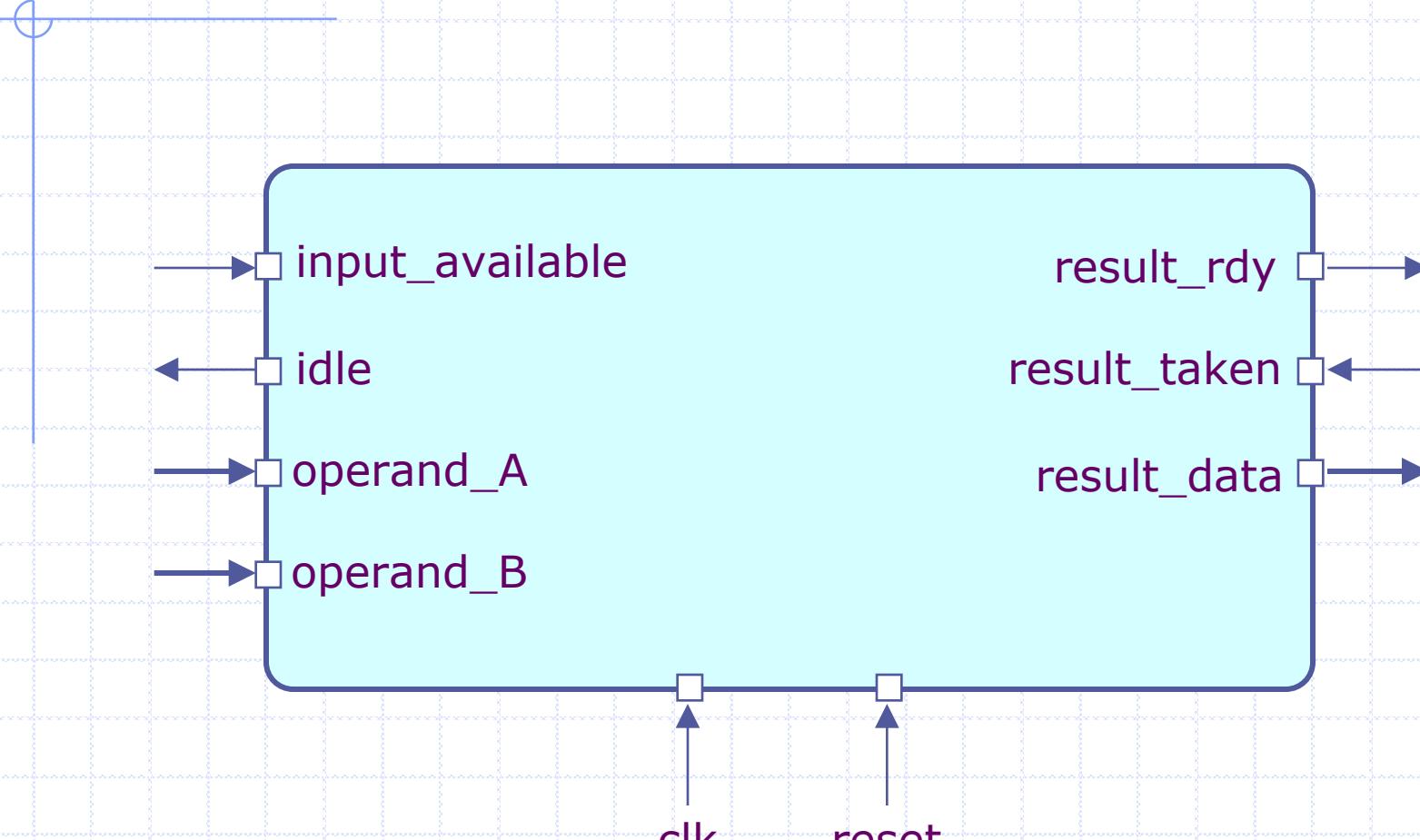Step 1: Design an appropriate port interface



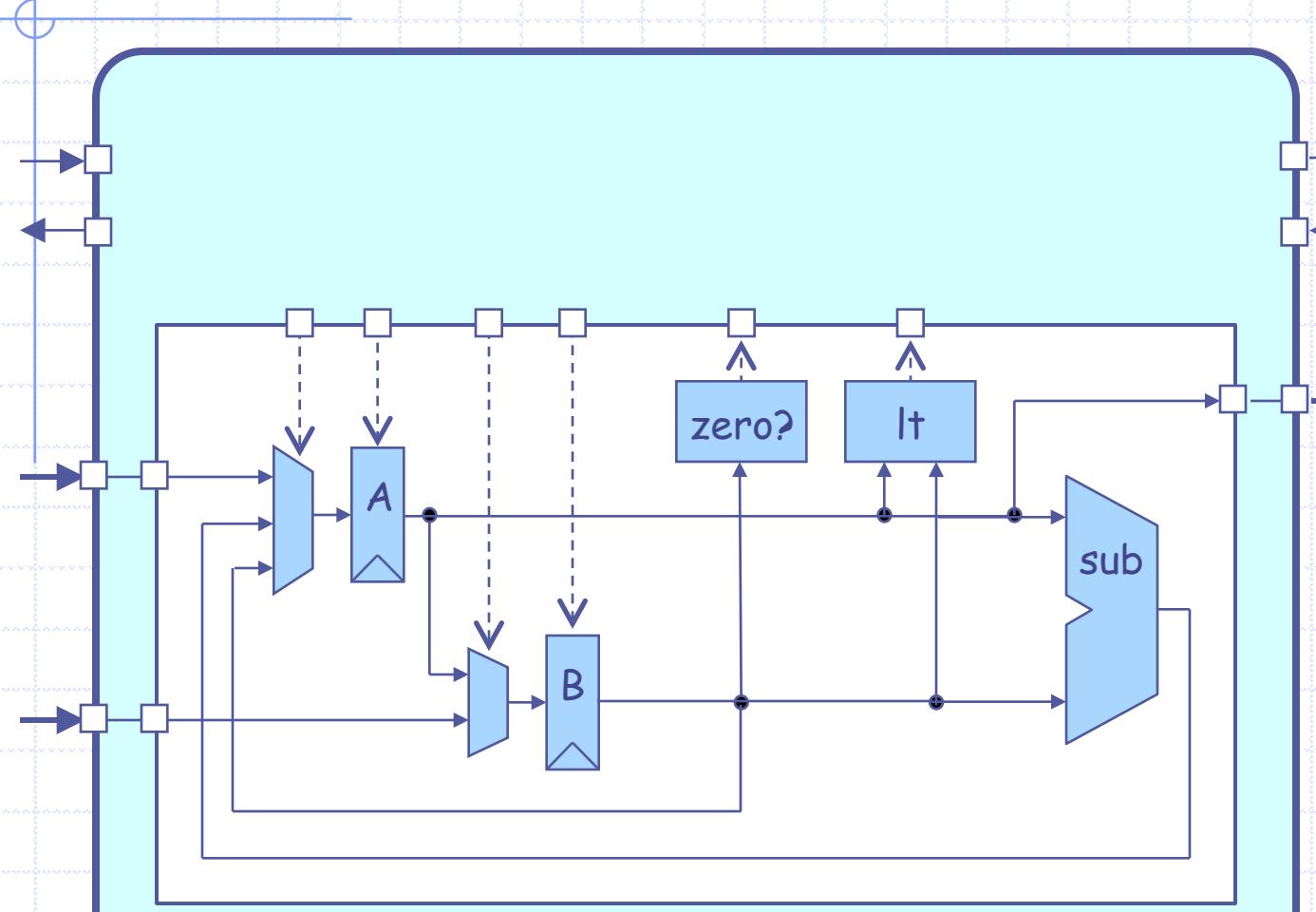Step 2: Design a datapath which has the functional units




```
A = inA; B = inB;  
while ( !done )  
begin  
if ( A < B )  
swap = A;  
A = B;  
B = swap;  
else if (B != 0)  
A = A - B;  
else  
done = 1;  
End  
Y = A;
```

Step 3: Add the control unit to sequence the datapath

Control unit
should be
designed to
be either busy
or waiting for
input or
waiting for
output to be
picked up
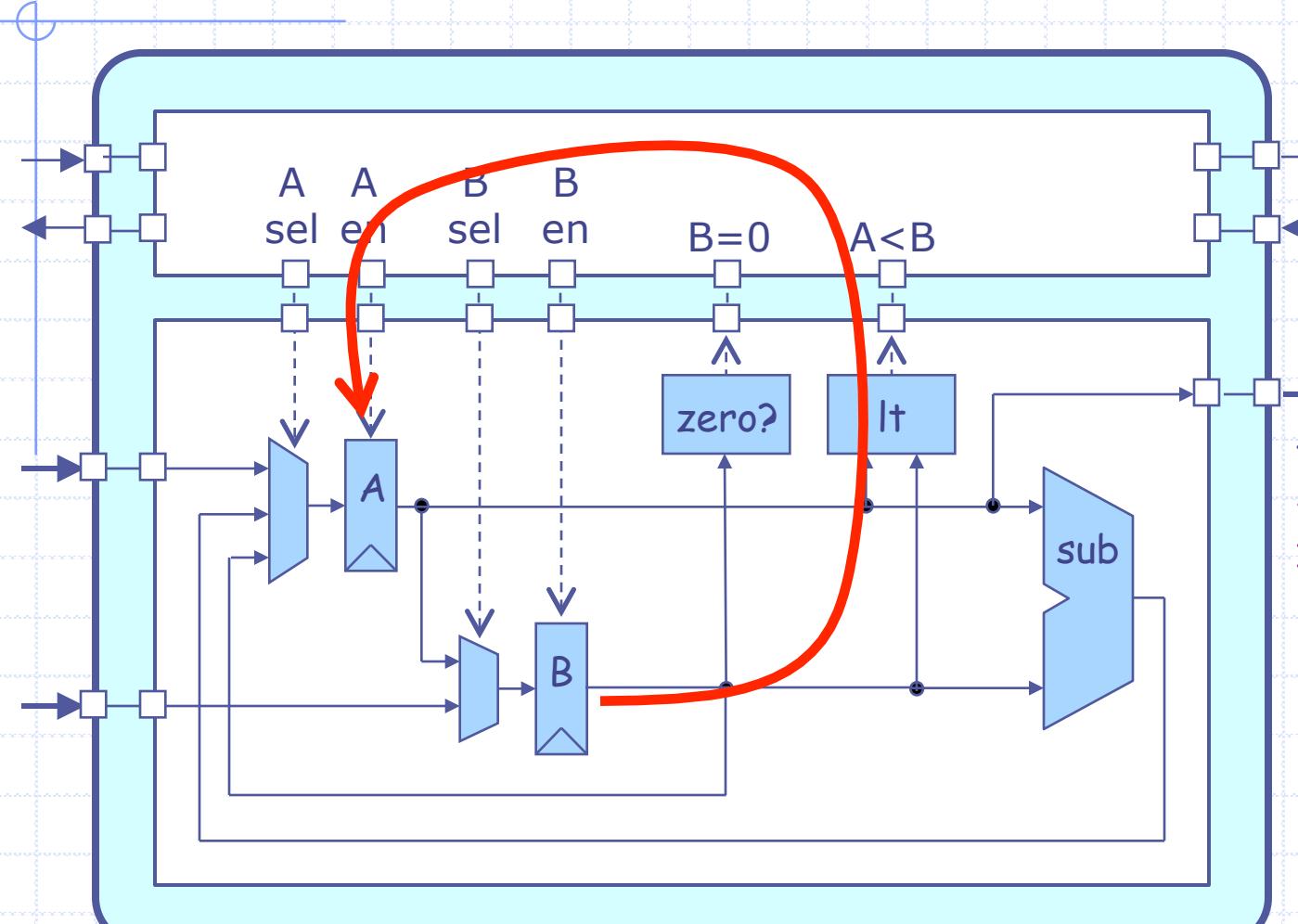
```
A = inA; B = inB;  
while ( !done )  
begin  
if ( A < B )  
swap = A;  
A = B;  
B = swap;  
else if (B != 0)  
A = A - B;  
else  
done = 1;  
End  
Y = A;
```




Courtesy of Arvind

L03-18

Datapath module interface
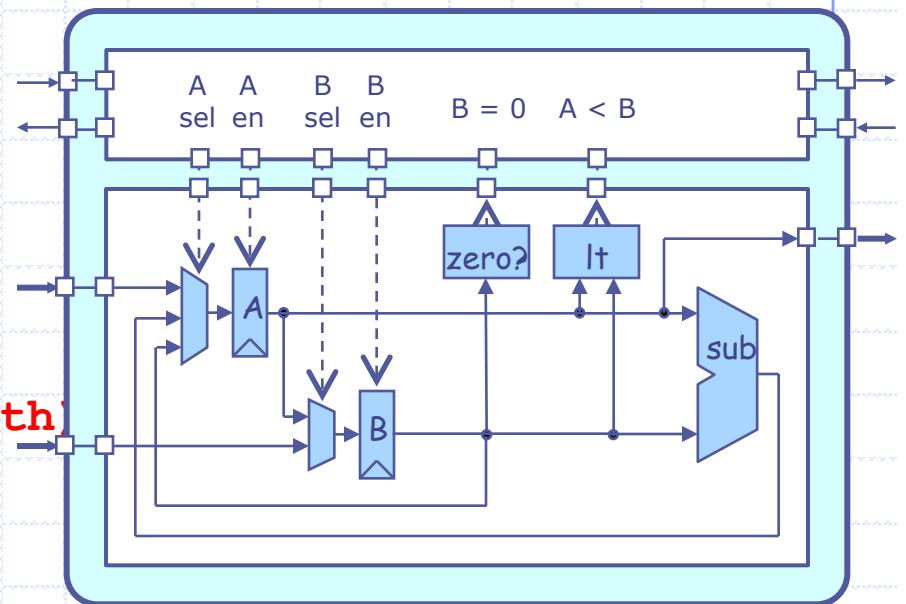
```
module GCDdatapath#( parameter W = 16 )
( input      clk,
  // Data signals
  input [W-1:0] operand_A,
  input [W-1:0] operand_B,
  output [W-1:0] result_data,
  // Control signals (ctrl->dpath)
  input      A_en,
  input      B_en,
  input [1:0]  A_sel,
  input      B_sel,
  // Control signals (dpath->ctrl)
  output     B_zero,
  output     A_lt_B
);
```




Courtesy of Arvind

L03-19

Connect the modules
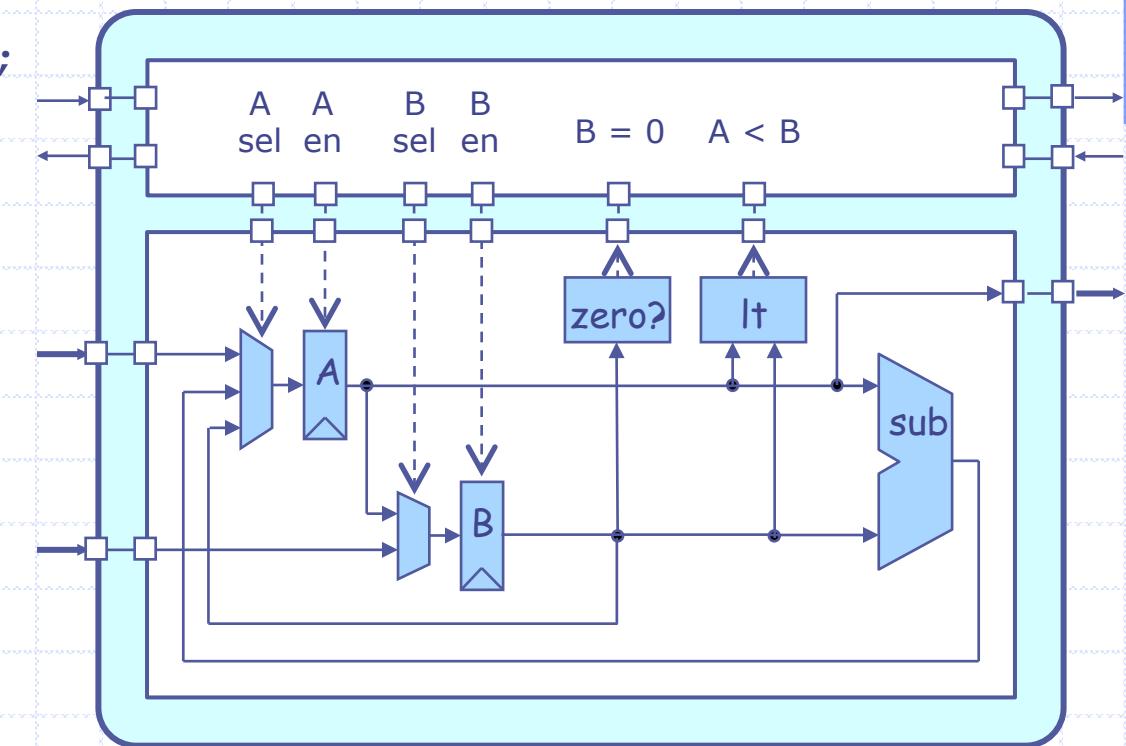
```
wire [W-1:0] B;  
wire [W-1:0] sub_out;  
wire [W-1:0] A_out;  
  
vcMux3#(W) A_mux  
( .in0 (operand_A),  
  .in1 (B),  
  .in2 (sub_out),  
  .sel (A_sel),  
  .out (A_out) );  
  
wire [W-1:0] A;
```



Connect the datapath modules ...

```
wire [W-1:0] B;  
wire [W-1:0] sub_out;  
wire [W-1:0] A_out;  
  
vcMux3#(W) A_mux  
( .in0 (operand_A),  
  .in1 (B),  
  .in2 (sub_out),  
  .sel (A_sel),  
  .out (A_out) );  
  
wire [W-1:0] A;  
vcEDFF_pf#(W) A_pf  
( .clk (clk),  
  .en_p (A_en),  
  .d_p (A_out),  
  .q_np (A) );
```


```
wire [W-1:0] B_out;  
vcMux2#(W) B_mux  
( .in0 (operand_B),  
  .in1 (A),  
  .sel (B_sel),  
  .out (B_out) );  
  
vcEDFF_pf#(W) B_pf  
( .clk (clk),  
  .en_p (B_en),  
  .d_p (B_out),  
  .q_np (B) );
```

```
assign B_zero = (B==0);  
assign A_lt_B = (A < B);  
assign sub_out = A - B;  
assign result_data = A;
```

Use structural
verilog
for datapath
registers.

Not quite right:
Continuous assignment
combinational
logic is fine for
datapath operators BUT
wrap them in a verilog
module and
instantiate structurally!

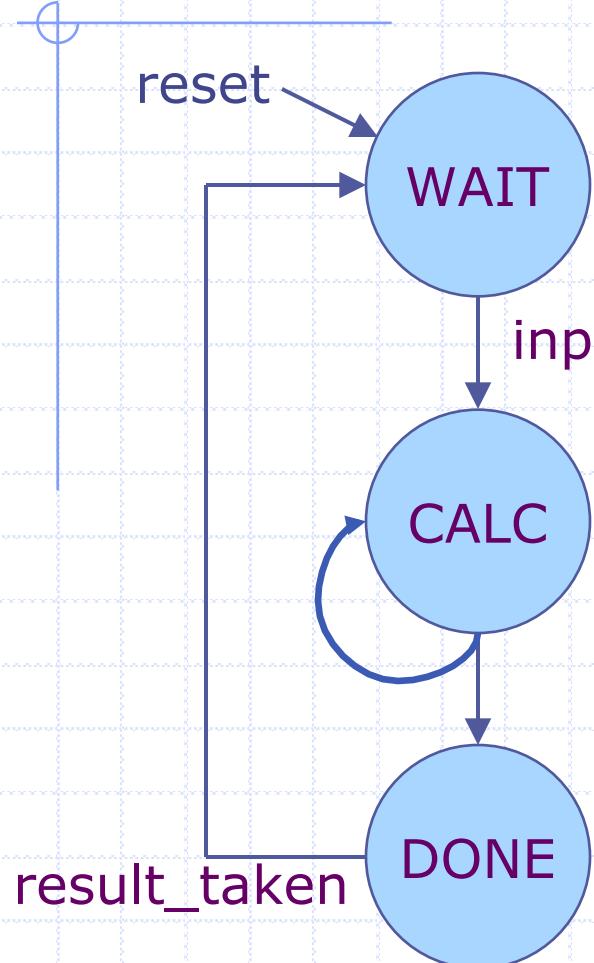Control unit requires a state machine for valid/ready signals



Implementing the control logic FSM in Verilog

```
localparam WAIT = 2'd0;
localparam CALC = 2'd1;
localparam DONE = 2'd2;

reg [1:0] state_next;
wire [1:0] state;

vcRDFF_pf#(2,WAIT)
state_pf
(.clk      (clk),
.reset_p  (reset),
.d_p      (state_next),
.q_np     (state));
```

Localparams are not really parameters at all. They are scoped constants.

Not quite right:
For registers in control logic, use RTL: e.g.

```
always @ (posedge clk)
if (reset)
    state <= WAIT;
else
    state <= state_next;
```

Output signals for control logic

```
reg [6:0] cs;
always @(*)
begin
    //Default control signals
    A_sel = A_SEL_X;
    A_en = 1'b0;
    B_sel = B_SEL_X;
    B_en = 1'b0;
    input_available = 1'b0;
    result_rdy = 1'b0;
    case ( state )
        WAIT :
            ...
        CALC :
            ...
        DONE :
            ...
    endcase
end
```

WAIT: begin

```
A_sel = A_SEL_IN;
A_en = 1'b1;
B_sel = B_SEL_IN;
B_en = 1'b1;
input_available = 1'b1;
```

end

CALC: if (A_lt_B)


```
A_sel = A_SEL_B;
A_en = 1'b1;
B_sel = B_SEL_A;
B_en = 1'b1;
```

else if (!B_zero)

```
A_sel = A_SEL_SUB;
A_en = 1'b1;
```

end

DONE: result_rdy = 1'b1;

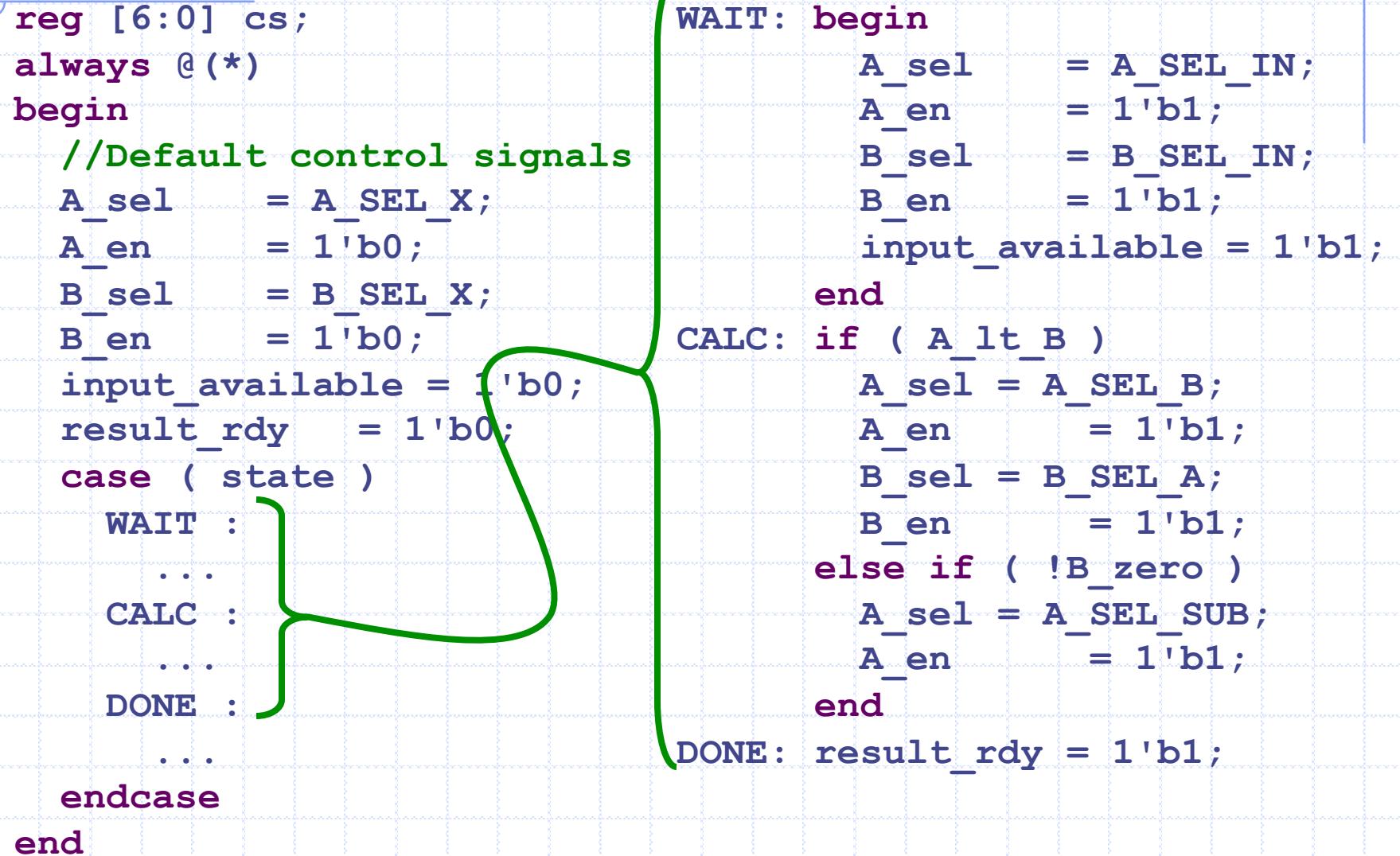


Next-state logic for Control Logic


```
always @(*)
begin
    // Default is to stay in
    // the same state
    state_next = state;

    case ( state )
        WAIT :
            if ( input_available )
                state_next = CALC;
        CALC :
            if ( B_zero )
                state_next = DONE;
        DONE :
            if ( result_taken )
                state_next = WAIT;
    endcase
end
```

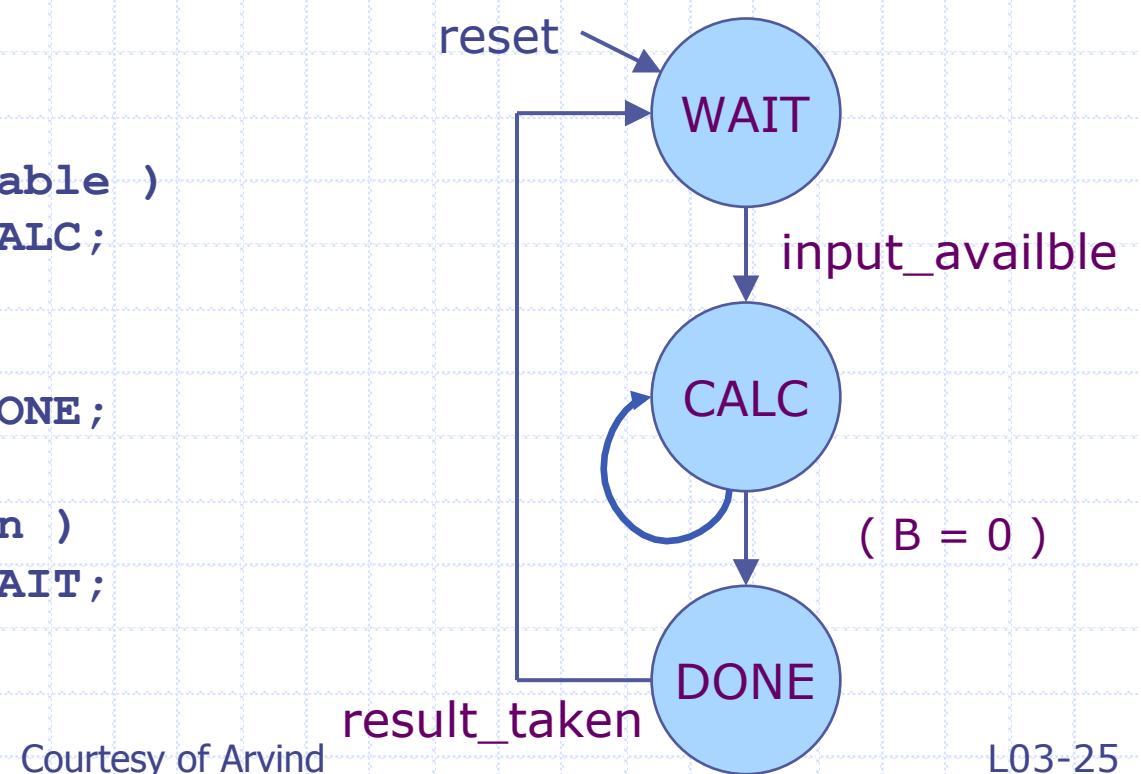
```
reg [1:0] state;
always @ (posedge clk)
    if (reset)
        state <= WAIT;
    else
        state <= state_next;
```



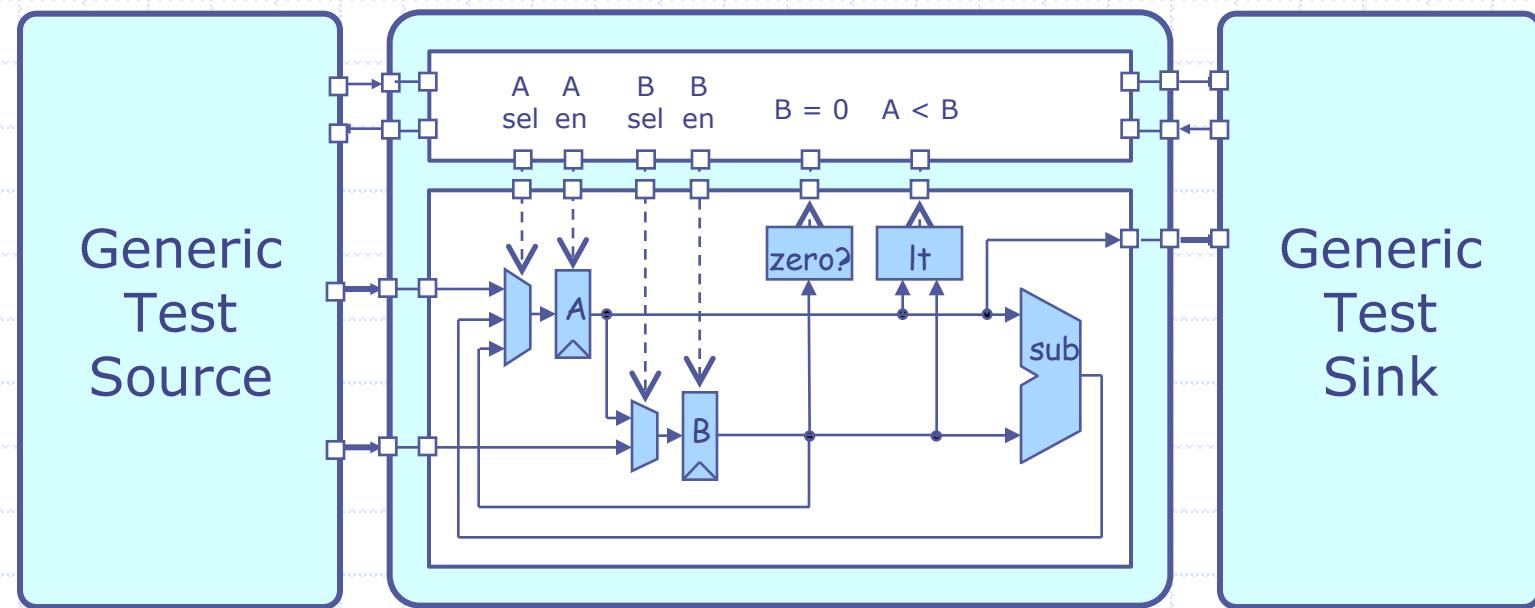RTL test harness requires proper handling of the ready/valid signals




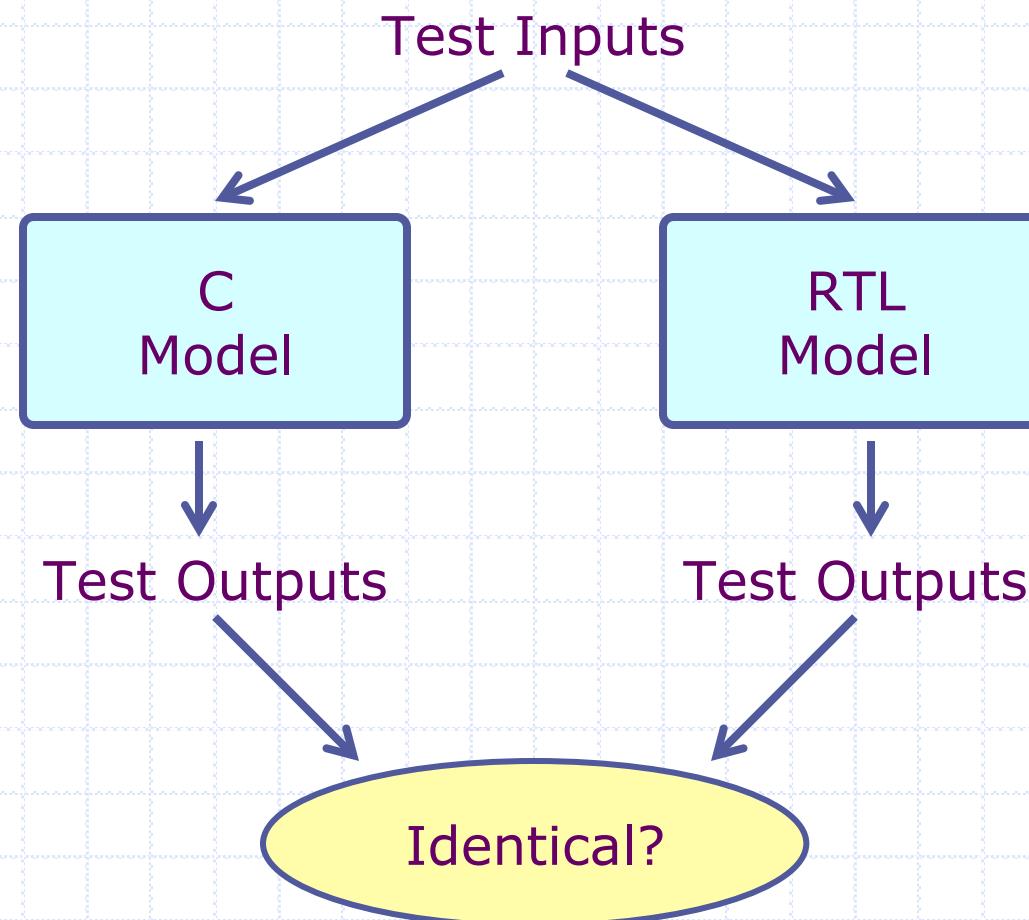Correctness: Compare behavioral and RTL implementations



Verilog Design Examples

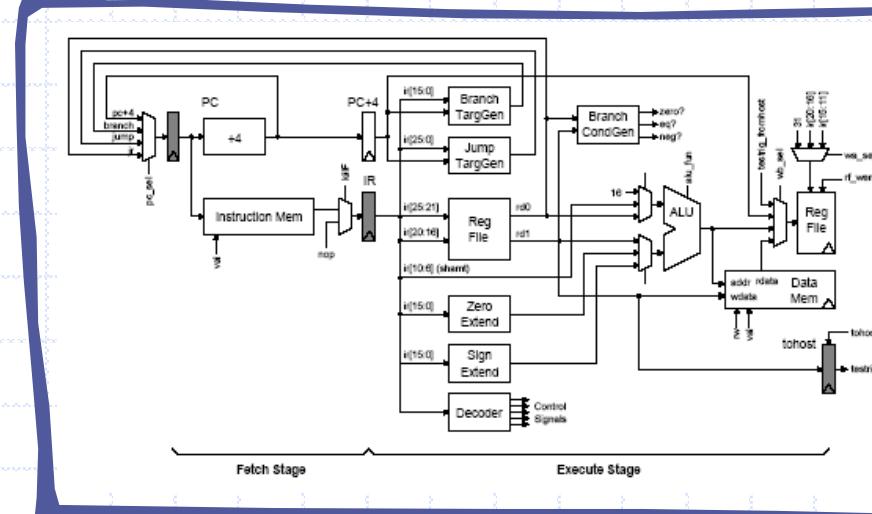- ◆ Greatest Common Divisor
- ◆ Unpipelined SMIPSv1 processor



Courtesy of Arvind

L03-28

SMIPS is a simple MIPS ISA which includes three variants

◆ SMIPSV1

- 5 instructions
- Lecture examples

31	24	25	21	20	16	15	11	10	6	5	0
opcode	rs		rt		rd	shamt		funct			R-type
opcode	rs		rt					immediate			I-type
opcode								target			J-type
Load and Store Instructions											
100011	base		dest				signed offset				LW rt, offset(rs)
101011	base		dest				signed offset				SW rt, offset(rs)
I-Type Computational Instructions											
001001	src		dest				signed immediate				ADDIU rt, rs, signed-imm.
001010	src		dest				signed immediate				SLTI rt, rs, signed-imm.
001011	src		dest				signed immediate				SLTIU rt, rs, signed-imm.
001100	src		dest				zero-ext. immediate				ANDI rt, rs, zero-ext-imm.
001101	src		dest				zero-ext. immediate				ORI rt, rs, zero-ext-imm.
001110	src		dest				zero-ext. immediate				XORI rt, rs, zero-ext-imm.
001111	00000		dest				zero-ext. immediate				LUI rt, zero-ext-imm.
R-Type Computational Instructions											
000000	00000	src		dest	shamt	000000					SLL rd, rt, shamt
000000	00000	src		dest	shamt	000010					SRL rd, rt, shamt
000000	00000	src		dest	shamt	000011					SRA rd, rt, shamt
000000	rshamt	src		dest	00000	000100					SLLV rd, rt, rs
				dest	00000	000110					SRLV rd, rt, rs
						000111					SRAV rd, rt, rs

SMIPSv1 ISA

Instruction	Semantics	Hardware Requirements
addiu rt, rs, imm	$R[rt] := R[rs] + \text{sext}(\text{imm})$	Needs adder, sext, 1w1r rf port
bne rs, rt, offset	if ($R[rs] \neq R[rt]$) pc := pc + sext(offset) + 4	Needs adder, sext, comparator, 2r rf port
lw rt, offset(rs)	$R[rt] := M[R[rs]] + \text{sext}(\text{offset})$	Needs adder, sext, memory read port, 1r1w rf port
sw rt, offset(rs)	$M[R[rs]] + \text{sext}(\text{offset}) = R[rt]$	Needs adder, sext, memory write port, 1r1w port

First step: Design a port interface

smipsTestHarness

testrig_tohost
testrig_fromhost

smipsProc

imemreq_bits_addr

imemreq_val

imemresp_bits_data

dmemreq_bits_rw

dmemreq_bits_addr

dmemreq_bits_data

dmemreq_val

dmemresp_bits_data

Magic
Dual Port
Memory


clk

reset

clk


reset

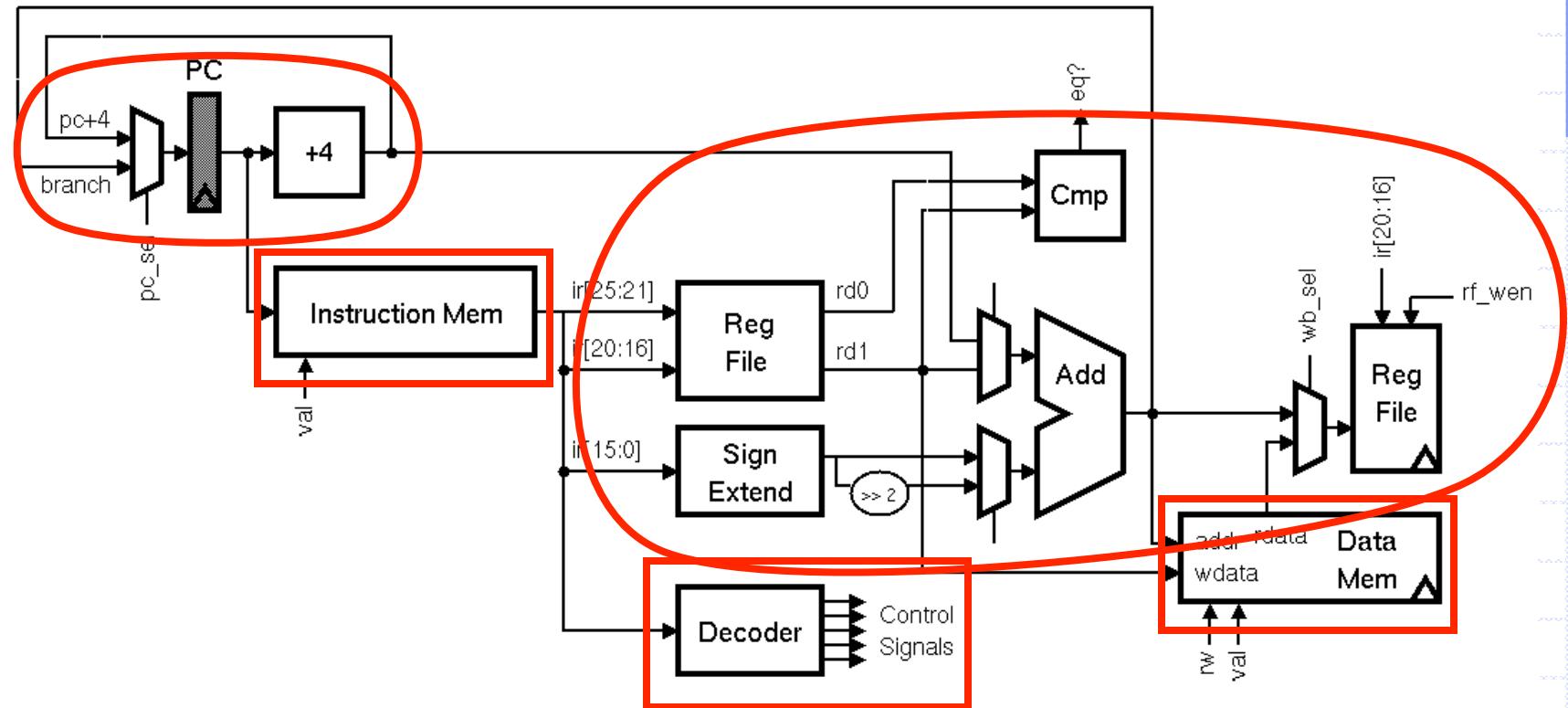Identify memories, datapaths, and random logic



Step 1: Identify the memories
Step 2: Identify the datapaths
Step 3: Everything else is random logic

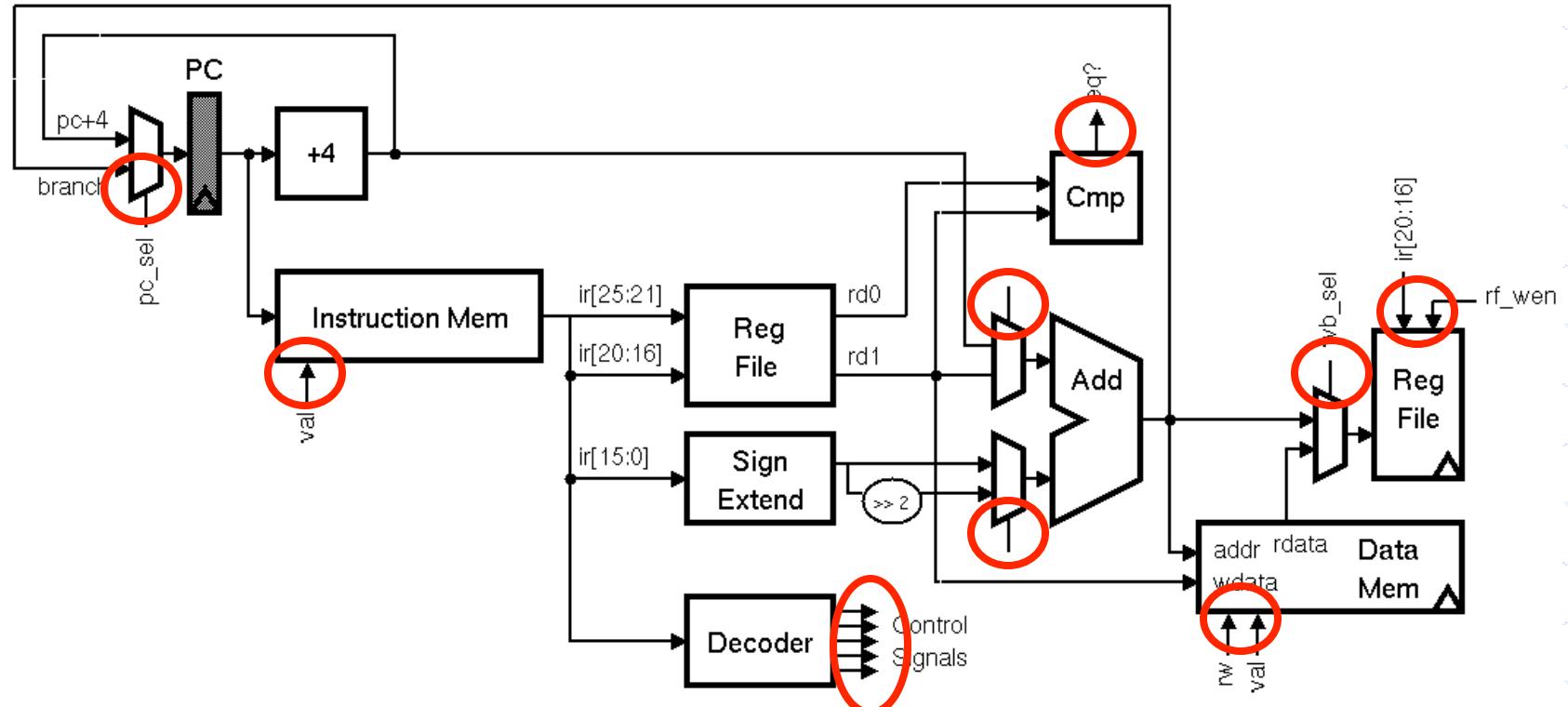Identify the signals to interface with the controller



SMIPSV1 datapath

```
module smipsProcDpath_pstr
( input clk, reset,
// Memory ports
output [31:0] imemreq_addr,
output [31:0] dmemreq_addr,
output [31:0] dmemreq_data,
input [31:0] dmemresp_data,
// Controls signals (ctrl->dpath)
input pc_sel,
input [ 4:0] rf_raddr0,
input [ 4:0] rf_raddr1,
input rf_wen,
input [ 4:0] rf_waddr,
input op0_sel,
input op1_sel,
input [15:0] inst_imm,
input wb_sel,
// Control signals (dpath->ctrl)
output branch_cond_eq,
output [7:0] tohost_next );
wire [31:0] branch_targ;
wire [31:0] pc_plus4;
wire [31:0] pc_out;
vcMux2#(32) pc_mux
( .in0 (pc_plus4),
.in1 (branch_targ),
.sel (pc_sel),
.out (pc_out) );
wire [31:0] pc;
vCRDFF_pf#(32,32'h0001000) pc_pf
( .clk (clk),
.reset_p (reset),
.d_p (pc_out),
.q_np (pc) );
assign imemreq_addr = pc;
vcInc#(32,32'd4) pc_inc4
( .in (pc),
.out (pc_plus4) );
```

Register file with 2 combinational read ports and 1 write port

```
module smipsProcDpathRegfile
( input          clk,
  input [ 4:0] raddr0, // Read 0 address (combinational input)
  output [31:0] rdata0, // Read 0 data (combinational on raddr)
  input [ 4:0] raddr1, // Read 1 address (combinational input)
  output [31:0] rdata1, // Read 1 data (combinational on raddr)
  input          wen_p, // Write enable (sample on rising clk edge)
  input [ 4:0] waddr_p, // Write address (sample on rising clk edge)
  input [31:0] wdata_p // Write data (sample on rising clk edge));

  // We use an array of 32 bit register for the regfile itself
  reg [31:0] registers[31:0];

  // Combinational read ports
  assign rdata0 = ( raddr0 == 0 ) ? 32'b0 : registers[raddr0];
  assign rdata1 = ( raddr1 == 0 ) ? 32'b0 : registers[raddr1];

  // Write port is active only when wen is asserted
  always @(posedge clk)
    if ( wen_p && (waddr_p != 5'b0) )
      registers[waddr_p] <= wdata_p;
endmodule
```

Verilog for SMIPSV1 control logic

```
`define LW    32'b100011?????-?????-?????-?????-?????-?????  
`define SW    32'b101011?????-?????-?????-?????-?????-?????  
`define ADDIU 32'b0011001?????-?????-?????-?????-?????-?????  
`define BNE   32'b000101?????-?????-?????-?????-?????-?????  
  
localparam cs_sz = 8;  
reg [cs_sz-1:0] cs;  
  
always @(*)  
begin  
    cs = {cs_sz{1'b0}};  
    casez ( imemresp_data )  
        // op0 mux op1 mux wb mux rfile mreq mreq tohost  
        // br type sel sel sel wen r/w val en  
        `ADDIU: cs ={br_pc4, op0_sx, op1_pc4, wmx_alu, 1'b1, mreq_x, 1'b0, 1'b0};  
        `BNE : cs ={br_neq, op0_sx2, op1_pc4, wmx_x, 1'b0, mreq_x, 1'b0, 1'b0};  
        `LW  : cs ={br_pc4, op0_sx, op1_rd0, wmx_mem, 1'b1, mreq_r, 1'b1, 1'b0};  
        `SW  : cs ={br_pc4, op0_sx, op1_rd0, wmx_x, 1'b0, mreq_w, 1'b1, 1'b0};  
        `MTC0: cs ={br_pc4, op0_x, op1_x, wmx_x, 1'b0, mreq_x, 1'b0, 1'b1};  
    endcase  
end
```

Verilog for SMIPSV1 control logic

```
// Set the control signals based on the decoder output
wire br_type = cs[7];
assign pc_sel = ( br_type == br_pc4 ) ? 1'b0
                                         : ( br_type == br_neq ) ? ~branch_cond_eq
                                         :
                                         1'bx;
assign op0_sel = cs[6];
assign op1_sel = cs[5];
assign wb_sel = cs[4];
assign rf_wen = ( reset ? 1'b0 : cs[3] );
assign dmemreq_rw = cs[2];
assign dmemreq_val = ( reset ? 1'b0 : cs[1] );
wire tohost_en = ( reset ? 1'b0 : cs[0] );
// These control signals we can set directly from the
instruction bits
assign rf_raddr0 = inst[25:21];
assign rf_raddr1 = inst[20:16];
assign rf_waddr = inst[20:16];
assign inst_imm = inst[15:0];
// We are always making an imemreq
assign imemreq_val = 1'b1;
```

Take away points

- ◆ Follow the simple guidelines to write synthesizable Verilog
- ◆ Parameterized models provide the foundation for reusable libraries of components
- ◆ Use explicit state to prevent unwanted state inference and to more directly represent the desired hardware
- ◆ Begin your RTL design by identifying the external interface and then move on to partition your design into the **memories, datapaths, and control logic**

Behavioral Verilog: For TestBenchs Only

- ◆ Characterized by heavy use of sequential blocking statements in large always blocks
- ◆ Many constructs are **not synthesizable** but can be useful for behavioral modeling and test benches
 - Data dependent for and while loops
 - Additional behavioral datatypes: **integer**, **real**
 - Magic initialization blocks: **initial**
 - Magic delay statements: **#<delay>**
 - ◆ Except for clk generation, use @ (negedge clk);
 - System calls: **\$display**, **\$assert**, **\$finish**

System calls for test harnesses and simulation

```
reg [ 1023:0 ] exe_filename;  
initial  
begin  
    // This turns on VCD (plus) output  
    $vcplusplus(0);  
    // This gets the program to load into memory from the  
    // command line  
    if ( $value$plusargs( "exe=%s", exe_filename ) )  
        $readmemh( exe_filename, mem.m );  
    else  
        begin  
            $display( "ERROR: No executable specified!  
                      (use +exe=<filename>)" );  
            $finish;  
        end  
    // Stobe reset  
    #0 reset = 1;  
    #38 reset = 0;  
end
```

Some dangers in writing behavioral models

```
module GCDTestHarness_behav;
    reg [15:0] inA, inB;
    wire [15:0] out;

    GCD_behav#(16) gcd_unit(.inA(inA), .inB(inB), .out(out));

initial
begin
    // 3 = GCD( 27, 15 )
    inA = 27; inB = 15;
    #10; ← without some delay
    if (out == 3)
        $display("Test gcd(27,15) succeeded, [%x==%x]", out, 3);
    else
        $display("Test gcd(27,15) failed, [%x != %x]", out, 3);
    $finish;
end
endmodule
```

out is bogus