
Chapter 2: Basic Ladder Logic Programming

Ladder Logic

Learning objectives

- **Understand basic ladder logic symbol**
- **Write ladder logic for simple applications**
- **Translate relay ladder logic into PLC ladder logic**

Simple Ladder Logic

Ladder Logic:

- **Primary Programming Language for PLCs.**
- **Visual and Graphical** language unlike **textual** high-level, such as C, C++, Java...
- **Derived from relay logic diagrams**
- **Primitive Logic Operations:**
 - **OR**
 - **AND**
 - **NOT**

Simple Ladder Logic

OR Operation

- **Control Behavior:** The light should be on when either switch A is on (i.e., closed) or switch B is on (closed). Otherwise it should be off
- Task: Implement this behavior using
 - Relay circuit
 - PLC Ladder Logic

Simple Ladder Logic


OR Operation

OR Truth Table

- Possible Combinations of the 2 Switches: (2^2)

A	B	Light
OFF	OFF	OFF
OFF	ON	ON
ON	OFF	ON
ON	ON	ON

OR Operation Relay Circuit

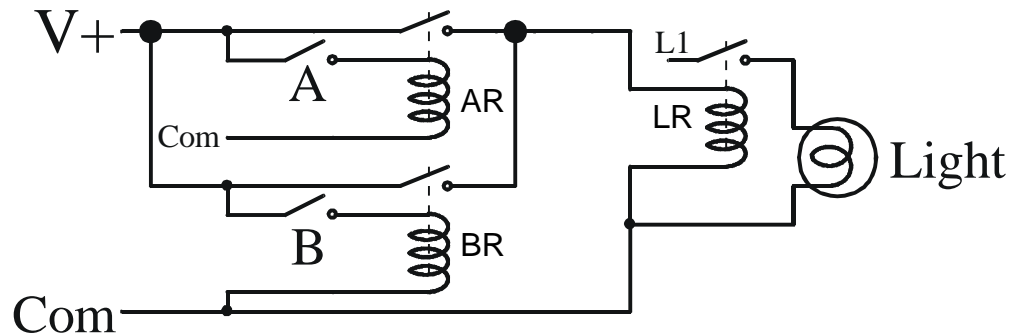


- Switches A and B are connected **in parallel** to relay coils AR & BR resp.
- When switch A (or switch B) is closed relay coil AR (or BR) gets energized
 - The *Normally Open (NO)* contact AR (or BR) gets closed
 - Power is transmitted to coil LR
 - Relay coil LR gets energized
 - The *NO* contact LR gets closed
 - **Power is transmitted to the Light bulb**

A typical coil can have up to 12 contacts


OR Operation

Relay Ladder Logic Circuit

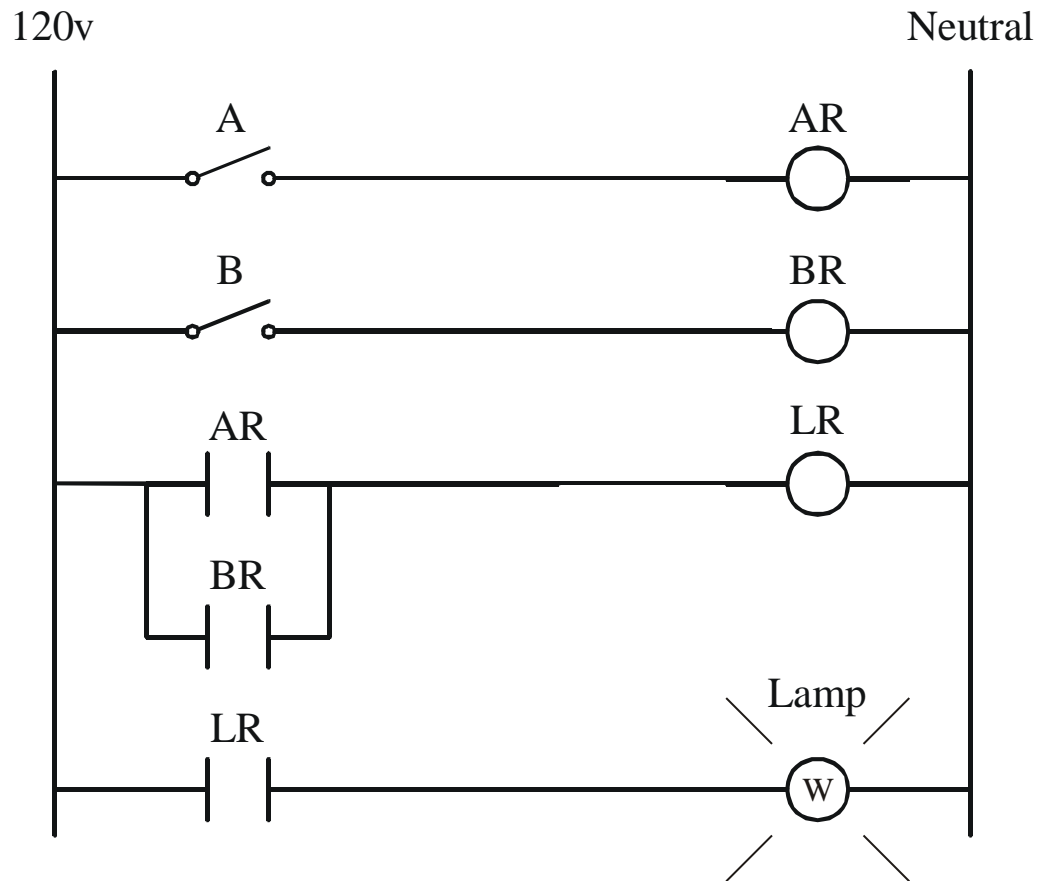

OR Operation

PLC Ladder Logic

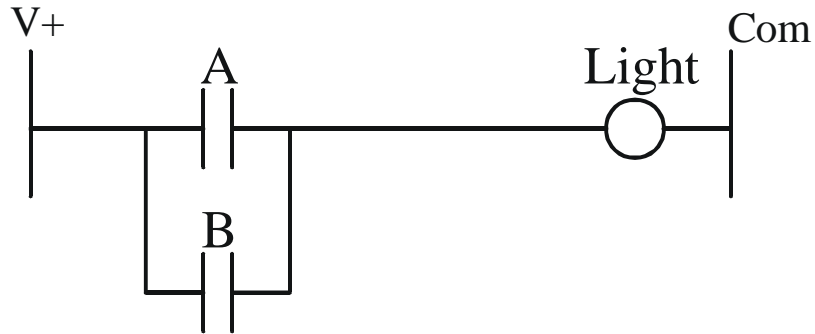

- Append above to the leading two rungs of relay ladder logic diagram
- Switch A and Switch B are connected to discrete input channels of the PLC
- Light is connected to discrete output channel (actuator) of the PLC

When input switch A (or switch B) is on
the light is on

Simple Ladder Logic

AND Operation

- **Control Behavior:** The light should be on when switch A is on (i.e., closed) and switch B is on (closed). Otherwise it should be off
- Task: Implement this behavior using
 - Relay circuit
 - PLC Ladder Logic

Simple Ladder Logic

AND Operation


- Possible Combinations of the 2 Switches: (2^2)

AND Truth Table

A	B	Light
OFF	OFF	OFF
OFF	ON	OFF
ON	OFF	OFF
ON	ON	ON

AND Operation

Relay Circuit

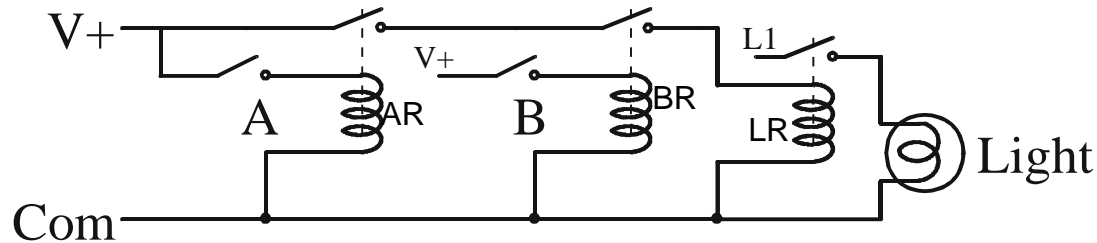


- Switches A and B are connected in **series** to relay coils AR & BR resp.
- When switch A is closed relay coil AR gets energized
 - The *Normally Open (NO)* contact AR gets closed
 - Power flows to *Normally Open (NO)* contact BR, where it terminates until BR is energized
 - Subsequently, when BR gets energized, LR is energized, which causes the *NO* contact LR to close
 - **Power is transmitted to the Light bulb**

What happens if BR is energized before AR?

AND Operation

PLC Ladder Logic Circuit

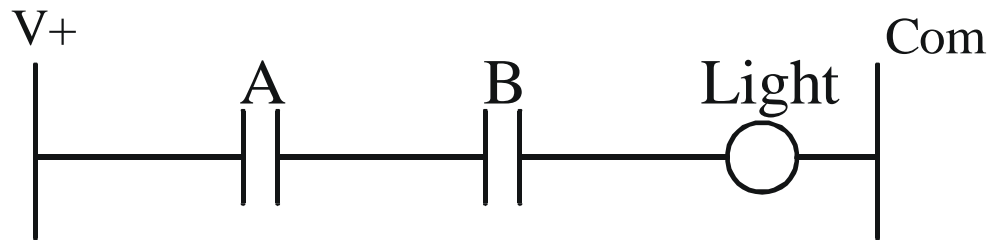

Simple Ladder Logic

NOT Operation

- **Control Behavior:** The light comes on only when switch A is on (i.e., closed) and switch B is off (open). Otherwise it should be off
- Task: Implement this behavior using
 - Relay circuit
 - PLC Ladder Logic

Simple Ladder Logic

NOT Operation


- Possible Combinations of the 2 Switches: (2^2)

NOT Truth Table

A	B	Light
OFF	OFF	OFF
OFF	ON	OFF
ON	OFF	ON
ON	ON	OFF

NOT Operation


Relay Circuit

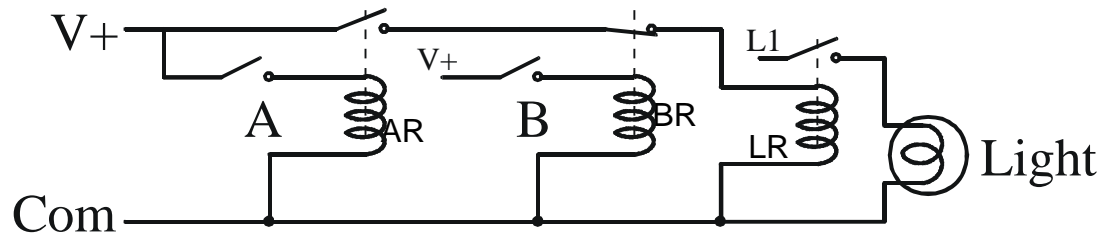

- Switches A and B are connected to relay coils AR & BR resp.
- When switch A is closed relay coil AR gets energized
- When switch B is off (on) relay coil BR is not energized (energized) and BR contact is normally-closed (normally-open)
-

NOT Operation

PLC Ladder Logic

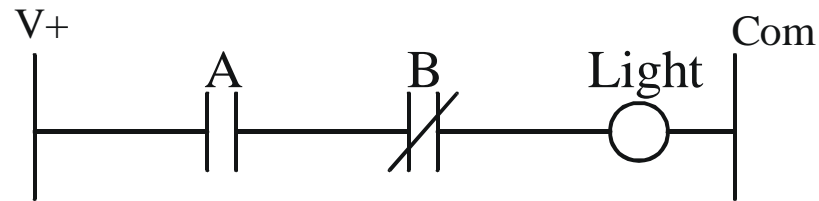

Simple Ladder Logic

NAND Operation

NAND (NOT AND)

- **Control Behavior:** The light comes on only when switch A is off and switch B is off. Otherwise it should be off
- **Task:** Implement this behavior using
 - Relay circuit
 - PLC Ladder Logic

Simple Ladder Logic


NAND Operation

- Possible Combinations of the 2 Switches: (2^2)

NAND Truth Table


A	B	Light
OFF	OFF	ON
OFF	ON	ON
ON	OFF	ON
ON	ON	OFF

NAND Operation Relay Circuit

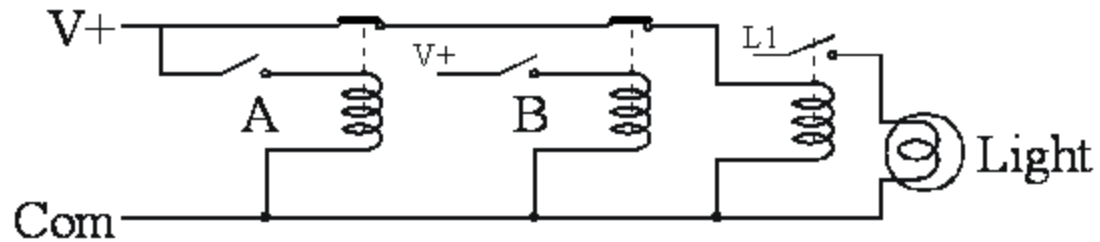

NAND Operation


Ladder Logic Circuit

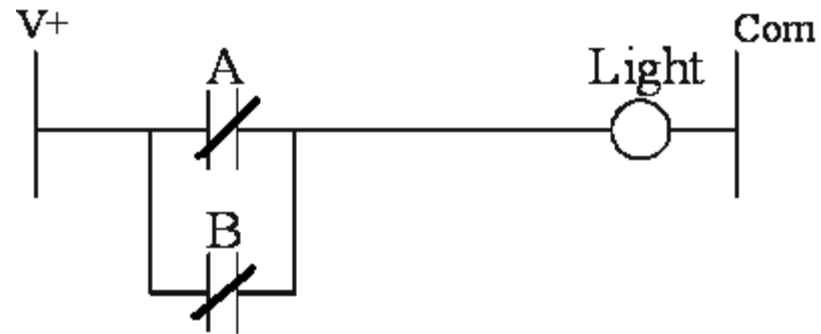

Digital Logic


Gates

AND

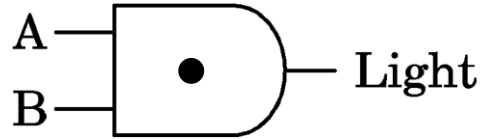


$$A \bullet B$$

OR

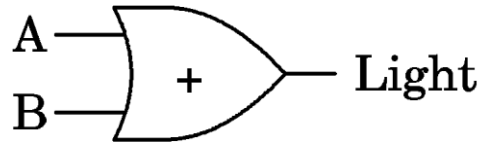


$$A + B$$

NAND

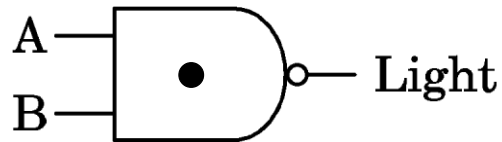


$$\overline{A \bullet B}$$

NOR

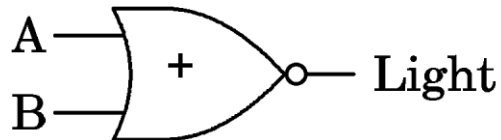


$$\overline{A + B}$$

NOT

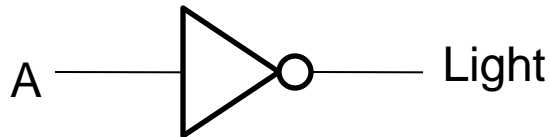

$$\overline{A}$$

Basic Ladder Logic Symbol

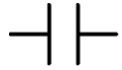


Normally open contact

Passes power (ON) if coil driving the contact is ON (closed)
Allen-Bradley calls it **XIC** - eXamine If Closed




Normally closed contact

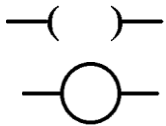Passes power (ON) if coil driving the contact is **off** (open)
Allen-Bradley calls it **XIO** - eXamine If Open



Output or coil

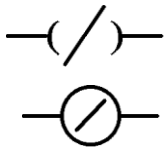If any left-to-right path of inputs passes power, output is energized
Allen-Bradley calls it OTE - OuTput Energize



Not Output or coil


If any left-to-right path of inputs passes power, output is de-energized


The IEC 61131-3 standards describe the complete list of ladder logic **contact** and **coil** symbols. **See also section 2.3.1**

PLC Ladder Logic

Symbols

- The symbols are ladder logic instructions
- The PLC scans (executes) the symbols:

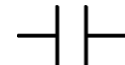
 = on = Closed = True = 1

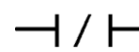 = off = Open = False = 0

- Every PLC manufacturer uses instruction symbols
- Industry trend is based on IEC 61131-3
 - Variations in symbols by Manufacturers
- Allen-Bradley ControlLogix symbols slightly different (Refer 2.3.3)

Ladder Logic Diagram

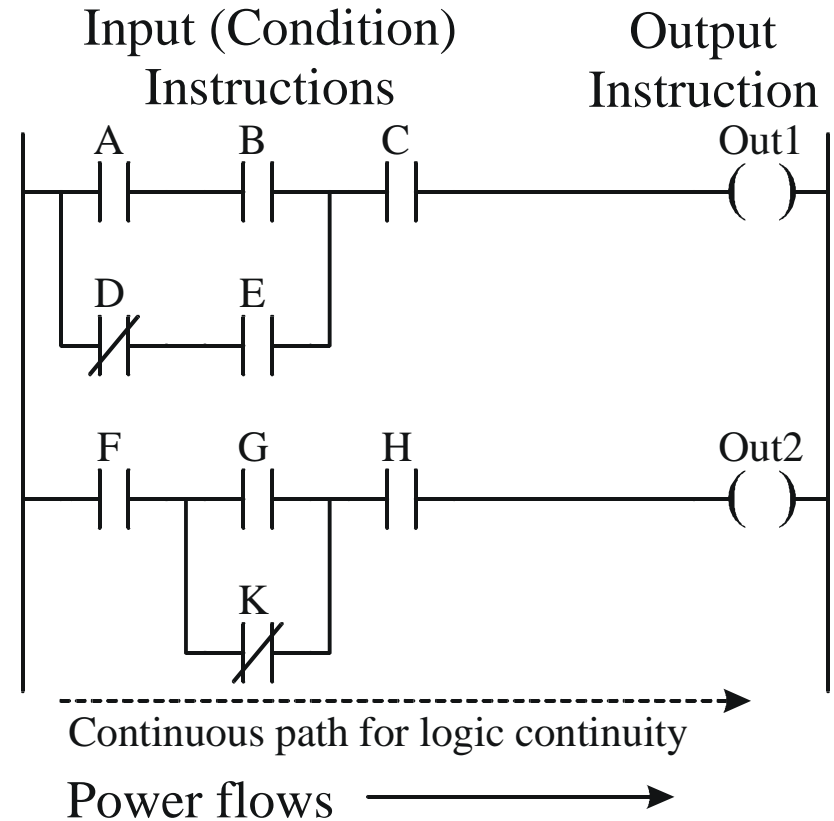- ❑ Power Rails - Pair of Vertical Lines
- ❑ Rungs - Horizontal Lines
- ❑ Contacts A, B, C, D... arranged on rungs
- ❑ Note in PLC Ladder Logic:
 - No Real Power Flow (like in relay ladder)
 - There must be continuous path thru' the contacts to energize the output




Ladder Logic Diagram Instructions

Two Classes of Ladder Logic Instructions

❑ **Output:** Appears on extreme RHS of rung always – Out1, Out2

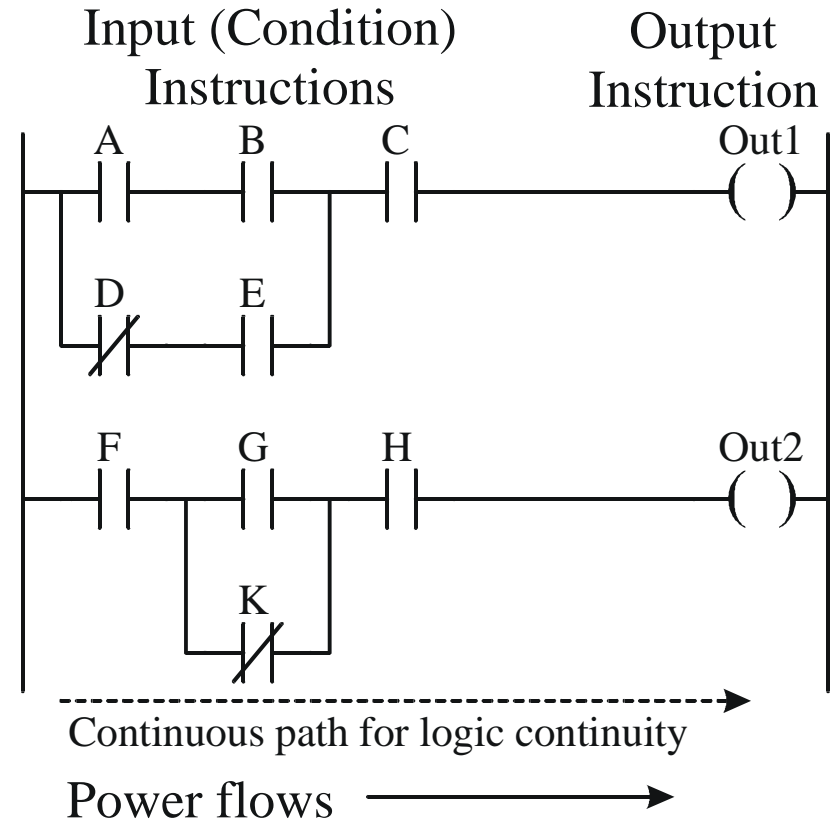❑ **Input:** Any instruction that can replace a contact




Can contacts appear on the RHS of a coil?

Ladder Logic Diagram

Function Block Instructions

Function Block Instructions

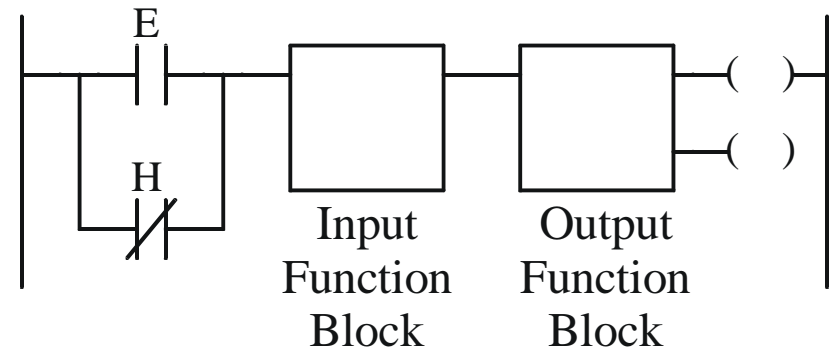- ❑ Any non-contact instruction:
 - Timer Instruction
 - Counter Instruction
 - Comparison Instruction



Ladder Logic Diagram

Example 1

Task:

Draw a ladder diagram that will cause the **output**, pilot light PL2, to be on when selector switch SS2 is **closed**, push button PB4 is **closed** and limit switch LS3 is **open**. (Note: no I/O addresses yet.)

Thought Process

- ❑ Identify the output: PL2 → PL2 appears on rhs of rung
- ❑ What is the behavior (type of connection to use):
sequential operation of all switches → series connection
- ❑ Type of contacts to implement output:


SS2 closed 

PB4 closed 

LS3 open 

Ladder Logic Diagram

Example 1

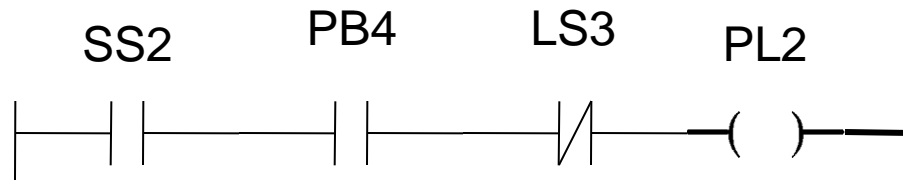


Ladder Logic Diagram

Example 2

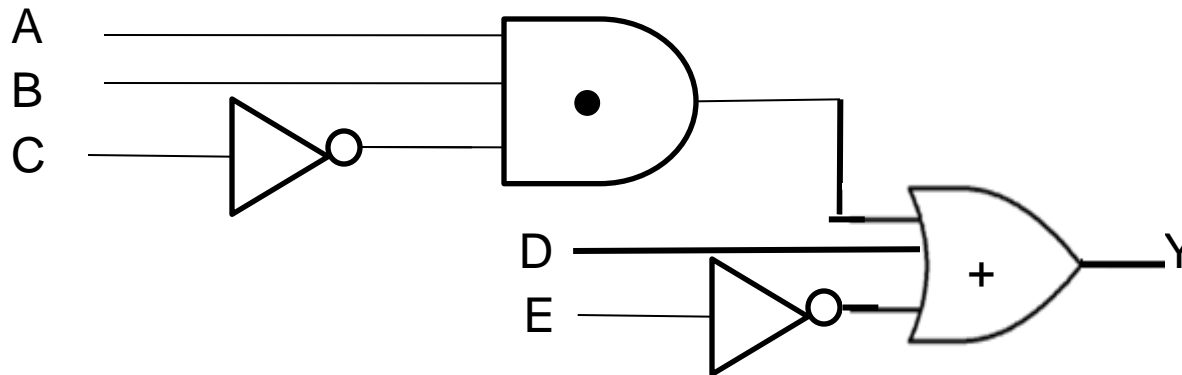Task:

Draw a ladder diagram that is equivalent to the following digital logic diagram



Y is on when (A is on, B is on and C is off) or D is on, or E is off

What is the Boolean logic expression?

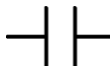
Ladder Logic Diagram

Example 2

■ Thought Process

- Identify the output: $Y \rightarrow$ Coil Y appears on rhs of rung
- What is the behavior (type of connection to use):
 - The inputs A, B, C for AND gate will be connected in series
 - The D, E inputs for OR gate will be connected in parallel with the output of AND gate
- Type of contacts to implement output (review the expected behavior again to determine contact types):

A is on: 

B is on: 


C is off: 

D is on: 

E is off: 

Ladder Logic Diagram


Example 2

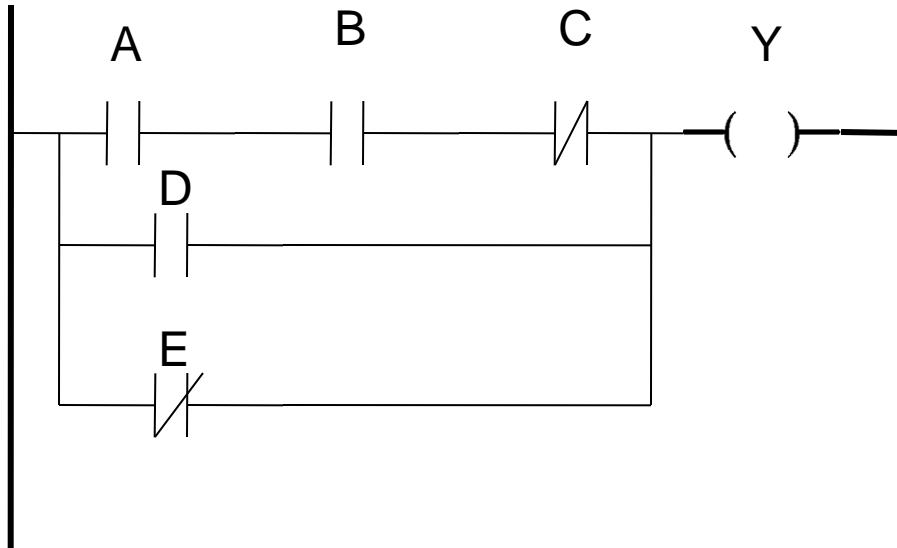

What happens if the D contact refers to Y?

Ladder Logic Diagram

Sealing an output

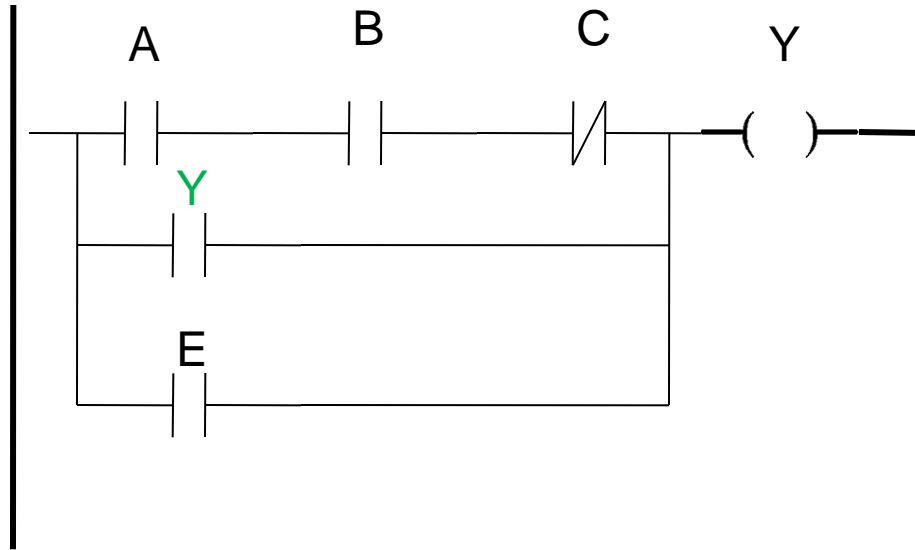


Output Y is set (latched) indefinitely

Ladder Logic Diagram Dangers

Repeated Output

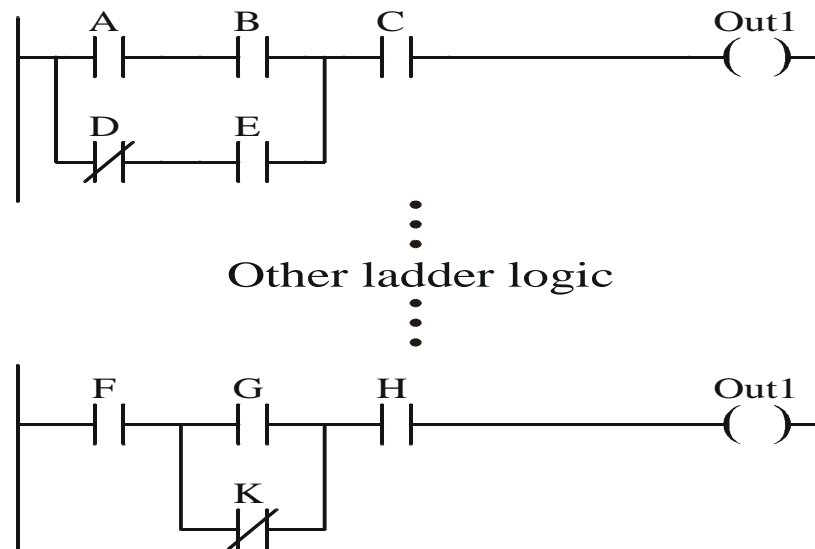- Do not repeat normal output coils that refer to the same address




- The coils for first and second rung refer to **Out1**
 - Second rung overrides the logic in first rung

Ladder Logic Diagram Dangers

Repeated Output - Correction

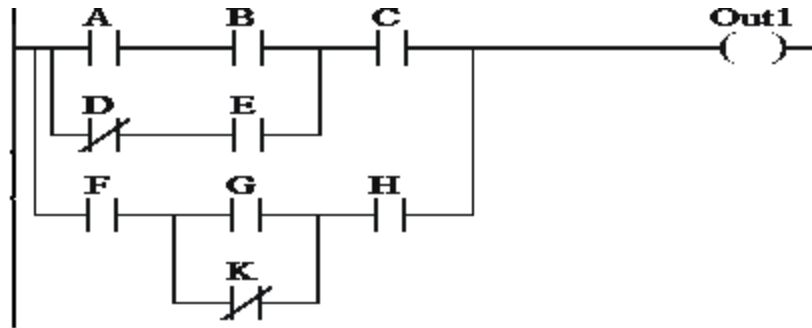- First consider the output
 - Next, consider ALL the conditions that drive the output (Out1) (Implement the conditions in parallel)




Ladder Logic Diagram Dangers

- Use set/seal (latch) and reset (unlatch) together:
 - If a set coil refers to an output there should be a reset coil for that output
 - Reverse power flow in contact matrix is not allowed
 - Power flow one way left to right (solid state relays)


Ladder Logic Diagram Dangers

Reverse Power Flow

- This is **not** allowed:

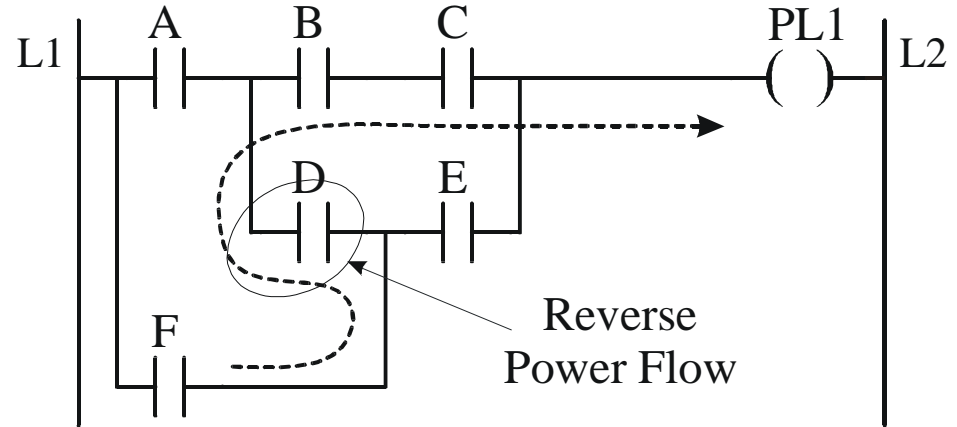


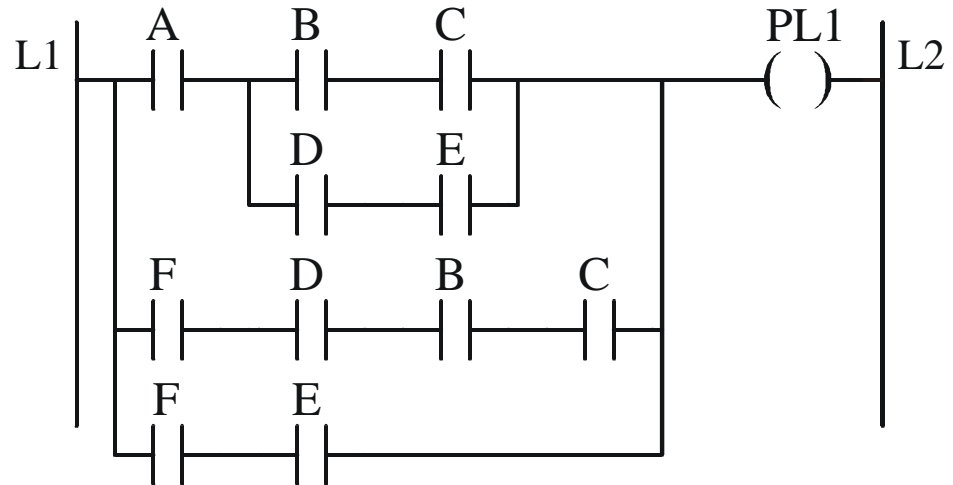- If the reverse power flow path is truly needed, then put it as a separate path, where the power flows from left to right:



Typical PLC Processor Scan

- Major tasks in a scan

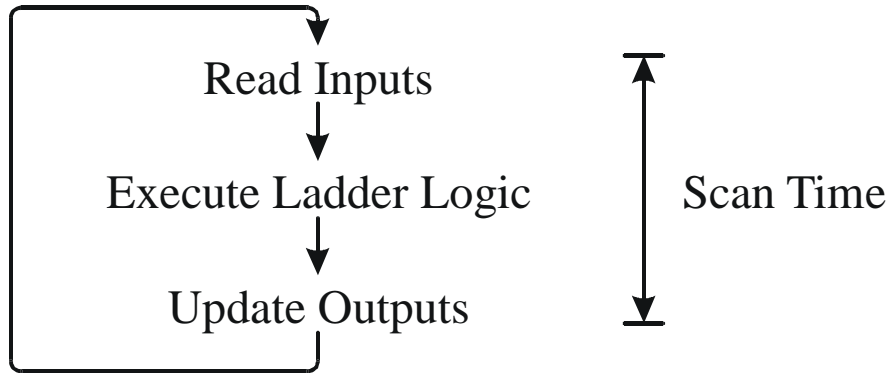


- Processor must read the state of the physical inputs and set the state of the Physical outputs

Typical PLC Processor Scan

■ Order of PLC Processor Scan

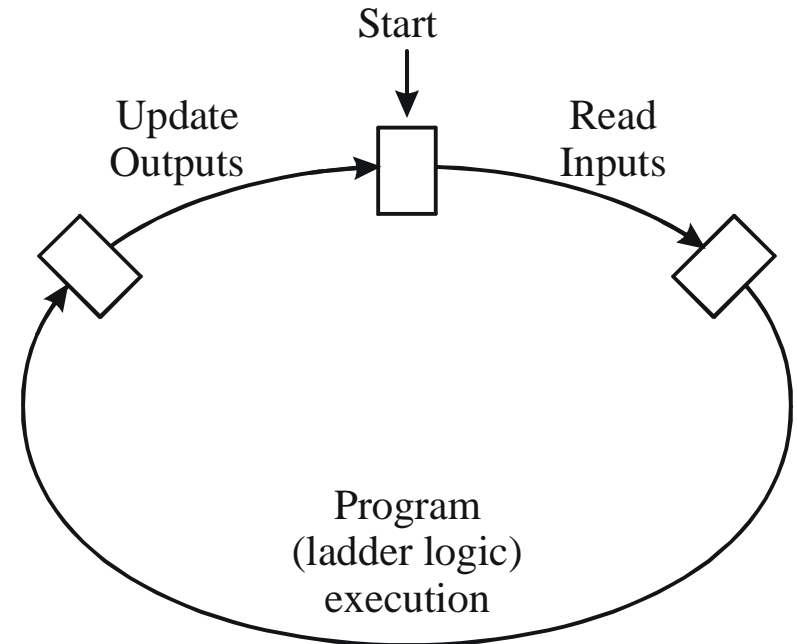- Read Physical Inputs
- Scan ladder logic program
- Write the physical outputs



■ Scan Time


- Time to complete above cycle
- Order of 1-200 milliseconds

What could happen if scan time exceeds more than 200 milliseconds?

Typical PLC Processor Scan

Scenario 2

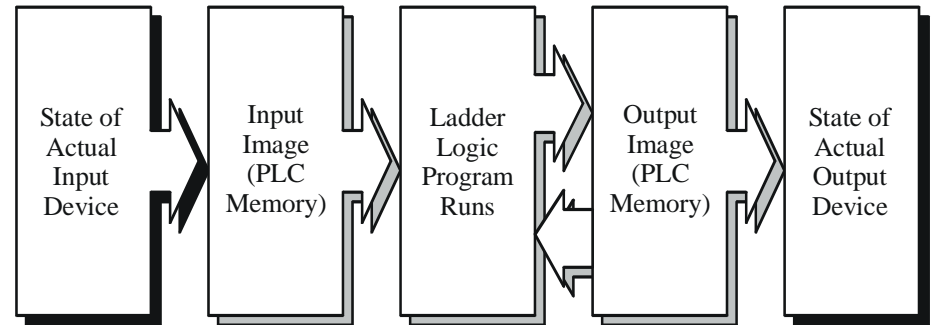- The state of actual input devices are copied to an area of the PLC Memory, **input data table** **before** the ladder logic program executes



- As the ladder logic program is scanned, it reads the input data table then writes to a portion of PLC memory - **the output data**, table as it executes
- The output data table is copied to the actual output devices **after** the ladder logic has been scanned.

What is the significance of the input and output data tables?

Typical PLC Processor Scan

Allen-Bradley RSLogix 5000

The execution of PLC Processor controlled by processor mode (Refer to lab 1)

- Run Mode:
 - Physical Input, Physical Outputs and Ladder logic all get scanned
- Remote Mode
 - Down load ladder logic to PLC Processor; and initiate scan from the remote terminal
- Program Mode
 - Ladder logic not scanned



Ladder Logic Evaluation

- For most PLC's, the ladder scan starts at the top of the ladder and proceeds to the bottom of the ladder, examining each rung from left to right.
 - Once a rung is examined, it is not examined again until the **next** scan.
 - The rungs are not examined in reverse order.
- The JMP instruction may be used to jump back up the ladder and execute earlier rungs.
 - Use of JMP not recommended **Why?**

Ladder Logic Evaluation

Push Button (PB)

Start PB:

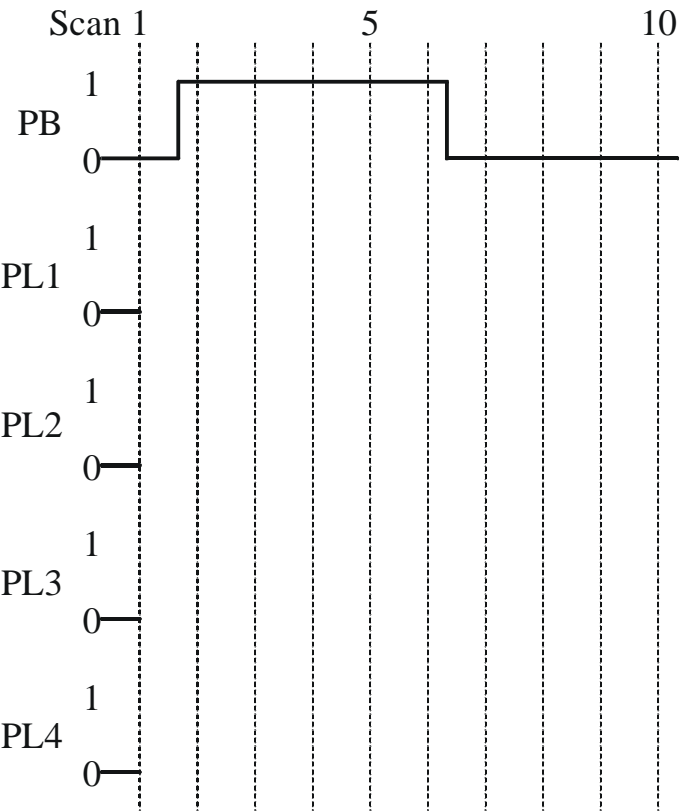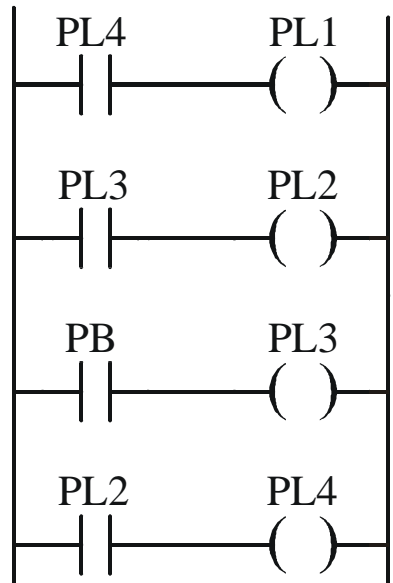

Physical Input: PB

Physical Outputs: PL1, PL2, PL3 and PL4

Start of PLC scans

State of PLC image memory for I/O devices:

Ladder Logic Evaluation

Push Button (PB)

Scan 1: Only the state of PB changes to **ON (1)** during the scan


Scan 2:
The **ON** state of PB is copied into Input data table before Ladder logic is scanned

When rung 1 is scanned → PL1 is still off (0)
When rung 2 is scanned → PL2 is still off (0) Why?
What is the value of PL4 and PL3 in Output Data table?

When rung 3 is scanned the Value of PL3 in the output data table changes to 1 Why?

When rung 4 is scanned, the Value of PL4 in the output data table remains at off (0). Why?

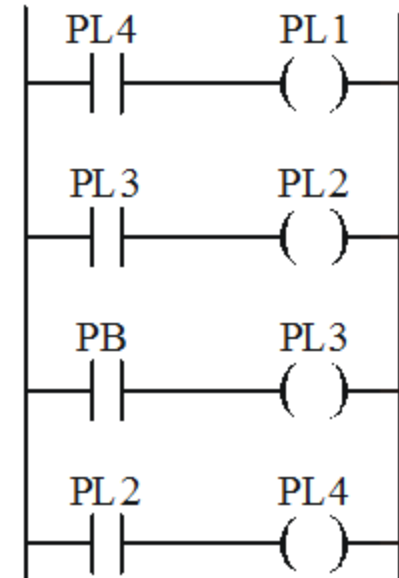At the end of scan 2 the values in Output data table are copied to the Physical Output Devices. **PL 3 turns on**



Ladder Logic Evaluation

Push Button (PB)

Scan 3:


When rung 1 is scanned the value of PL4 in output data table is still 0 → PL1 in output data table remains 0

When rung 2 is scanned the value of PL3 in Output Data table is currently 1 → value of PL2 in Output Data table changes to 1

When rung 3 is scanned the Value of PB in the input data table is still 1 → Value of PL3 in Output data table remains at 1

When rung 4 is scanned Value of PL2 in the output data table is now 1 so the value of PL4 in the Output Data table changes to 1

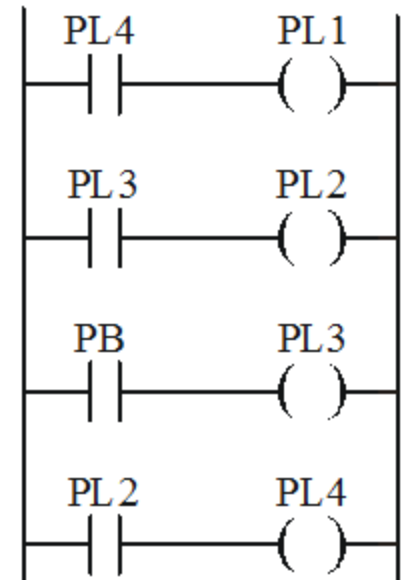At the end of scan 3 the values in Output data table are copied to the Physical Output Devices:
PL2 and PL4 turn on simultaneously
(PL3 remains on)



Ladder Logic Evaluation

Push Button (PB)

Scan 4:


When rung 1 value of PL4 in output data table is now 1

→ value of PL1 in output data table changes to 1

When rung 2 is scanned the value of PL3 in Output Data table is still 1 → value of PL2 in Output Data table remains at 1

When rung 3 is scanned the Value of PB in the input data table is still 1 → Value of PL3 in Output data table remains at 1

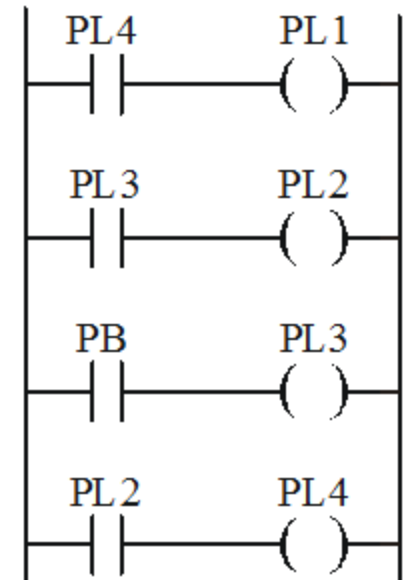When rung 4 is scanned Value of PL2 in the output data table is still 1 so the value of PL4 in the Output Data table remains at 1



At the end of scan 4 the values in Output data table are copied to the Physical Output Devices:

PL1 turns on


(PL2, PL3 and PL4 remain on)

Ladder Logic Evaluation

Push Button (PB)


Scans 5 and 6: Nothing Changes

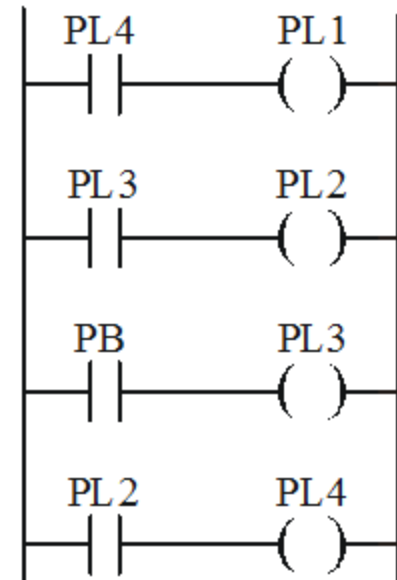Scans 7 – 9 : Similar to Scans 2 – 4 except that state changes from 1 (on) to 0 (off)



Ladder Logic Evaluation

Push Button (PB) Scan Timing Diagram

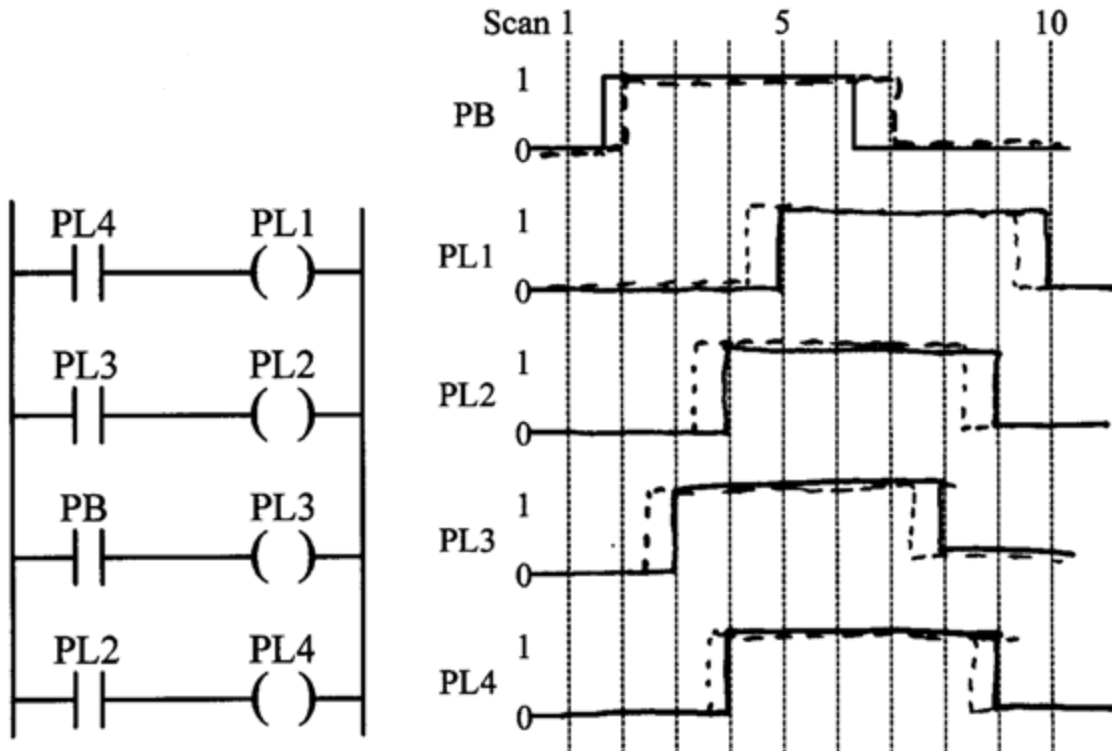



I/O Terminal: -----

I/O Data Table: _____

Ladder Logic Evaluation

Push Button (PB1)

Assume rungs are scanned from top - down

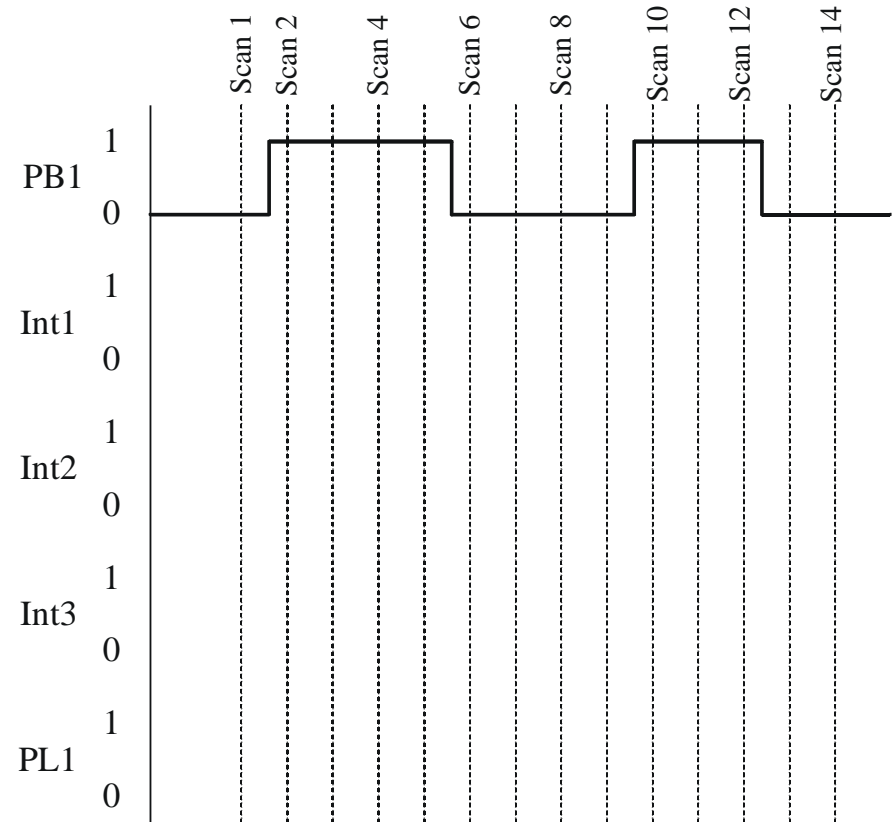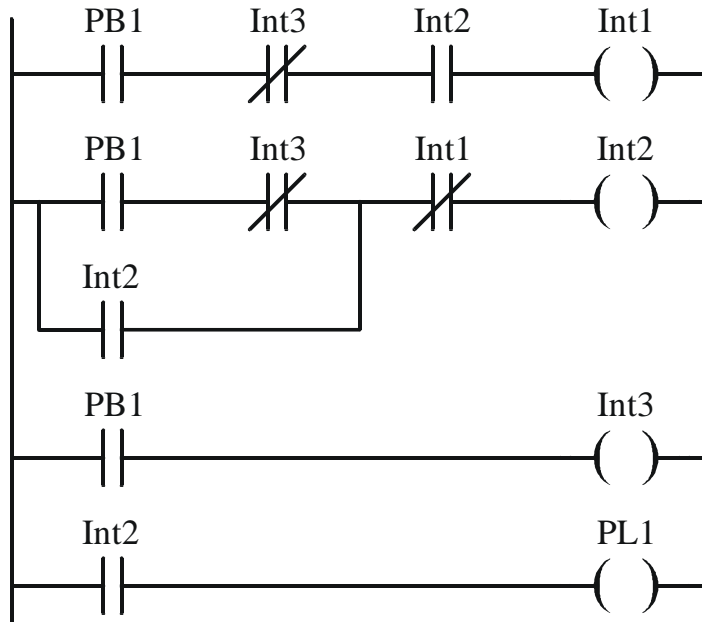

Physical Input: PB1

Physical Output: PL1

Ladder Logic Evaluation

Push Button (PB1)

Scan 1: Only the state of PB1 changes to **ON (1)**
during the scan, new state copied at next scan


Scan 2:
The **ON** state of PB1 is copied into Input data table
before Ladder logic is scanned

When rung 1 is scanned, PB1 is ON, Int3 is off so power goes to Int2, But Int2 is off → Int1 is off (0)

When rung 2 is scanned PB1 is ON, Power goes thru' Int3 and Int1 → Int2 is On

When rung 3 is scanned the Value of PB1 in the input data table is now 1 so Int3 is energized and Int3 contact is ON

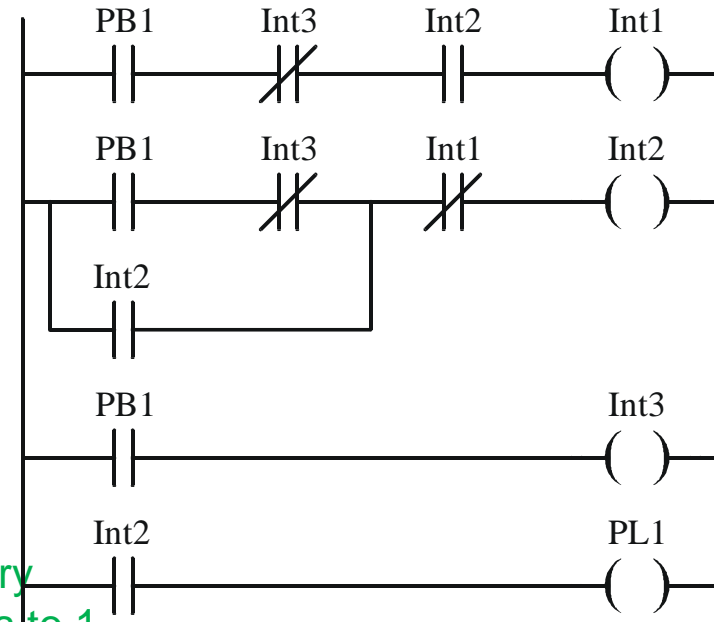When rung 4 is scanned, the Value of Int2 in the PLC memory is now 1 so the value of PL1 in the Output data table changes to 1



At the end of scan 2 the values in Output data table are copied to the Physical Output Devices. **PL1 turns on**


Ladder Logic Evaluation

Push Button (PB1)

Scan 3: No change in the rung output coils

When rung 1 is scanned There is continuity thru' PB1 and Int2 but not Int3

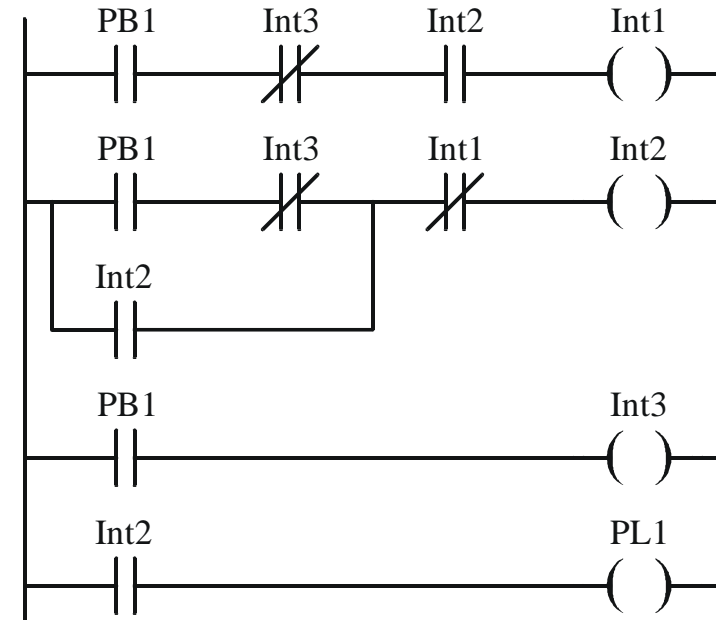When rung 2 is scanned – no continuity thru' top branch
But continuity thru' lower branch → Int2 remains ON




At the end of scan 3 the values in Output data table are copied to the Physical Output Devices. **PL1 remains on**

Ladder Logic Evaluation

Push Button (PB1)

Scans 4 - 5:

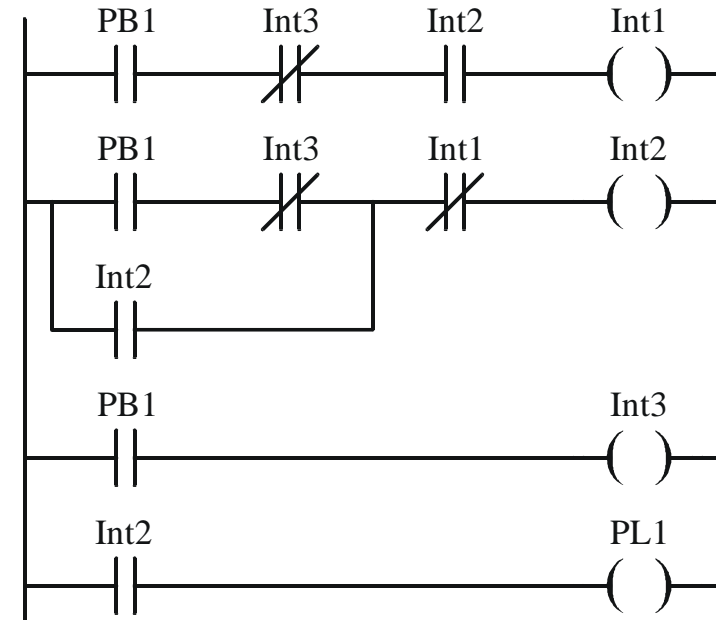
No change in the rung output coils because there is no change in the contacts



At the end of scans 4 and 5 the values in Output data table are copied to the Physical Output Devices. **PL1 remains on**



Discrete Input/Output

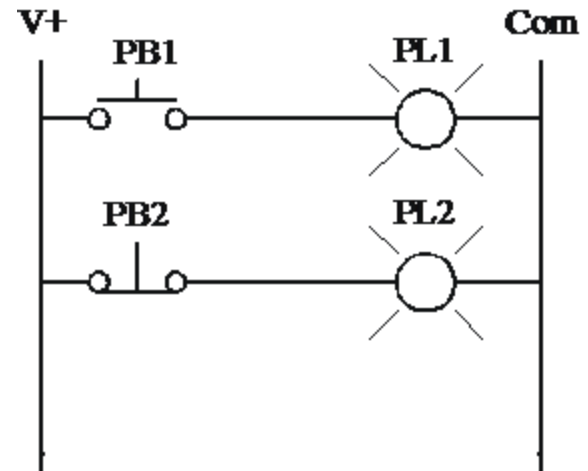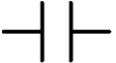- An actual PLC has connections to the “real” world, and is not just ladder logic.



An example hard-wired ladder circuit

Programming with NC Contacts

- If you want “action” (turn ON) when switch is closed (relay energized), use . 
- If you want “action” (turn ON) when switch is open (relay de-energized), use . 
-

In the rungs, think of the contact as a symbol,

 = ON = CLOSED = TRUE = 1

 = OFF = OPEN = FALSE = 0

Note: this is probably the most confusing concept in ladder logic